

Mechanical Engineering

Question 1

$$V = 415\text{V} \quad \text{P.F.} = 0.7$$

$$P = 80\text{H}_3 \quad \text{Power adjusted} = 74.6\text{kW}$$

Unity 1

$$C = \frac{\text{KWAR}}{\text{KW}} = 0$$

$$C = \frac{2\pi f V^2}{\dots}$$

$$\text{KWAR} = P \times (\tan \text{actual p.f.} - \tan \text{target p.f.})$$

$$\text{actual p.f.} = \cos \theta = 0.7$$

$$\theta = \cos^{-1}(0.7)$$

$$\theta = 45.57$$

$$\tan(45.57) = 1.0201$$

$$\text{target p.f.} = \cos \theta = 1$$

$$\theta = \cos^{-1}(1)$$

$$\theta = 0$$

$$\tan(0) = 0$$

$$\text{KWAR} = 74.6 \cdot (1.0201 - 0)$$

$$\approx 76$$

$$C = \frac{76}{\dots}$$

$$2\pi \times 50 \times 415^2$$

$$\approx 21.4 \times 10^6 \text{ C}_3$$

Question 1

Longing 0.9

Actual P.F = 1.0201

Target P.F = $\cos \theta = 0.7$

$$\theta = \cos^{-1}(0.7)$$

$$\theta = 154.16^\circ$$

$$\tan(154.16) = -0.48$$

$$\text{ICVAR} = 74.6 (1.0201 - \cos \theta)$$

$$= 111.9$$

$$\approx 112$$

$$L = \frac{112}{2 \times 60 \times 418^2}$$

$$= 9.92 \times 10^{-7} \text{ s}$$

$$\approx 9.92 \times 10^{-7} \text{ s}$$

Question 2

$N = 415 \text{ r/min}$


$f = 50 \text{ Hz}$

$p = 6 \text{ poles}$

$s = \frac{5}{6} = 0.833$

$R = Z_1 = 0.25 + j0.75$

$Z_2 = 1.173 + j0.52$

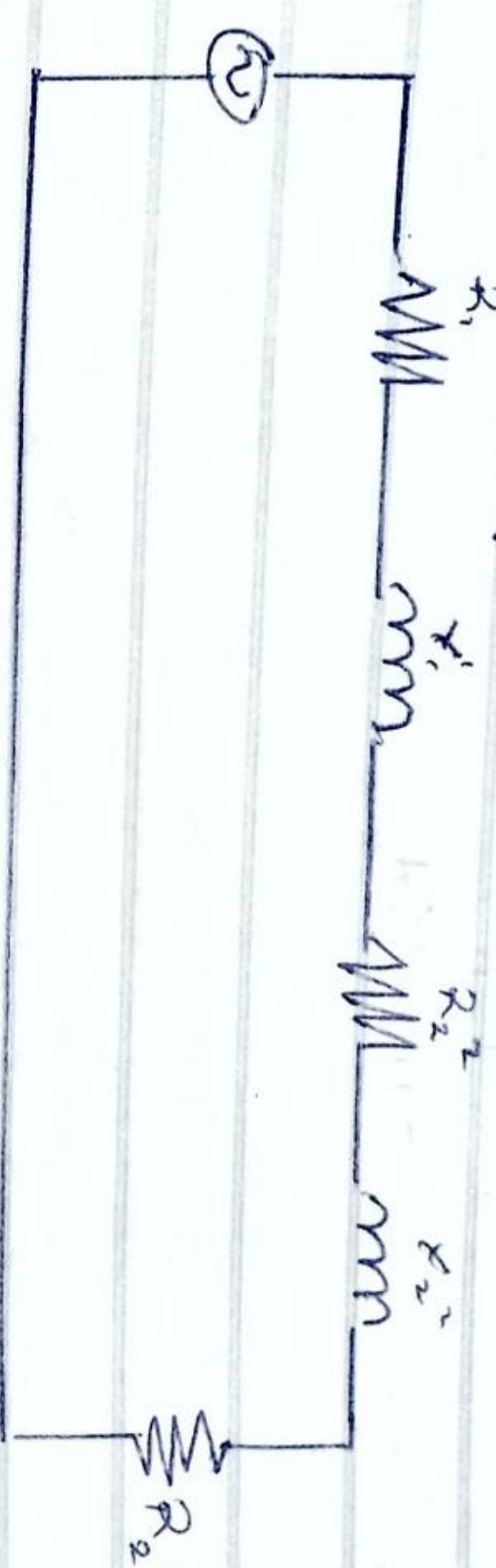

Supply voltage per phase, $V = \frac{415}{\sqrt{3}} = 237.60 \text{ V}$

Rotor

$R_{02} = (R_2 + k^2 R_1)$

$= (1.173 + (0.833^2) \times 0.25)$

$R_{02} = 1.347 \Omega$

$X_{02} = (X_2 + k^2 X_1)$

$= (0.52 + (0.833^2) \times 0.75)$

$= 1.041$

$Z_{02} = R_{02} + jX_{02}$

$= 1.347 + j1.041$

$= \sqrt{1.347^2 + 1.041^2}$

$Z_{02} = 1.7 \Omega$

17/eng 06/01
Mechanical Engineering

300244

Question 2

Rotational

$$\Rightarrow T_2 = \frac{F_2}{20}$$

Recall $F_2 = 10 \text{ kN}$

$$= 239.6 \times 0.8$$

$$= 191.67 \text{ N}$$

$$T_2 = \frac{191.67}{1.7}$$

$$= 112.75 \text{ N}$$

Question 3

$P = 50 \text{ kW}$

$I = 0.74$

$R = 15 \Omega$

$N = 2200 \text{ rpm}$

$N_2 = 2000 \text{ rpm}$

$Z = 0.25 \text{ M}$

$\frac{I}{N_1} = \frac{N_2}{N_1} = \frac{T_{b2}}{T_{b1}}$

$v - T_b = I_L \cdot R$

so $\frac{T_{b2}}{T_{b1}} = \frac{N_2}{N_1}$

$v - [I_L \cdot R] = T_b$

$T_{b2} \cdot N_2 = T_{b1} \cdot N_1$

$T_b = 2200 - [0.74 \cdot 15]$

$= 209.5 \text{ N}$

$M_{ac} = 2000 \times \frac{202.52 \text{ N}}{209.5 \text{ V}}$

$M_{ac} = 1933.37 \text{ rpm}$

Power factor, $\cos \phi = \frac{T_{b2} + I \cdot R}{v}$

$= \frac{202.52 + 10.5}{220}$

$\rightarrow 0.968 \text{ lagging}$

developed; $T_w = T_{b2} \times I$

$T_{ac} = \frac{T_{b2} \times I}{w}$

where $w = \text{speed in rad/s}$

$w = 2\pi \times N$

where $N = \text{speed in rpm}$

$T_{ac} = \frac{T_{b2} \times I}{2\pi \times \frac{N_{ac}}{60}}$

$T_{ac} \rightarrow \frac{202.52 \times 0.74 \times 60}{2\pi \times 1933.37}$

$= 0.100 \text{ Nm}$

17/eng 06/02
Mechanical Engineering

300/AL

Question 3

AC Suppl.

~~Supply~~ Voltage = 220V

$$\text{Current} = I_L = 0.7A$$

$$\text{Resistance drop} = I_L * R = 0.7 * 15 = 10.5V$$

$$\text{Reactance voltage drop} = I_L * X_L = 0.7 * 20 \mu\Omega$$

$$\text{where } X_L = \mu\omega L = 20 \mu\Omega$$

$$= 0.7 * 20 \times 10^{-6} * 50 * 0.25 \\ = 54.98V$$

$$E_{\text{base}} = \sqrt{V^2 - I^2 X_L^2} - IR$$

$$= \sqrt{220^2 - 54.98^2} - 10.5$$

$$E_{\text{base}} = 202.52V$$