
 


4 Bit Binary Counter

 

J-K truth table

J	K	Output
0	0	No change
0	1	Reset (0)
1	0	Set (1)
1	1	Toggle



Timing diagram

Binary Counting System

Q ₃	Q ₂	Q ₁	Q ₀	
0	0	0	0	Before applying clock pulse
0	0	0	1	After pulse 1
0	0	1	0	✓ 2
0	0	1	1	✓ 3
0	1	0	0	✓ 4
0	1	0	1	✓ 5
0	1	1	0	✓ 6
0	1	1	1	✓ 7
1	0	0	0	✓ 8
1	0	0	1	✓ 9
1	0	1	0	✓ 10
1	0	1	1	✓ 11
1	1	0	0	✓ 12
1	1	0	1	✓ 13
1	1	1	0	✓ 14
1	1	1	1	✓ 15
0	0	0	0	✓ 16 (Returns to 0)
0	0	0	1	✓ 17
0	0	1	0	✓ 18
0	0	1	1	✓ 19



2) MOD Number = $2^6 = 64$

ii) Frequency at the last flip flop will equal the input clock frequency divided by mod number.

$$\Rightarrow \text{frequency at } Q_3 = \frac{1 \text{ MHz}}{64} = 15.625 \text{ KHz}$$

iii) The counter will count from 000000 to 111111 a total of 64 states

 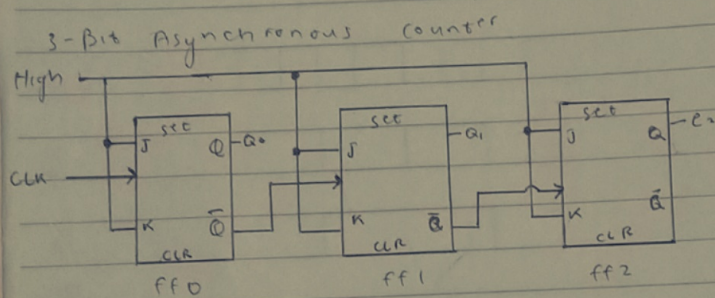iv) It is a MOD-64 counter, so every 64 pulses will bring the counter back to its initial state therefore after 128 pulses, the counter is back to 000000 and after the 129th pulse it brings the counter to 000001 state.



Timing diagram

Truth Table

State	Q_0	Q_1	Q_2
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1