

17/EM606/080 3002

1)  $V = 415V$ ,  $3-\phi$ ,  $A = 400A$ ,  $f = 50 \text{ Hz}$ ,  $P = 74.6$ ,  $P.F. = 0.7$   
 $\% \text{ eff} = 85\%$

b

i)  $V_{\text{avg}} = 1$

$C = 1200 \mu F$

2)  $P.F.$

$-7 \text{ KVAR} = P \times (\tan \text{ actual } P.F. - \tan \text{ target } P.F.)$

Actual  $P.F. = 0.7$

$\theta = \cos^{-1} 0.7$

$= 45.57$

$\tan (45.57) = 1.0201$

target  $P.F. = 1$

$\theta = \cos^{-1} 1 = 0$

$\tan 0 = 0$

$1200A = 74.6 \times (1.0201 - 0)$

$C = \frac{74.6}{10}$

$\lambda \times 11150 \times 45.2$

$= 0.00004$

$\Rightarrow 1.4 \times 10^{-6} \mu$

(ii) 0.9 lagging

Actual  $P.F. = 1.0201$

target  $P.F. = 1.0201 = -0.9$

$\theta = \cos^{-1} (-0.9)$

$= 154.16$

$\tan \theta = -0.44$

$1200A = 74.6 \times (1.0201 - (-0.44))$

$= 111.90 \approx 112$

$$C = \frac{12 \text{ VAR}}{2\pi fV}$$

$$= \frac{1129}{2\pi \times 50 \times 415}$$

$$= 2.07 \times 10^{-6}$$

$$\approx 2.07 \times 10^{-6}$$

$$\approx 2.07 \times 10^{-6}$$

17/ENG06/080


3002

(2)

$$V_{LL} = 415V, \text{ H.P.} = 9, \text{ P.F.} = 0.8, f = 50\text{Hz}, \lambda = \frac{5}{6} = 0.83$$

$$Z_1 = 0.25 + j0.75 \quad \text{--- 7 stator}$$
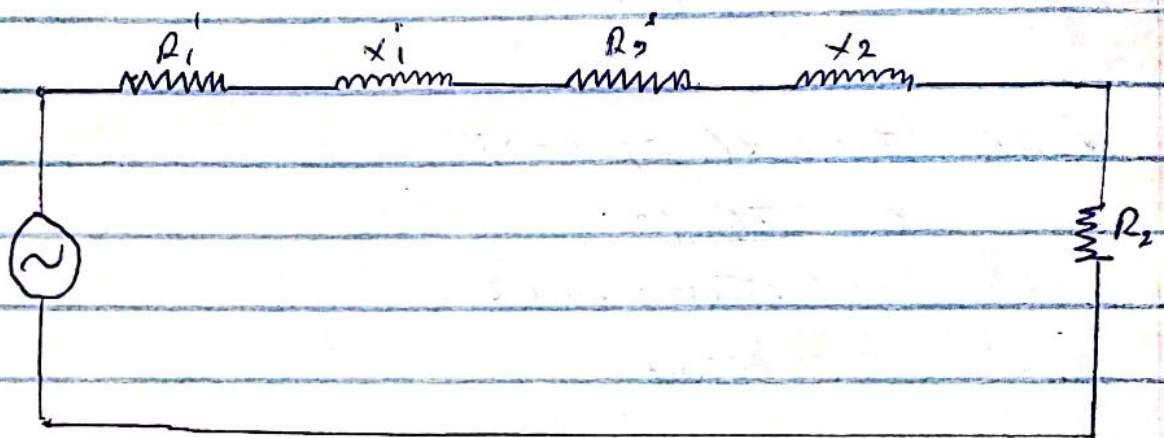
$$Z_2 = 1.173 + j0.52 \quad \text{--- 7 stator}$$



Supply Voltage per phase,  $V = \frac{415}{\sqrt{3}} = 239.60V$

Referring to rotor

$$R_{02} = (R_2 + \lambda^2 R_1)$$

$$= (1.173 + (\frac{5}{6})^2 \times 0.25)$$

$$R_{02} = 1.347 \Omega$$

$$X_{02} = (X_2 + \lambda^2 X_1)$$

$$= j(0.52 + (\frac{5}{6})^2 \times 0.75)$$

$$= 1.041$$

$$Z_{02} = R_{02} + X_{02}$$
$$= 1.5471 + j 1.041$$

$$Z_{02} = \sqrt{1.547^2 + 1.041^2}$$
$$= 1.72$$

To find refer current

$$I_2 = \frac{E_2}{Z_{02}}$$

Recall that  $E_2 = 120V$

$$= 239.6 \times 0.85$$

$$= 199.67V$$

$$\therefore I_2 = \frac{199.67}{1.7} = 117.45 \text{ A}$$

17/EN16061080 3002.

(3)


$f = 50\text{Hz}$ ,  $1/4\text{hp}$ ,  $N_2 = 2000\text{rpm}$ ,  $V = 220$

$15\Omega$  and  $0.25\text{H}$

On DC supply

Supply Voltage =  $220\text{V}$

Current drawn,  $I = 0.7\text{A}$

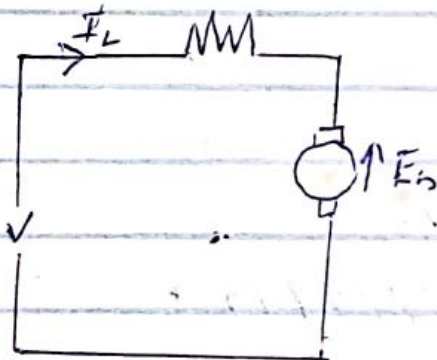

$$V - E_b = I_L \times R$$

$$V - [I_L \times R] = E_b$$

$$E_b = 220 - [0.7 \times 15]$$

$$= 209.5\text{V}$$

Speed on DC

$$N_{dc} = 2000\text{rpm}$$

On AC supply

Supply Voltage =  $220\text{V}$


Current drawn,  $I_L = 0.7\text{A}$

$$\text{Reactance drop} = I_L \times R = 0.7 \times 15 = 10.5 \text{ V}$$

$$\text{Reactive Voltage drop} = I_L \times X_L = 0.7 \times 2\pi f L$$

$$\text{Where } X_L = \omega L = 2\pi f L$$
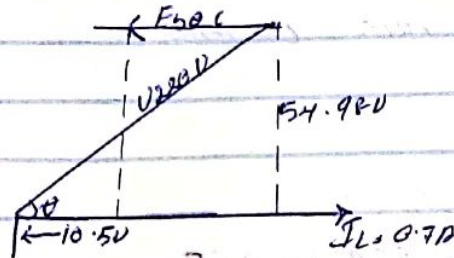
$$= 0.7 \times 2\pi \times 30 \times 0.25 = 54.98 \text{ V}$$



$$E_b = \sqrt{V^2 - [X_L]^2} - IR$$

$$= \sqrt{(220)^2 - (54.98)^2} - 10.5 \text{ V}$$

$$= 202.52 \text{ V}$$

⇒ Review speed. (constant equation)

$$N_s = E_b, \quad \text{So } E_{b1} = N_{s1}$$

$$N_1, \quad E_{b1}, \quad E_{b2}, \quad N_2$$

making  $N_{s1}$  subject of the formula

$$N_{s1} = N_{s2} \times \frac{E_{b2}}{E_{b1}} = \frac{2000 \times 202.52}{209.5}$$

$$N_{s1} = 1933.37 \text{ rpm}$$

$$\text{power factor, } \cos \phi = \frac{E_{b1} + IR}{V}$$

$$= \frac{202.52 + 10.5}{220} = 0.965$$

$$\text{Torque developed } [W = E_{b1} \times I]$$

$$T_{dev} = \frac{E_{b1} \times I}{\omega}$$

Review speed. (constant equation) where  $\omega$  is speed

$$\text{in rad/s, } \omega = 2\pi n, \quad \text{where } n \text{ is rpm}$$

$$T_{dev} = \frac{E_{b1} \times I}{2\pi \times \frac{N_{s1}}{60}} = \frac{202.52 \times 0.7 \times 60}{2\pi \times 1933.37}$$

$$= 0.700 \text{ Nm}$$