

MANASSEE DAVID

15/ENUG2/036

COE 506

- ① $A(x_1, x_2, x_3, x_4) = \sum m(3, 7, 8, 9, 11, 15)$
 $B(x_1, x_2, x_3, x_4) = \sum m(3, 4, 5, 7, 10, 14, 15)$
 $C(x_1, x_2, x_3, x_4) = \sum m(1, 5, 7, 11, 15)$

TRUTH TABLE

x_1	x_2	x_3	x_4	A	B	C
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	0
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	0
1	1	1	0	0	1	0
1	1	1	1	1	1	1

Output A:

$x_3 \backslash x_2$	00	01	11	10
00	0	0	0	1
01	0	0	0	1
11	1	1	1	1
10	0	0	0	0

$$A = x_2 \bar{x}_3 + x_3 x_4$$

Output B:

x_3/x_2	00	01	11	10
00	0	1	0	0
01	0	1	0	0
11	1	1	1	0
10	0	0	1	1


$$B = \bar{x}_1 x_2 \bar{x}_3 + \bar{x}_1 x_3 x_4 + x_2 x_3 x_4 + x_1 x_3 \bar{x}_4$$

Output C:

x_3/x_2	00	01	11	10
00	0	0	0	0
01	1	1	0	0
11	0	1	1	1
10	0	0	0	0

$$C = \bar{x}_1 \bar{x}_3 x_4 + x_2 x_3 x_4 + x_1 x_3 x_4$$

Logic Circuit Diagram:

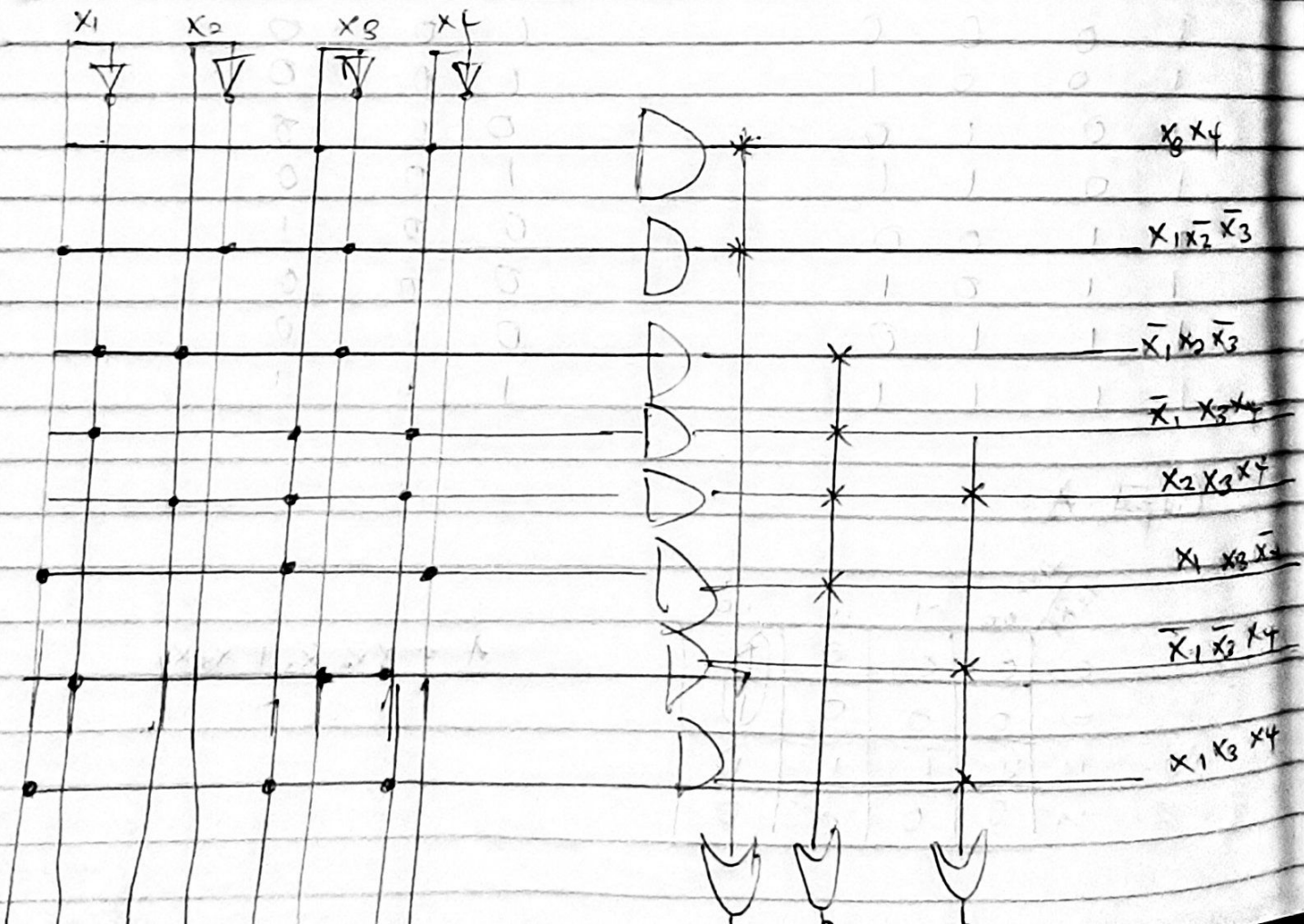


(2) (i) $2^4 = 16$ states

TRUTH TABLE:

S_{W1}	S_{W2}	S_{W3}	S_{W4}	X (output)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	X
1	0	1	0	1
1	0	1	1	X
1	1	0	0	1
1	1	0	1	X
1	1	1	0	1
1	1	1	1	X

$S_{W3} S_{W4}$ \ $S_{W1} S_{W2}$	00	01	11	10
00	0	0	1	0
01	1	1	X	X
11	1	1	X	X
10	0	1	1	1
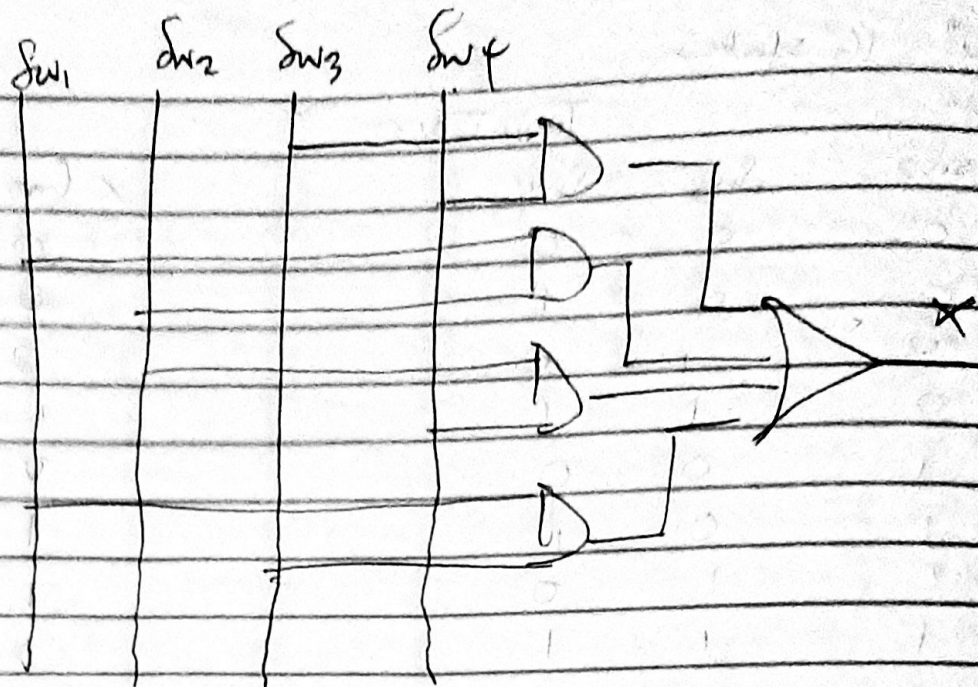
$$X = S_{W3} S_{W4} + S_{W1} S_{W2} + S_{W2} S_{W4} + S_{W1} S_{W3}$$



Code:

```

library IEEE;
use IEEE.Std.Logic.1164;
entity Switches is
port Swa, Swb, Swc, Swd: In
Std.Logic; x: Out Std.Logic;

```

end Switches.

```

Architecture Dataflow of Switches is
begin x <= (Swc and Swd) or
(Swa and Swb) or
(Swb and Swd) or
(Swa and Swc);

```

end data flow;