

DEVIAR ATTORNY

15/ENG05/006

MCT 510

Assignment 3

1) Prove that ripple factor  $[R.F.] = [F.F^2 - 1]^{0.5}$

Ripple factor =  $\frac{\text{RMS value of the AC voltage (input)}}{\text{D.C voltage (output of rectifier)}}$

$$r.f = \frac{V_{rms}}{V_{dc}}$$
$$V_{rms} = \sqrt{V_{rms}^2 - V_{d.c}^2}$$

$$r.f = \sqrt{\left(\frac{V_{rms}}{V_{d.c}}\right)^2 - 1}$$

Recall  $F.F = V_{rms}/V_{dc}$

$$r.f = \sqrt{F.F^2 - 1}$$

$$R.F = [F.F^2 - 1]^{0.5}$$

a) Assuming  $R.F = 10\%$

$$R_{total} = R + R_f = 50 + 10 = 60\Omega$$

i)

$$I_{dc} = \frac{1}{T} \int_0^T I_m \sin \omega t d(\omega t)$$

$$= \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t d(\omega t)$$

$$= \frac{I_m}{2\pi} [-\cos \omega t]_0^{\pi}$$

$$= \frac{I_m}{2\pi} [-\cos \pi - [-\cos 0]]$$

$$= \frac{I_m}{2\pi} [-[-1] - [-1]] \quad \text{where } \pi = 180$$

$$I_m = V_m/R \quad ; \quad V_m = 110V$$

$$\frac{V_m}{2\pi R} [2] = \frac{V_m}{\pi R} = \frac{110}{\pi \times 60}$$

$$I_{dc} = 0.5835A$$

ii)  $V_{dc} = I_{dc} \times R_L$  where  $R_T = R + R_f$

$$= 0.5835 \times (50 + 10)$$

$$= 35.01V$$

$$3) I_{rms} := \left[ \frac{1}{T} \int_0^T V_m^2 \sin^2 \omega t \, d(\omega t) \right]^{0.5}$$

$$= \left[ \frac{V_m^2}{2T(R+R_f)} \int_0^T \sin^2 \omega t \, d(\omega t) \right]^{0.5}$$

Recall  $\sin^2 \theta = \frac{1 - \cos 2\theta}{2}$

$$= \left[ \frac{V_m^2}{2T(R+R_f)} \int_0^T \left( \frac{1 - \cos 2\omega t}{2} \right) d(\omega t) \right]^{0.5}$$

$$= \left[ \frac{V_m^2}{4T(R+R_f)} \int_0^T d(\omega t) - \frac{\cos 2\omega t}{2} d(\omega t) \right]^{0.5}$$

$$= \frac{V_m^2}{4T(R+R_f)} \left[ \left. \frac{d\omega t}{2} \right|_0^T - \left. \frac{\sin 2\omega t}{2} \right|_0^T \right]^{0.5}$$

$$= \frac{V_m^2}{4T(R+R_f)} [\pi - 0] - \left[ \frac{\sin 2\pi}{2} - \frac{\sin 0}{2} \right]^{0.5}$$

$$= \left[ \frac{V_m^2}{4T(R+R_f)} \pi \right]^{0.5}$$

$$= V_m / 2(R+R_f)$$

$$= \frac{110}{2(50+10)} = 0.917 A$$

$$4) V_{rms} = I_{rms} \times (R+R_f) \\ = 0.917 \times (60+10) \\ = 55 V$$

$$5) P_{dc} = V_{dc} \times I_{dc} \\ = 35.01 \times 0.5825 \\ = 20.43 W$$

$$6) P_{ac} = V_{rms} \times I_{rms} \\ = 55 \times 0.917 \\ = 50.4 W$$

$$7) \text{Efficiency} = \frac{P_{dc}}{P_{ac}} = \frac{20.43}{50.4} = 0.405 \%$$

$$8) f \cdot f = \frac{V_{rms}}{V_{dc}} = \frac{55}{35.01} = 1.57$$

$$\begin{aligned} R.F &= [F \cdot f^2 - 1]^{-0.5} \\ &= [1.571^2 - 1]^{-0.5} \\ &= 1.212 \end{aligned}$$

$$7 \quad T.H.F = 2\sqrt{2} / \pi^2 = 0.289$$

$$9 \quad P.V = V_m = 110V$$

$$10 \quad C.F = 2V_m / V_m = 2.$$