

ERIC PATRICK INI-OBONG


16 / ENG 04 / 018

Electrical / Electronics Engineering

EEE 561 [ASSIGNMENT]

Derive the analysis for the output voltage in using Operational Amplifier for

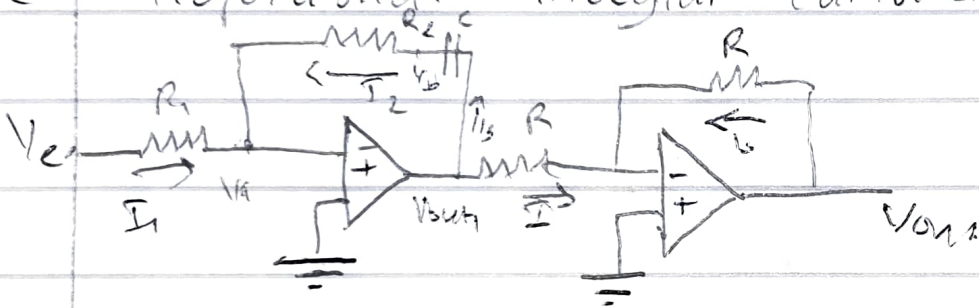(i) Proportional integral controller mode



$$V_{out2} = \frac{-R}{R} (V_{out1}) = -V_{out1} \quad \text{[Inverting Co. cont.]}$$

PI Controller \$V_e = 0\$

$$I_1 + I_2 = 0 \quad \text{--- (1)}$$

$$I_3 - I_2 = 0 \quad \text{--- (2)}$$

Current through the capacitor

$$I_C = C \frac{dV_C}{dt}$$

$$I_1 = \frac{V_e - V_A}{R_1} = \frac{V_e}{R_1}$$

$$I_2 = \frac{V_B - V_A}{R_2} = \frac{V_B}{R_2}$$

$$I_3 = C \frac{d(V_{out1} - V_B)}{dt}$$

from eqn (1) $\frac{V_e}{R_1} + \frac{V_B}{R_2} = 0$

$$V_b = -\frac{R_2}{R_1} V_e$$

from eqn 2 $\frac{C d(V_{out1} - V_b)}{dt} - \frac{V_b}{R_2} = 0 \quad \text{--- (3)}$

take the Laplace transform of eqn (3) above

$$sC(V_{out1}(s) - V_b(s)) - \frac{V_b(s)}{R_2} = 0$$

$$sC V_{out1}(s) = sC V_b(s) + \frac{V_b(s)}{R_2}$$

$$sC V_{out1}(s) = V_b(s) \left(sC + \frac{1}{R_2} \right)$$

$$V_b = -\frac{R_2}{R_1} V_e$$

$$\therefore sC V_{out1}(s) = -\frac{R_2}{R_1} V_e(s) \left(sC + \frac{1}{R_2} \right)$$

divide by sC

$$V_{out1}(s) = \frac{-R_2}{sCR_1} V_e(s) \left(sC + \frac{1}{R_2} \right)$$

(the brackets)

$$V_{out1}(s) = -\frac{R_2}{R_1} V_e(s) + -\frac{R_2}{R_1} \frac{1}{sCR_2} (V_e(s))$$

from the balancing circuit

$$V_{out}(s) = -V_{out1}$$

$$\hat{\Delta} V_{out} = - \left(- \frac{R_2}{R_1} (V_{in}(s)) - \frac{R_2}{R_1} \frac{1}{sCR_2} V_{in}(s) \right)$$

$$V_{out}(s) = \frac{R_2}{R_1} V_{in}(s) + \frac{R_2}{R_1} \frac{1}{sCR_2} V_{in}(s)$$

taking the inverse Laplace

$$V_{out} = \frac{R_2}{R_1} V_{in} + \frac{R_2}{R_1} \frac{1}{R_2 C} \int_0^t V_{in}(t) dt + V_{out}(0)$$

(where $\frac{1}{s} = \int_0^t dt + K$, $K = \text{Constant of integration}$)


$$V_{out} = G_p V_{in} + G_p G_I \int_0^t V_{in} dt + V_{out}(0)$$

where $G_p = \frac{R_2}{R_1}$ (Proportional gain)

$G_I = \frac{1}{R_2 C}$ (Integral gain)

Proportional Derivative Controller

Mode Design

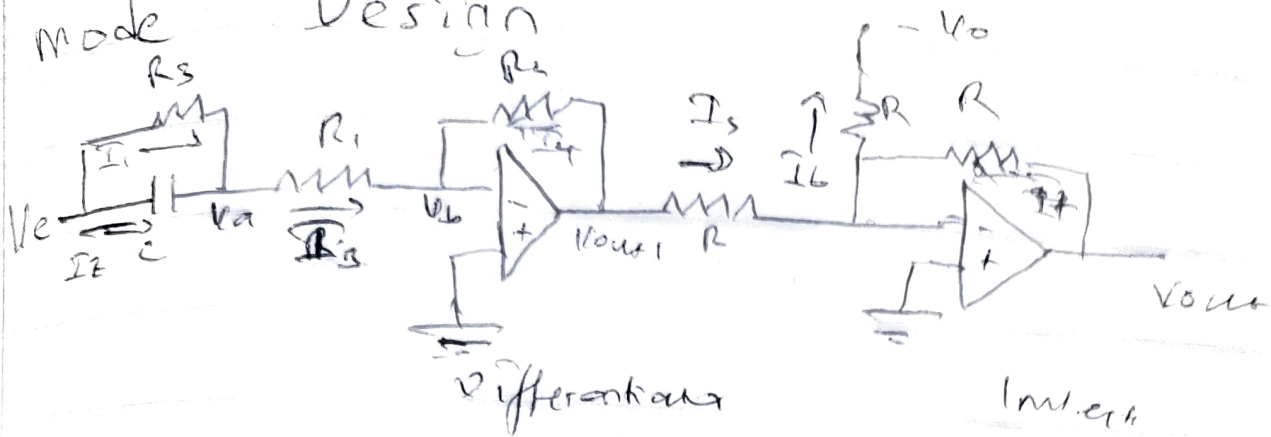

PD Controller: ($T_a \ll T_s$ $\ll CL$)

$$I_1 + I_2 = I_3 \quad \text{--- (1)}$$

$$I_3 + I_4 = 0 \quad \text{--- (2)}$$

from eqn (1)

$$\frac{V_e - V_a}{R_3} + C \frac{d(V_e - V_a)}{dt} = \frac{V_a}{R_1} \quad \text{--- (3)}$$

from eqn (2)

$$\frac{V_a}{R_1} + \frac{V_{out1}}{R_2} = 0 \quad \text{--- (4)}$$

$$V_a = -\frac{R_1}{R_2} V_{out1}$$

from eqn (3)

$$\frac{V_e - V_a}{R_3} + C \frac{d(V_e - V_a)}{dt} - \frac{V_a}{R_1} = 0$$

for

$$I_1 = \frac{V_e - V_a}{R_3}$$

$$I_2 = C \frac{d(V_e - V_a)}{dt}$$

$$I_3 = \frac{V_a}{R_1} \quad (V_b = 0)$$

$$I_3 = \frac{V_a}{R_1}$$

$$I_4 = \frac{V_{out1} - V_b}{R_2}$$

$$(V_b = 0)$$

$$I_4 = \frac{V_{out1}}{R_2}$$

effective res.

$$R = \frac{R_1 R_3}{R_1 + R_3}$$

$$R_1 + R_3$$

taking Laplace transform of eqn (3)

$$\frac{V_e - V_a(s)}{R_3} + sC(V_e(s) - V_a(s)) - \frac{V_a(s)}{R_1} = 0$$

$$1. \frac{V_e}{R_3} - \frac{V_a}{R_3} + sC(V_e(s) - V_a(s)) - \frac{V_a(s)}{R_1} = 0$$

rearrange

$$\frac{V_e}{R_3} + sC V_e(s) = \frac{V_a(s)}{R_1} + \frac{V_a(s)}{R_3} + sC V_a(s)$$

$$V_e(s) \left(\frac{1}{R_3} + sC \right) = V_a(s) \left(\frac{1}{R_1} + \frac{1}{R_3} + sC \right)$$

Eqn $V_a = \frac{-R_1}{R_2} V_{out}$

$$V_e(s) \left(\frac{1}{R_3} + sC \right) = \frac{-R_1}{R_2} V_{out} \left(\frac{1}{R_1} + \frac{1}{R_3} + sC \right)$$

$$V_e(s) \left(\frac{1 + R_3 sC}{R_3} \right) = \frac{-R_1}{R_2} V_{out} \left(\frac{R_3 + R_1 + sC R_1 R_3}{R_1 R_3} \right)$$

multiply

through by R_3

$$V_e(s) \left(\frac{1 + R_3 sC}{R_3} \right) \times R_3 = \frac{-R_1}{R_2} V_{out} \left(\frac{R_3 + R_1 + sC R_1 R_3}{R_3} \right) \times R_3$$

$$V_e(s) (1 + R_3 sC) = \frac{-V_{out}(s)}{R_2} (R_3 + R_1 + sC R_1 R_3)$$

method V_{out} subject

$$-V_{out}(s) = \frac{V_e(s) + (1 + SCR_3) R_1}{R_1 + R_3 + SCR_1 R_3}$$

$$-V_{out}(s) = \frac{V_e(s) (R_2 + SCR_2 R_3)}{R_1 + R_3 + SCR_1 R_3}$$

dividing the ~~numerator~~ ~~and~~ through by $R_1 + R_3$

$$V_{out}(s) = \frac{V_e(s) (R_2 + SCR_2 R_3)}{R_1 + R_3}$$

$$\frac{R_1 + R_3}{R_1 + R_3} + \frac{SCR_1 R_3}{R_1 + R_3}$$

effective resistance

$$R = \frac{R_1 R_3}{R_1 + R_3}$$

$$-V_{out}(s) = \frac{V_e(s) (R_2 + SCR_2 R_3)}{R_1 + R_3 + 1 + SCR R}$$

if $SCR \ll 1$

$$-V_{out}(s) = \frac{V_e(s) (R_2 + SCR_2 R_3)}{R_1 + R_3}$$

but from inverting (current)

$$V_{out} = -V_{out} + V_e$$

$$-(-V_{out}(s) + V_e) = \frac{V_e (R_2 + SCR_2 R_3)}{R_1 + R_3}$$

$$-(V_i - V_{out}(s) + V_o) = \frac{V_e (R_2 + sCR_2R_1)}{R_1 + R_3}$$

$$V_{out}(s) - V_o = \frac{V_e(s) R_2}{R_1 + R_3} + \frac{sCR_2R_1 V_e(s)}{R_1 + R_3}$$

$$V_{out}(s) = \frac{R_2}{R_1 + R_3} V_e(s) + \frac{R_2 R_3 C s V_e(s)}{R_1 + R_3} + V_o$$

taking the inverse Laplace transform

$$V_{out} = \frac{R_2}{R_1 + R_3} V_e + \frac{R_2 R_3 C}{R_1 + R_3} \frac{dV_e}{dt} + V_o$$

$$V_{out} = G_p V_e + G_D \frac{dV_e}{dt} + V_o$$

where $G_p = \frac{R_2}{R_1 + R_3}$ --- proportional gain

$G_D = R_3 C$ --- derivative gain