

ABBAY FLOURISH OBARI-AKASE

16/ENG04/001

ELECT/ELECT

EEE 561

### Assignment


Derive the analysis for the output voltage in using operational Amplifier for:

1. Proportional **I**ntegral Controller mode
2. Proportional Derivative Controller mode.

### Solution

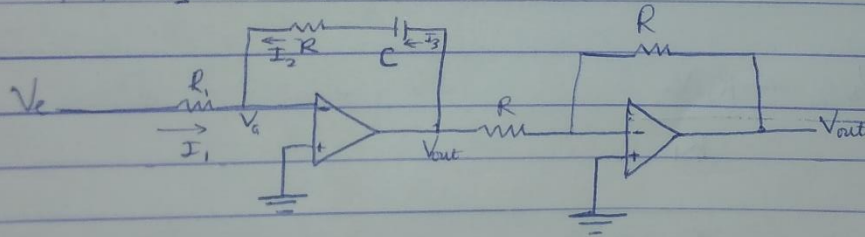1. Proportional-Integral mode [PI]

$$P = K_p e_p + K_p K_i \int_0^t e_p dt + P_i(\omega)$$



$$V_a = 0$$

$$I_1 + I_2 = 0$$

$$I_3 - I_2 = 0$$

$$I_c = C \frac{dv}{dt}$$

$$I_1 = \frac{V_e}{R_1}$$

$$I_2 = \frac{V_b}{R_2}$$

$$\Rightarrow I_1 + I_2 = 0$$

$$\frac{V_e}{R_1} + \frac{V_b}{R_2} = 0 \quad \dots \dots \dots \textcircled{1}$$

$$\Rightarrow I_3 + I_2 = 0$$

$$\Rightarrow I_3 = C \frac{d[V_{out} - V_b]}{dt} - \frac{V_b}{R_2} = 0 \quad \dots \dots \dots \textcircled{2}$$

from equation 1

$$\frac{V_e}{R_1} + \frac{V_b}{R_2} = 0$$

$$V_b = - \frac{R_2 V_e}{R_1} \quad \dots \dots \dots \textcircled{3}$$

Method 1:

Taking Laplace transform of equation 2

$$sC[V_{out}(s) - V_b(s)] - \frac{V_b(s)}{R} = 0$$

$$sC V_{out}(s) = sC V_b(s) + \frac{V_b(s)}{R_2}$$

$$sC V_{out}(s) = V_b(s) \left( sC + \frac{1}{R_2} \right)$$

Equation 3

$$V_b = -\frac{R_2}{R_1} V_e$$

$$\therefore sC V_{out}(s) = -\frac{R_2}{R_1} V_e(s) \left( sC + \frac{1}{R_2} \right)$$

$$\therefore V_{out}(s) = -\frac{R_2}{sCR_1} V_e(s) \left( sC + \frac{1}{R_2} \right)$$

$$V_{out}(s) = -\frac{R_2}{R_1} V_e(s) - \frac{R_2}{R_1} \frac{1}{sCR_2} V_e(s)$$

from the inverting circuit.

$$V_{out} = -V_{in}$$

$$\therefore V_{out}(s) = - \left[ -\frac{R_2}{R_1} V_e(s) - \frac{R_2}{R_1} \frac{1}{sCR_2} V_e(s) \right]$$

$$V_{out}(s) = \frac{R_2}{R_1} V_e(s) + \frac{R_2}{R_1} \frac{1}{sCR_2} V_e(s)$$

Making inverse laplace

$$V_{out} = \frac{R_2}{R_1} V_{cos} + \frac{R_2}{R_1} \frac{1}{R_2} \int_0^t V_{cos} dt + V_0$$

or

$$V_{out} = C_p V_e + C_p R_2 \int_0^t V_e dt + V_{cos}$$

where

$$C_p = \frac{R_2}{R_1}$$

$$C_I = \frac{1}{R_2 C}$$

method 2:

Substituting equation 3 into 2

$$C \frac{d}{dt} \left[ V_{out} + \frac{R_2 V_e}{R_1} \right] + \frac{R_2 V_e}{R_1 R_2}$$

$$C \frac{dV_{out}}{dt} + \frac{R_2}{R_1} C \frac{dV_e}{dt} + \frac{V_e}{R_1} = 0$$

Dividing through by C

$$\frac{dV_{out}}{dt} + \frac{R_2}{R_1} \frac{dV_e}{dt} + \frac{V_e}{R_1 C} = 0 \quad \text{--- (4)}$$

Integrating equation f with respect to dt

$$\int_0^{V_{out}} \frac{dV_{out}}{dt} dt + \frac{R_2}{R_1} \int_0^{V_e} \frac{dV_e}{dt} dt + \frac{1}{R_1 C} \int_0^{V_e} V_e dt = 0$$

$$V_{out} + \frac{R_2}{R_1} V_e + \frac{1}{R_1 C} \int_0^t V_e dt + V_{(0)} = 0$$

$$\frac{R_2}{R_1} V_e + \frac{1}{R_1 C} \int_0^t V_e dt + V_{(0)} = -V_{out}$$

from the inverting circuit;

$$V_{out} = -V_{out}$$

$$\Rightarrow V_{out} = \frac{R_2}{R_1} V_e + \frac{1}{R_1 C} \int_0^t V_e dt + V_{(0)}$$

multiplying through by  $R_2/R_2$

$$\frac{R_2}{R_2} V_{out} = \frac{R_2}{R_2} \cdot \frac{R_2}{R_1} V_e + \frac{R_2}{R_2} \cdot \frac{1}{R_1 C} \int_0^t V_e dt + V_{(0)}$$

$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1} * \frac{1}{R_2 C} \int_0^t V_e dt + V_{(0)}$$

OR

$$V_{out} = G_p V_e + G_I G_I \int_0^t V_e dt + V_{(0)}$$


where;

$$G_p = \frac{R_2}{R_1} \longrightarrow \text{Proportional gain}$$

$$G_I = \frac{1}{R_2 C} \longrightarrow \text{Integral gain.}$$
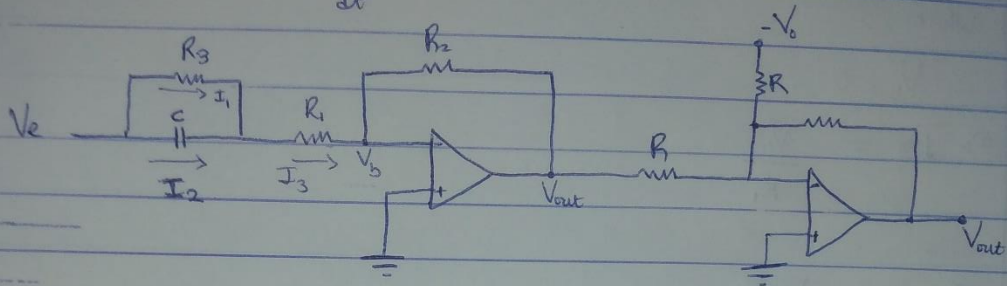
## Proportional-Derivative [PD]

$$P(s) = K_p e_p + K_p K_D \frac{d e_p}{dt} + P(s)$$



Effective resistance  $R$  is given as:

$$R = \frac{R_1 R_3}{R_1 + R_3} \quad \dots \dots \dots *$$

Applying KCL,

$$I_1 + I_2 = I_3$$

$$\Rightarrow I_1 + I_2 - I_3 = 0$$

Also

$$I_1 + I_3 = 0$$

from the circuit;

$$I_1 = \frac{V_e - V_a}{R_3}$$

$$I_2 = \frac{cd [V_e - V_a]}{dt}$$

$$I_3 = \frac{V_a - V_b}{R_1}$$

where

$$V_b = 0$$

$$\Rightarrow I_3 = \frac{V_a}{R_1}$$

$$I_4 = \frac{V_{out1}}{R_2}$$

Combining with Ohm's law

$$\frac{V_e - V_a}{R_3} + C \frac{d}{dt} [V_e - V_a] - \frac{V_a}{R_1} = 0 \quad \text{--- (1)}$$

$$\frac{V_a}{R_1} + \frac{V_{out1}}{R_2} = 0 \quad \text{--- (2)}$$

from equation (2)

Making  $V_a$  subject of formula.

$$\frac{V_a}{R_1} = - \frac{V_{out1}}{R_2}$$

$$V_a = - \frac{R_1 V_{out1}}{R_2} \quad \text{--- (3)}$$

Taking Laplace transform of equation 1

$$\frac{V_{e(s)} - V_{a(s)}}{R_3} + SC [V_{e(s)} - V_{a(s)}] - \frac{V_{a(s)}}{R_1} = 0$$

$$\frac{V_{e(s)}}{R_3} - \frac{V_{a(s)}}{R_3} + SC V_{e(s)} - SC V_{a(s)} - \frac{V_{a(s)}}{R_1} = 0$$

$$\frac{V_{e(s)}}{R_3} + SC V_{e(s)} = \frac{V_{a(s)}}{R_3} + SC V_{a(s)} + \frac{V_{a(s)}}{R_1}$$

$$\left[ \frac{1}{R_3} + SC \right] V_{e(s)} = \left[ \frac{1}{R_3} + SC + \frac{1}{R_1} \right] V_{a(s)} \dots \dots \dots \textcircled{4}$$

Substituting eqn 3 into eqn 4

$$\left[ \frac{1}{R_3} + SC \right] V_{e(s)} = \left[ \frac{1}{R_3} + SC + \frac{1}{R_1} \right] \left( - \frac{R_1 V_{out 1}}{R_2} \right)$$

$$\left[ \frac{1 + R_3 SC}{R_3} \right] V_{e(s)} = \left[ \frac{R_1 + R_1 R_3 SC + R_3}{R_1 R_3} \right] \left( - \frac{R_1 V_{out 1}}{R_2} \right)$$

$$\left[ 1 + R_3 SC \right] V_{e(s)} = \frac{-V_{out 1}}{R_2} \left[ R_1 + R_1 R_3 SC + R_3 \right]$$

making  $-V_{out 1}(s)$  subject of formula.

$$\left[ R_2 + R_2 R_3 SC \right] V_{e(s)} = -V_{out 1}(s) \left[ R_1 + R_1 R_3 SC + R_3 \right]$$

$$-V_{out 1}(s) = \frac{\left[ R_2 + R_2 R_3 SC \right] V_{e(s)}}{\left[ R_1 + R_1 R_3 SC + R_3 \right]}$$



$$-V_{out1}(s) = \frac{V_{in}(s) [R_2 + R_2 R_3 s C]}{[R_1 + R_1 R_3 s C + R_3] / R_1 + R_3}$$

$$-V_{out1} = \frac{V_{in}(s) [R_2 + R_2 R_3 s C] / R_1 + R_3}{\frac{R_1 + R_3}{R_1 + R_3} + \frac{R_1 R_3 s C}{R_1 + R_3}}$$

$$-V_{out1} = \frac{V_{in}(s) [R_2 + R_2 R_3 s C] / R_1 + R_3}{1 + \frac{R_1 R_3 s C}{R_1 + R_3}}$$

from eqn \*

$$R = \frac{R_1 R_3}{R_1 + R_3}$$

$$\Rightarrow -V_{out1} = \frac{V_{in}(s) [R_2 + R_2 R_3 s C] / R_1 + R_3}{1 + R s C}$$

If  $1 \gg R s C$

then

$$-V_{out} = \frac{V_{in}(s) [R_2 + R_2 R_3 s C] / R_1 + R_3}{1} = \frac{V_{in}(s) (R_2 + R_2 R_3 s C)}{R_1 + R_3}$$

from the inverting circuit.

$$V_{out1} = -V_{out} + V_0$$

$$\Rightarrow V_{out}(s) = \frac{V_e(s) (R_2 + R_2 R_3 s C)}{R_1 + R_3} + V_0$$

$$V_{out}(s) = \frac{R_2 V_e(s)}{R_1 + R_3} + \frac{R_2 R_3 s C}{R_1 + R_3} V_e(s) + V_0$$

$$V_{out}(s) = \frac{R_2}{R_1 + R_3} V_e + \frac{R_2}{R_1 + R_3} R_3 s C V_e + V_0$$

Taking inverse laplace

$$V_{out} = \left[ \frac{R_2}{R_1 + R_3} \right] V_e + \left[ \frac{R_2}{R_1 + R_3} \right] R_3 C \frac{dV_e}{dt} + V_0$$

or

$$V_{out} = G_p V_e + G_D G_D \frac{dV_e}{dt} + V_0$$

where

$$G_p = \left[ \frac{R_2}{R_1 + R_3} \right] \text{----- Proportional gain}$$

$$G_D = \left[ R_3 C \right] \text{----- Derivative gain.}$$