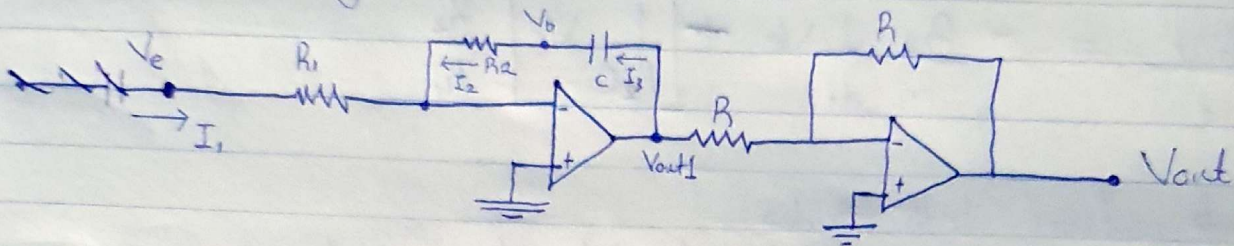


Egh Ochiabo Emmanuel  
 161ENG01017  
 Mechatronics Engr  
 MCT 511 - Process Automation

Assignment.

1) Proportional Integral Controller Mode



$$I_1 + I_2 = 0$$

$$I_3 - I_2 = 0$$

$$I_c = C \frac{dV_c}{dt}$$

Combining this with ohm's law

$$\frac{V_e}{R_1} + \frac{V_b}{R_2} = 0 \quad \text{--- (i)}$$

$$C \frac{d[V_{out1} - V_b]}{dt} - \frac{V_b}{R_2} = 0 \quad \text{--- (ii)}$$

From (i)

$$V_b = - \frac{R_2}{R_1} V_e \quad \text{--- (iii)}$$

Substituting (iii) into (ii)

$$C \frac{dV_{out1}}{dt} - C \frac{d}{dt} \left[ - \frac{R_2}{R_1} V_e \right] - \frac{1}{R_2} \left[ - \frac{R_2}{R_1} V_e \right] = 0$$

$$C \frac{dV_{out}}{dt} + C \frac{R_2}{R_1} \frac{dV_e}{dt} + \frac{R_2}{R_1} \left[ \frac{1}{R_2 C} V_e \right] = 0$$

Multiplying all through by  $1/C$

$$\frac{dV_{out}}{dt} + \frac{R_2}{R_1} \frac{dV_e}{dt} + \frac{R_2}{R_1} \left[ \frac{1}{R_2 C} V_e \right] = 0$$

$$\frac{dV_{out}}{dt} = - \frac{R_2}{R_1} \frac{dV_e}{dt} + \left[ \frac{1}{R_2 C} V_e \right] \frac{R_2}{R_1}$$

Integrating both sides

$$V_{out} = - \frac{R_2}{R_1} V_e - \frac{R_2}{R_1} \int_0^t \frac{1}{R_2 C} V_e dt + V(0)$$

After Inverting

$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1 R_2 C} \int_0^t V_e dt + V(0)$$


$$\therefore V_{out} = G_P V_e + G_I G_I \int_0^t V_e dt + V(0)$$

Where

$$G_P = \frac{R_2}{R_1} \quad \text{Proportional Gain}$$

$$G_I = \frac{1}{R_2 C} \quad \text{Integral Gain}$$
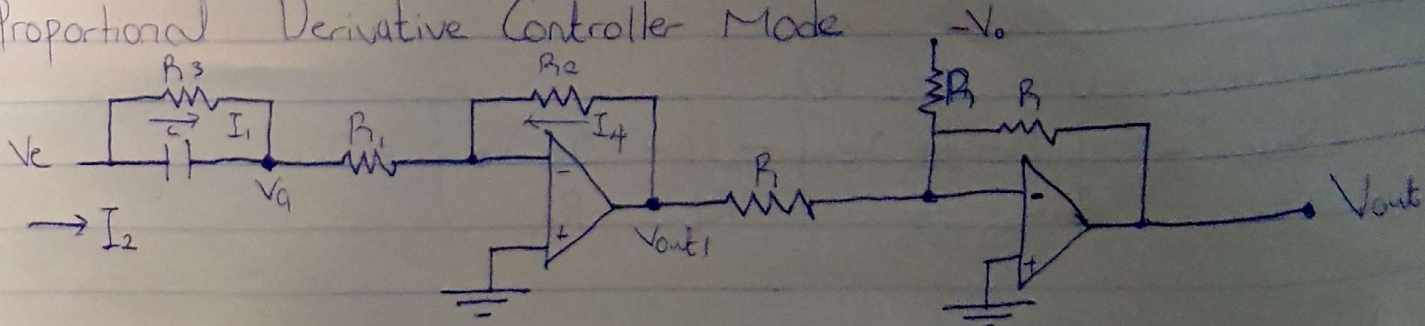
## 2 Proportional Derivative Controller Mode



By KCL

$$I_1 + I_2 - I_3 = 0$$

$$I_4 + I_3 = 0$$

Combining with Ohm's Law

$$\frac{V_e - V_a}{R_3} + C \frac{d[V_e - V_a]}{dt} - \frac{V_a}{R_1} = 0 \quad \text{--- (a)}$$

$$\frac{V_{out}}{R_2} + \frac{V_a}{R_1} = 0 \quad \text{--- (b)}$$

~~From~~ From eqn (b)

$$V_a = - \frac{R_1}{R_2} V_{out} \quad \text{--- (c)}$$

Substituting (c) into (a)

$$\frac{V_e}{R_3} - \frac{1}{R_3} \left[ - \frac{R_1}{R_2} V_{out} \right] + C \frac{dV_e}{dt} - C \frac{d}{dt} \left[ - \frac{R_1}{R_2} V_{out} \right] - \left[ - \frac{R_1}{R_2} V_{out} \right] \frac{1}{R_1} = 0$$

$$\frac{V_e}{R_3} + \frac{R_1}{R_2 R_3} V_{out} + C \frac{dV_e}{dt} + \frac{R_1 C}{R_2} \frac{dV_{out}}{dt} + \frac{1}{R_2} V_{out} = 0$$

Multiplying through by  $R_3$

$$V_e + \frac{R_1}{R_2} V_{out} + R_3 C \frac{dV_e}{dt} + \frac{R_1 R_3 C}{R_2} \frac{dV_{out}}{dt} + \frac{R_3}{R_2} V_{out} = 0$$

$$\frac{R_1}{R_2} V_{out} + \frac{R_1 R_3 C}{R_2} \frac{dV_{out}}{dt} + \frac{R_3}{R_2} V_{out} = -V_e - R_3 C \frac{dV_e}{dt}$$

$$\left[ \frac{R_1 + R_3}{R_2} \right] V_{out} + \frac{R_1 R_3 C}{R_2} \frac{dV_{out}}{dt} = -V_e - R_3 C \frac{dV_e}{dt}$$

Multiply althrough by  $\left[ \frac{R_2}{R_1 + R_3} \right]$

$$V_{out} + \left[ \frac{R_1}{R_1 + R_3} \right] R_3 C \frac{dV_{out}}{dt} = - \left[ \frac{R_2}{R_1 + R_3} \right] V_e - \left[ \frac{R_2}{R_1 + R_3} \right] R_3 C \frac{dV_e}{dt}$$

After Inverting

$$V_{out} + \left[ \frac{R_1}{R_1 + R_3} \right] R_3 C \frac{dV_{out}}{dt} = \left[ \frac{R_2}{R_1 + R_3} \right] V_e + \left[ \frac{R_2}{R_1 + R_3} \right] R_3 C \frac{dV_e}{dt}$$

$$\therefore V_{out} = \left[ \frac{R_2}{R_1 + R_3} \right] V_e + \left[ \frac{R_2}{R_1 + R_3} \right] R_3 C \frac{dV_e}{dt} + V(0)$$

OR

$$V_{out} = G_p V_e + G_p G_D \frac{dV_e}{dt} + V(0)$$

where

$$G_p = \frac{R_2}{R_1 + R_3} \quad - \text{Proportional Gain}$$

$$G_D = R_3 C \quad - \text{Derivative Gain.}$$