

16/ENG04/019

Daniel

NAME: FASHINA, Oluwadamilola Temiloluwa

MATRIC NO. 16/ENG04/019

DEPT: Electrical/ Electronics

Question


Derive the analysis for the output voltage in using operational Amplifier:

- (a) Proportional Integral controller mode
- (b) Proportional Derivative controller mode

Solution

For Proportional Integral Controller mode
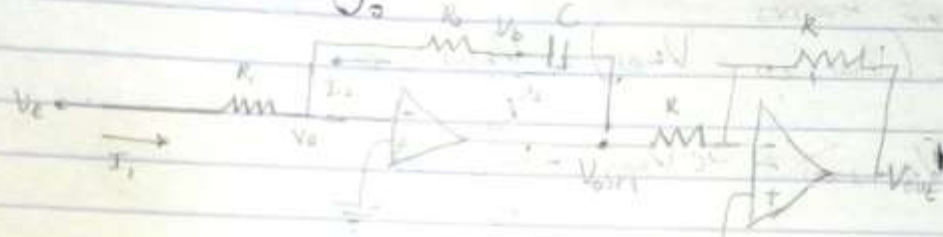
$$P = K_p E_p + K_p K_I \int^t E_p dt + P I(0)$$



NB There is no current through the op-amp input terminals, and no voltage across the input terminals

$$V_a = 0$$

$$I_1 + I_2 = 0$$

$$I_3 - I_2 = 0$$

The relationship between the voltage across the capacitor and the current through a capacitor:

$$I_c = C \frac{dV_c}{dt}$$

$$\text{since } I_1 = \frac{V_e - V_a}{R_1} = \frac{V_e - 0}{R_1} = \frac{V_e}{R_1}$$

$$I_1 = \frac{V_e}{R_1}$$

$$I_2 = \frac{V_b - V_3}{R_2} = \frac{V_b - 0}{R_2} = \frac{V_b}{R_2} \quad \left| \quad I_3 = \frac{C \cdot d}{dt} (V_{out} - V_b) \right.$$

Considering ohm law

$$\frac{V_b}{R_1} + \frac{V_b}{R_2} = 0 \quad \dots \times$$

$$C \frac{d}{dt} (V_{out} - V_b) - \frac{V_b}{R_2} = 0 \quad \dots \times \times$$

$$\rightarrow \frac{V_b}{R_2} = -\frac{V_e}{R_1}$$

making V_b subject of formula

$$V_b = -\frac{R_2}{R_1} V_e \quad \dots \times \times \times$$

making use of laplace transform in s-domain
equation becomes

$$sC (V_{out}(s) - V_b(s)) - \frac{V_b(s)}{R_2} = 0$$

$$sC V_{out}(s) - sC V_b(s) - \frac{V_b(s)}{R_2} = 0$$

$$sC V_{out}(s) = sC V_b(s) + \frac{V_b(s)}{R_2}$$

$$sC V_{out}(s) = V_b(s) \left(sC + \frac{1}{R_2} \right) \quad \dots \times \times \times$$

Substitute from equation into equation in s-domain

$$sC V_{out}(s) = \frac{-R_2}{R_1} V_e(s) \left(sC + \frac{1}{R_2} \right)$$

$$V_{out}(s) = \frac{-R_2}{sCR_1} V_e(s) \left(sC + \frac{1}{R_2} \right)$$

$$V_{out}(s) = -\frac{R_2}{R_1} V_e(s) - \frac{R_2}{R_1} \frac{1}{sCR_2} V_e(s)$$

From the inverting circuit in the op-amp

$$V_{out1} = -V_{out}$$

$$\therefore V_{out}(s) = - \left(- \frac{R_2}{R_1} \frac{V(s)}{s} - \frac{R_2}{R_1} \frac{1}{sCR_2} V(s) \right)$$

$$V_{out}(s) = \frac{R_2}{R_1} V(s) + \frac{R_2}{R_1} \frac{1}{sCR_2} V(s) \quad \dots \times \times \times \times$$

Substituting $\times \times \times \times$ using inverse Laplace transform

$$V_{out} = \frac{R_2}{R_1} V(s) + \frac{R_2}{R_1} \frac{1}{R_2} \int_0^t V(s) dt + V(s)$$

$$V_{out} = \frac{R_2}{R_1} V(s) + \frac{R_2}{R_1} \frac{1}{R_2} \int_0^t V(s) dt + V(s)$$

Inverse Laplace transform s^{-1} can be expressed as $\int_0^t dt + c$

$$s^{-1} = \int_0^t dt + c \quad \dots \times \times \times \times$$

$$\therefore V_{out} = G_p V_e + G_p G_I \int_0^t V_e dt + V(s)$$


$$\text{where } G_p = \frac{R_2}{R_1}$$

$$G_I = \frac{1}{R_2 C}$$

$$\therefore V_{out} = G_p V_e + G_p G_I \int_0^t V_e dt + V(s)$$

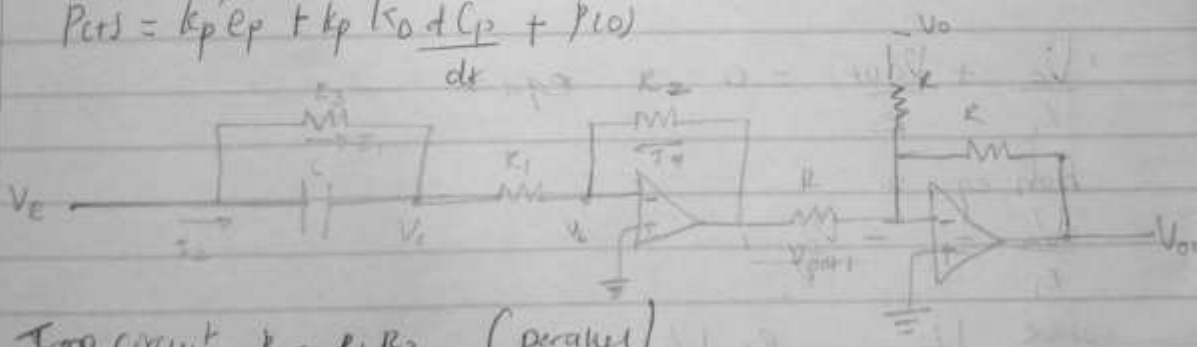(2) For the Proportional Derivative Controller Mode.

$$P(s) = k_p e_p + k_p k_D \frac{d(e_p)}{dt} + P(s)$$



$$\text{From circuit } k = \frac{R_1 R_2}{R_1 + R_3} \quad (\text{parallel})$$

where R_3 is the effective resistance

$$\sum I_{in} = I_c = 0$$

Using KCL - AD control

$$I_1 + I_2 - I_3 = 0$$

$$I_1 + I_2 = I_3$$

$$I_4 + I_3 = 0 \quad / \quad I_3 + I_4 = 0$$

$$\text{where } I_1 = \frac{V_c - V_a}{R_3}$$

$$I_2 = \frac{d}{dt} (V_c - V_a)$$

$$I_3 = \frac{V_a - V_b}{R_1} = \frac{V_a - 0}{R_1} = \frac{V_a}{R_1} \quad (V_b = 0)$$

$$I_4 = \frac{V_{out1} - V_b}{R_2} \quad (V_b = 0)$$

$$I_4 = \frac{V_{out1}}{R_2} - 0 = \frac{V_{out1}}{R_2}$$

Combining ohms law

$$\frac{V_c - V_a}{R_3} + \frac{d}{dt} (V_c - V_a) - \frac{V_a}{R_1} = 0$$

$$\frac{V_c - V_a}{R_3} + \frac{d}{dt} (V_c - V_a) - \frac{V_a}{R_1} \dots \text{equ 1}$$

$$\frac{V_a}{R_1} + \frac{V_{out1}}{R_2} = 0 \dots \text{equ 2}$$

From equ 2

$$\frac{V_a}{R_1} = -\frac{V_{out1}}{R_2}$$

$$\text{where } V_a = -\frac{R_1}{R_2} V_{out1} \dots \text{equ 3}$$

$$\frac{V_c - V_o}{R_3} + C \frac{d(V_c - V_o)}{dt} - \frac{V_o}{R_1} = 0$$

To Replacing with Laplace

$$\frac{V_c(s) - V_o(s)}{R_3} + sC (V_c(s) - V_o(s)) - \frac{V_o(s)}{R_1} = 0$$

~~rearranging~~ rearranging equations

$$\frac{V_c(s)}{R_3} + sC V_c(s) = \frac{V_o(s)}{R_1} + \frac{V_o(s)}{R_3} + sC V_o(s)$$

Replacing V_o in equ 3.

$$V_c(s) \left(\frac{1}{R_3} + sC \right) = V_o(s) \left(\frac{1}{R_1} + \frac{1}{R_3} + sC \right)$$

$$V_c(s) \left(\frac{1 + R_3 sC}{R_3} \right) = - \frac{R_1}{R_2} V_{out}(s) \left(\frac{R_2 + R_1 + sC R_1 R_2}{R_1 R_2} \right)$$

$$V_c(s) (1 + sC R_3) = - \frac{R_1}{R_2} V_{out}(s) \left(\frac{R_2 + R_1 + sC R_1 R_2}{R_1 R_2} \right)$$

$$V_c(s) (1 + sC R_3) = - \frac{V_{out}(s)}{R_2} (R_2 + R_1 + sC R_1 R_2)$$

$$- V_{out}(s) = \frac{V_c(s) (1 + sC R_3) R_2}{(R_1 + R_2 + sC R_1 R_2)}$$

$$- V_{out}(s) = \frac{V_c(s) (R_2 + sC R_2 R_3)}{(R_1 + R_2 + sC R_1 R_2)}$$

Divide all through by $R_1 + R_2$

$$- V_{out}(s) = V_c(s) \frac{(R_2 + sC R_2 R_3) / (R_1 + R_2)}{\frac{R_1 + R_2}{R_1 + R_2} + \frac{sC R_1 R_2}{R_1 R_2}}$$

Parallel circuit $\cdot R = R_1 R_2$

Replacing

$$-V_{out}(s) = \frac{V_{in}(s) (R_2 + sCR_2R_3)}{R_1 + R_3}$$

where $sCR_2R_3 \ll 1$

$$-V_{out}(s) = \frac{V_{in}(s) (R_2 + sCR_2R_3)}{R_1 + R_3}$$

Applying the inverting circuit from the OP-amp
 $V_{out} = -V_{out} + V_0$

$$-(-V_{out}(s) + V_0) = \frac{V_{in}(s) (R_2 + sCR_2R_3)}{R_1 + R_3}$$

$$V_{out}(s) - V_0 = \frac{V_{in}(s) R_2}{R_1 + R_3} + \frac{sCR_2R_3}{R_1 + R_3} V_{in}(s)$$

$$V_{out}(s) = \frac{R_2}{R_1 + R_3} V_{in}(s) + \frac{R_2}{R_1 + R_3} R_3 sC (V_{in}(s) + V_0)$$

Applying inverse Laplace transform

$$V_{out}(t) = \frac{R_2}{R_1 + R_3} V_{in} + \frac{R_2}{R_1 + R_3} R_3 \left(\frac{dV_{in}}{dt} + V_0 \right)$$

$$V_{out}(t) = G_p V_{in} + G_p G_0 \frac{dV_{in}}{dt} + V_0$$

$$V_{out}(t) = G_p V_{in} + G_p G_0 \frac{dV_{in}}{dt} + V_0$$

recall

$$\therefore G_p = \frac{R_2}{R_1 + R_3}$$

$$G_0 = R_3 C$$