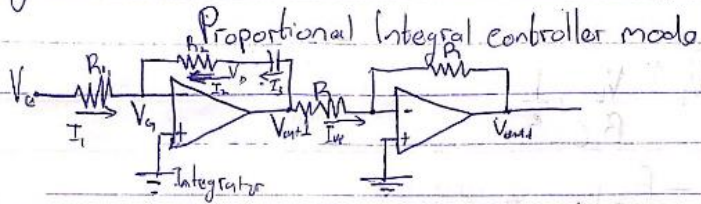


Adegoke Fiyidade
16/ENR04/004

Assignment Solution



$$V_{out} = -\frac{R_2}{R_1} (V_{out}) = -V_{out} \left[\text{Inverting circuit} \right]$$

$$V_a = 0$$

Applying KCL to the Integrator OP amp

$$I_1 + I_2 = 0 \quad \text{--- (1)}$$

$$I_3 - I_2 = 0 \quad \text{--- (2)}$$

$$\text{Note: } I_2 = I_c = C \frac{dV_c}{dt} = C \frac{d(V_{out} - V_a)}{dt} \quad \text{--- (3)}$$

Applying ohm's law to equation (1) and (2).

$$\frac{V_a}{R_1} + \frac{V_a}{R_2} = 0 \quad \text{--- (4)}$$

$$\therefore V_b = -\frac{R_2}{R_1} V_a \quad \text{--- (5)}$$

$$\frac{C \frac{d(V_{out} - V_a)}{dt} - \frac{V_b}{R_2} = 0 \quad \text{--- (6)}$$

By expansion, eqn(6)

$$C \frac{dV_{out}}{dt} - C \frac{dV_a}{dt} - \frac{V_b}{R_2} = 0$$

divide through by C

$$\frac{dV_{out}}{dt} - \frac{dV_a}{dt} - \frac{V_b}{R_2 C} = 0 \quad \text{--- (7)}$$

Take the Laplace of eqn(7)

$$S V_{out} - S V_a - \frac{V_b}{R_2 C} = 0$$

$$V_{out} = V_b + \frac{V_b}{R_2 C s}$$

$$V_b = -\frac{R_2}{R_1} V_o, \text{ eqn (1) below}$$

~~$$V_{out} = -\frac{R_2}{R_1} V_o + \frac{-\frac{R_2}{R_1} V_o}{R_2 C s}$$~~

$$V_{out} = -\frac{R_2}{R_1} V_o - \frac{R_2}{R_1} \frac{1}{R_2 C s} V_o$$

~~$$\text{By substituting } V_b = -\frac{R_2}{R_1} V_o \text{ Also, } V_{out} = -V_{out}$$~~

$$\therefore -V_{out} = -\frac{R_2}{R_1} V_o - \frac{R_2}{R_1} \frac{1}{R_2 C s} V_o$$

$$V_{out} = \frac{R_2}{R_1} V_o + \frac{R_2}{R_1} \frac{1}{R_2 C s} V_o$$

Taking inverse Laplace transform

$$\frac{1}{s} = \int dt + k, \quad k = \text{Integration constant}$$

Also, applying the integrator circuit analysis principle:

$$V_{out} = \frac{R_2}{R_1} V_o + \frac{R_2}{R_1} \frac{1}{R_2 C} \int V_o dt + V_{out}(0)$$


$$V_{out} = G_p V_o + G_I \int V_o dt + V_{out}(0)$$

$V_{out}(0) =$ Output Voltage with no error Voltage

$$G_p = \frac{R_2}{R_1} \quad \left[\text{Proportional gain} \right]$$

$$G_I = \frac{1}{R_2 C} \quad \left[\text{Integral gain} \right]$$

Proportional Derivative Controller Mode

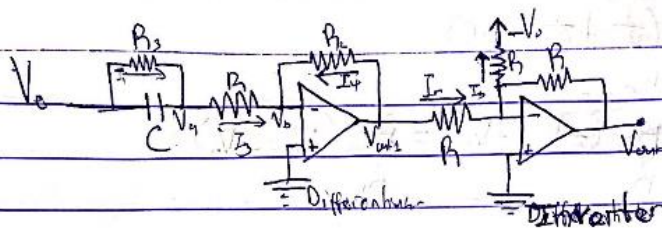

$$R = \frac{R_1 R_3}{R_1 + R_3}$$

R is effective resistance

Then, the condition becomes as usual: $2\pi f_m RC = 0.1$

By KCL

$$I_1 + I_2 - I_3 = 0 \quad \dots (1)$$

$$I_4 + I_3 = 0 \quad \dots (2)$$

Combining with ohm's law

$$\frac{V_0 - V_1}{R_2} + C \frac{d(V_0 - V_1)}{dt} - \frac{V_1}{R_1} = 0 \quad \dots (3)$$

$$\frac{V_{out1}}{R_2} + \frac{V_1}{R_1} = 0 \quad \dots (4)$$

$$V_1 = -\frac{R_1}{R_2} V_{out1} \quad \dots (5)$$

$$\text{Also: } I_5 + I_7 - I_6 = 0 \quad \dots (6)$$

$$\frac{V_{out1}}{R} + \frac{V_{out}}{R} - \frac{V_0}{R} = 0 \quad \dots (7)$$

$$\therefore V_{out} = -V_{out1} + V_0 \quad \dots (8)$$

By expanding eqn (3), because:

$$\frac{V_0}{R_2} + C \frac{dV_0}{dt} = \frac{V_1}{R_2} + \frac{V_1}{R_1} + C \frac{dV_1}{dt}$$

$$V_o \left(\frac{1}{R_3} + sC \right) = V_o \left(\frac{1}{R_3} + \frac{1}{R_1} + sC \right)$$

By substitution

$$V_o = -\frac{R_1}{R_2} V_{in} = -\frac{R_2}{R_2} (-V_{out} + V_o) = \frac{R_1}{R_2} (V_{out} - V_o)$$

again below:

$$\left(\frac{R_1}{R_2} \right) (V_{out} - V_o) \left(\frac{1}{R_3} + \frac{1}{R_1} + sC \right) = V_o \frac{(1 + R_3 sC)}{R_3}$$

$$\left(\frac{R_1}{R_2} \right) (V_{out} - V_o) \frac{(R_1 + R_3 + R_1 R_3 sC)}{R_3 R_1} = V_o \frac{(1 + R_3 sC)}{R_3}$$

$$V_{out} - V_o = \frac{V_o (1 + R_3 sC) \times R_2}{R_1 + R_3 + R_1 R_3 sC}$$

Divide both numerator/denominator by $R_1 + R_3$

$$V_{out} - V_o = V_o \frac{\left(\frac{1}{R_1 + R_3} + \frac{R_3 sC}{R_1 + R_3} \right) R_2}{1 + \frac{R_1 R_3 sC}{R_1 + R_3}}$$

$$V_{out} - V_o = \frac{\left(\frac{R_2}{R_1 + R_3} + \frac{R_1 R_3 sC}{R_1 + R_3} \right) V_o}{1 + R_3 sC}$$

If $R_3 sC \ll 1$

$$V_{out} - V_o = \frac{R_2}{R_1 + R_3} V_o + \frac{R_2}{R_1 + R_3} R_3 sC V_o$$

By taking inverse Laplace transform

$$sV_o = \frac{dV_o}{dt}, \quad V_{out} = \frac{R_2}{R_1 + R_3} V_o + \frac{R_2}{R_1 + R_3} R_3 C \frac{dV_o}{dt} + V_o$$

$$V_{out} = G_p V_o + G_D \frac{dV_o}{dt} + V_o$$

$$G_p = \frac{R_2}{R_1 + R_3} \rightarrow \text{Proportional gain}$$

$$G_D = R_3 C \rightarrow \text{Derivative gain}$$