

Name: Sanni Oluwatobiloba


Matric: 161EN0051030

Course Code: MCT 511

Course Title: Process Control & Automation

Department: Mechatronics

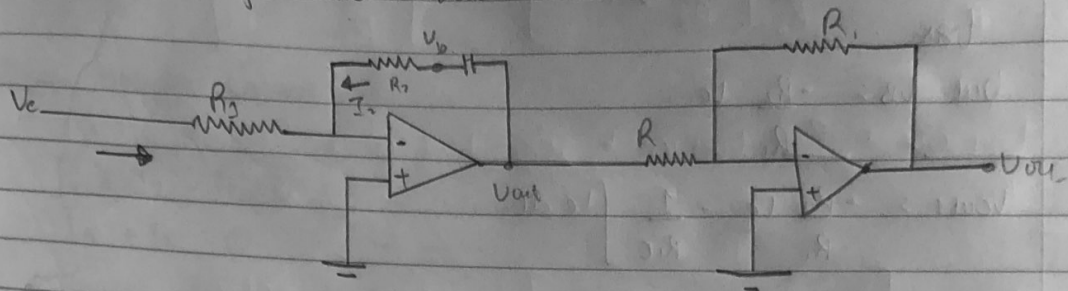i7. Proportional - Integral mode Controller.



Using Kirchhoff's Current Law:

$$V_a = 0$$

$$I_1 + I_2 = 0 \quad \text{--- (i)}$$

$$I_3 - I_2 = 0 \quad \text{--- (ii)}$$

where: [Ohm's Law]

$$I_1 = \frac{V_e}{R_1}$$

$$I_2 = \frac{V_o}{R_2}$$

$$I_3 = C \frac{dV_e}{dt}$$

∴ from equ (i)

$$\frac{V_e}{R_1} + \frac{V_o}{R_2} = 0$$

∴ from equ (ii)

$$C \frac{d[V_{out} - V_B]}{dt} = \frac{V_o}{R_2}$$

Combining equation (i) and (ii) [i.e. equ (i) + equ (ii)]

$$\frac{V_e}{R_1} + C \frac{d[V_{out} - V_B]}{dt} = 0$$

$$C \frac{d[V_{out} - V_B]}{dt} = -\frac{V_e}{R_1}$$

Integrating both sides.

$$C [V_{out} - V_B] = -\frac{1}{R_1} \int V_e dt$$

$$V_{out} = V_B - \frac{1}{R_1 C} \int V_e dt$$

but

$$V_B = -\frac{R_2}{R_1} V_e$$

$$V_{out} = -\frac{R_2}{R_1} V_e - \frac{1}{R_1 C} \int V_e dt$$

$$V_{out} = -\frac{R_2}{R_1} V_e - \frac{R_2}{R_1} \cdot \frac{1}{R_2 C} \int V_e dt$$

$$\text{i.e. } \frac{R_2}{R_2} = 1$$

After inverting

$$-V_{out} = V_{out}$$

$$-V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1} \cdot \frac{1}{R_2 C} \int V_e dt \quad \text{[i.e. multiply both sides]}$$

becomes

$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1} \cdot \frac{1}{R_2 C} \int V_e dt + V(0)$$

Considering initial conditions.

Or.


$$V_{out} = G_p V_e + G_p G_I \int V_e dt + V(0)$$

where

$$G_p = \frac{R_2}{R_1}$$

$$G_I = \frac{1}{R_2 C}$$
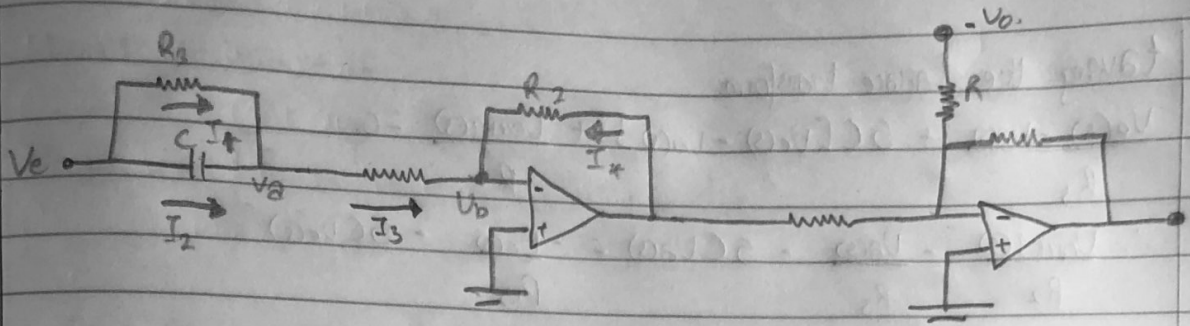
$$G_I = \frac{1}{R_2 C} \quad \text{— Integral gain.}$$



Considering  $2\lambda \text{ fmax } RC = 0$ .

Using Kirchoff's Current law.

$$I_1 + I_2 - I_3 = 0 \quad \text{--- (i)}$$

$$I_x + I_3 = 0 \quad \text{--- (ii)}$$

$$R = \frac{R_1 R_3}{R_1 + R_3}$$

Where  $R$  is the effective resistance.

As per Ohm's law:

$$I_1 = \frac{V_e - V_a}{R_3}$$

$$I_2 = C \frac{d[V_e - V_a]}{dt}$$

$$I_3 = \frac{V_a}{R_1}$$

$$I_x = \frac{V_{out1}}{R_2}$$

∴ from equ (i).

$$\frac{V_e - V_a}{R_3} + C \frac{d[V_e - V_a]}{dt} - \frac{V_a}{R_1} = 0$$

from equ (ii)

$$\frac{V_{out1}}{R_2} + \frac{V_a}{R_1} = 0$$

Add Summing equ (i) and equ (ii)

$$\frac{V_e - V_a}{R_3} + C \frac{d[V_e - V_a]}{dt} + \frac{V_{out1}}{R_2} = 0$$

taking the Laplace transform.

$$\frac{V_o(s) - V_{oc}(s)}{R_3} + S C [V_o(s) - V_{oc}(s)] + \frac{V_{out}(s)}{R_2} = 0.$$

$$\therefore \frac{V_{out}(s)}{R_2} - \frac{V_{oc}(s)}{R_3} - S C V_{oc}(s) = -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s)$$

Expressing  $V_{oc}(s)$  in terms of  $V_{out}$ .

$$\frac{V_{out}(s)}{R_2} = \frac{1}{R_3} \left[ -\frac{R_1}{R_2} V_{out}(s) \right] - S C \left[ -\frac{R_1}{R_2} V_{out}(s) \right] = -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s)$$

$$\frac{V_{out}(s)}{R_2} + \frac{R_1}{R_2 R_3} V_{out}(s) + \frac{S C R_1}{R_2} V_{out}(s) = -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s)$$

$$V_{out}(s) \left[ \frac{1}{R_2} + \frac{R_1}{R_2 R_3} + \frac{S C R_1}{R_2} \right] = -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s)$$

$$V_{out}(s) \left[ \frac{R_3 + R_1 R_3 + S C R_1 R_3}{R_2 R_3} \right] = -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s)$$

$$V_{out}(s) = \left[ \frac{R_2 R_3}{R_3 + R_1 R_3 + S C R_1 R_3} \right] \left[ -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s) \right]$$

$$V_{out}(s) = \left[ \frac{R_2 R_3 / R_1 R_3}{R_1 + R_3 / R_1 R_3 + S C R_1 R_3 / R_1 R_3} \right] \left[ -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s) \right]$$

$$V_{out}(s) = \left[ \frac{R_2 R_3}{R_1 + R_3} \right] \left[ -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s) \right]$$

if  $S C R_1 \ll 1$ .

$$V_{out}(s) = \left[ \frac{R_2 R_3}{R_1 + R_3} \right] \left[ -\frac{V_{oc}(s)}{R_3} - S C V_{oc}(s) \right]$$

$$\therefore V_{out}(s) = - \left[ \frac{R_2}{R_1 + R_3} \right] V_{oc}(s) - \left[ \frac{R_2 R_3}{R_1 + R_3} \right] S C V_{oc}(s)$$

taking the inverse Laplace transform.

$$V_{out}(t) = - \left[ \frac{R_2}{R_1 + R_3} \right] v_e - \left[ \frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dv_e}{dt}$$

from the inverting AMP.

$$V_{out}(t) = - (V_{oc} + (-V_o))$$



$$V_{out} + V_0 = -V_{out} + V_0$$

$$V_{out} = - \left[ \frac{R_2}{R_1 + R_3} \right] V_e - \left[ \frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dV_e}{dt}$$

$$\therefore -V_{out} + V_0 = - \left[ \frac{R_2}{R_1 + R_3} \right] V_e - \left[ \frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dV_e}{dt}$$

$$-V_{out} = - \left[ \frac{R_2}{R_1 + R_3} \right] V_e - \left[ \frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dV_e}{dt} - V_0$$

$$V_{out} = \left[ \frac{R_2}{R_1 + R_3} \right] V_e + \left[ \frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dV_e}{dt} + V_0$$

Where

$$G_p = \frac{R_2}{R_1 + R_3} \quad \text{--- Proportional Gain}$$

$$G_D = R_3 C \quad \text{--- Derivative Gain}$$

$$\therefore V_{out} = G_p V_e + G_p G_D \frac{dV_e}{dt} + V_0$$