

## Latihan Basik


161ENG041043 - Electrical Electronics Engineering

EEF561 - Process control & Automation

### Question

Derive the analysis for the output voltage using operational amplifier in proportional integral controller mode

Soln:

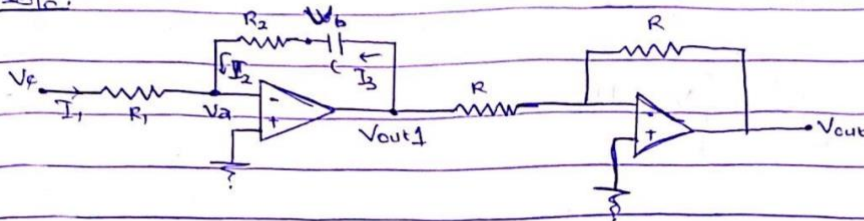

Since no current flows through the op-amp,  $V_a = 0$  (no voltage across its terminals)

$$* \text{KCL } I_3 = I_2 ; I_3 - I_2 = 0$$

$$- I_1 + I_2 = 0$$

$$I_3 - I_2 = 0$$

recall  $I = C \frac{dv}{dt}$  hence  $I_3$  flowing through capacitor  $C =$

$$I_3 = C \frac{d(V_{out1} - V_b)}{dt}$$

$$I_1 = \frac{V_f - V_a}{R_1} = \frac{V_f - 0}{R_1} = \frac{V_f}{R_1}$$

$$I_2 = \frac{V_b - V_a}{R_2} = \frac{V_b - 0}{R_2} = \frac{V_b}{R_2}$$

Substituting the values into KCL equations above.

$$\frac{V_f}{R_1} + \frac{V_b}{R_2} = 0 ; \frac{V_b}{R_2} = -\frac{V_f}{R_1} ; V_b = -\frac{R_2}{R_1} V_f \dots \text{(eqn*)}$$

$$C \frac{d(V_{out1} - V_b)}{dt} - \frac{V_b}{R_2} = 0$$

recall  $\frac{V_b}{R_2} = -\frac{V_f}{R_1}$

$$C \frac{d(V_{out1} - V_b)}{dt} + \frac{V_f}{R_1} = 0$$

\*can also be done using laplace!!

$$C \frac{d(V_{out1} - V_b)}{dt} - \frac{V_b}{R_2} = 0$$

recall  $V_b = -\frac{R_2}{R_1} \cdot V_f$

$$C \frac{d(V_{out1} - V_b)}{dt} + \frac{R_2}{R_1} \cdot \frac{1}{R_2} \cdot V_f = 0$$

$$\frac{d(V_{out1} - V_b)}{dt} = -\frac{1}{C} \cdot \frac{R_2}{R_1} \cdot \frac{1}{R_2} \cdot V_f$$

$$d(V_{out1} - V_b) = -\frac{R_2}{R_1 R_2 \cdot C} \cdot V_f \cdot dt$$

Take integral of both sides.

$$\int d(V_{out1} - V_b) = \int -\frac{R_2}{R_1 R_2 \cdot C} \cdot V_f dt$$

$$V_{out1} - V_b = -\frac{R_2}{R_1 R_2 C} \int V_f dt$$

$$V_b = -\frac{R_2}{R_1} V_f$$

$$V_{out1} + \frac{R_2}{R_1} V_f = -\frac{R_2}{R_1 R_2 C} \int V_f dt$$

$$V_{out1} = -\frac{R_2}{R_1} V_f - \frac{R_2}{R_1} \cdot \frac{1}{R_2 C} \int V_f dt$$

inverting circuit  $V_{out} = -\frac{R}{R} (V_{in}) = -V_{in}$  hence  $V_{out} = -V_{in}$   
inverting

$$V_{out} = \frac{R_2}{R_1} V_f + \frac{R_2}{R_1} \cdot \frac{1}{R_2 C} \int V_f dt$$

Taking initial condition into consideration.

$$V_{out} = \frac{R_2}{R_1} V_f + \frac{R_2}{R_1} \cdot \frac{1}{R_2 C} \int V_f dt + V_{co}$$

recall for PI controller mode

~~$$R_2 \cdot V_f \cdot \frac{1}{R_1} + \frac{R_2}{R_1} \cdot \frac{1}{R_2 C} \int V_f dt + V_{co}$$~~

$$V_{out} = G_p V_f + G_p G_I \int_0^t V_e dt + V_{co} \quad \dots \dots \dots \text{(eqn ***)}$$

comparing coefficients,


$$G_P = \frac{R_2}{R_1} = \text{proportional gain}$$

$$G_I = \frac{1}{R_2 \cdot C} = \text{integral gain}$$

$$V_{out} = G_P V_e + G_P G_I \int_0^t V_e \cdot dt + V_{co}$$

Question 2.

Proportional Derivative controller mode.

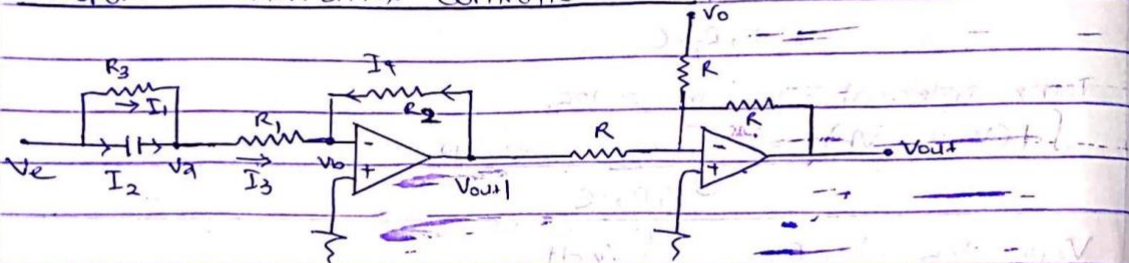

No current flows through the op-amp, hence no voltage across

$$V_b = 0$$

finding equation for I using KCL.

$$I_1 + I_2 = I_3 \quad \dots \quad I_1 + I_2 - I_3 = 0$$

$$I_3 + I_4 = 0 \quad \dots \quad I_1 + I_2 + I_4 = 0$$

Resolving parallel resistors  $R_1$  &  $R_3$

$$R = \frac{R_1 \times R_3}{R_1 + R_3} \quad ; \quad R = \text{effective resistance}$$

$$2\pi f_{max} RC = 0.1$$

finding I using ohm's law.

$$I_1 = \frac{V_e - V_b}{R_3}$$

$$I_2 = \frac{C d(V_e - V_a)}{dt}$$

$$I_3 = \frac{V_a - V_b}{R_1} = \frac{V_a}{R_1}$$

$$I_4 = \frac{V_{out1} - V_b}{R_2} = \frac{V_{out1}}{R_2}$$

Substituting I into KCL eqn.

$$\frac{V_F - V_A}{R_3} + C \frac{d(V_F - V_A)}{dt} - \frac{V_A}{R_1} = 0$$

$$\frac{V_{out} - V_b}{R_2} + \frac{V_A - V_b}{R_1} = I_3 + I_4 = 0 \quad ; V_b = 0$$

$$\frac{V_{out}}{R_2} + \frac{V_A}{R_1} = 0$$

$$V_A = -\frac{R_1}{R_2} \cdot V_{out}$$

$$I_1 + I_2 + I_4 = 0$$

$$\frac{V_F - V_A}{R_3} + C \frac{d(V_F - V_A)}{dt} + \frac{V_{out}}{R_2} = 0$$

Taking Laplace transform.

$$\frac{V_F(s) - V_A(s)}{R_3} + sC[V_F(s) - V_A(s)] + \frac{V_{out}(s)}{R_2} = 0$$

$$\frac{V_F(s)}{R_3} + sC V_F(s) + \frac{V_{out}(s)}{R_2} = \frac{V_A(s)}{R_3} + sC V_A(s)$$

$$\frac{V_{out}(s)}{R_2} - \frac{V_A(s)}{R_3} - sC V_A(s) = -\frac{V_F(s)}{R_3} - sC V_F(s)$$

$$\text{recall } V_A = -\frac{R_1}{R_2} \cdot V_{out}$$

$$\frac{V_{out}(s)}{R_2} + \frac{R_1}{R_2 \cdot R_3} \cdot V_{out} + sC \cdot \frac{R_1}{R_2} \cdot V_{out} = -\frac{V_F(s)}{R_3} - sC V_F(s)$$

$$V_{out}(s) \left[ \frac{1}{R_2} + \frac{R_1}{R_2 R_3} + \frac{sC R_1}{R_2} \right] = -\frac{V_F(s)}{R_3} - sC V_F(s)$$

$$V_{out}(s) \left[ \frac{R_3 + R_1 + sC R_1 R_3}{R_2 R_3} \right] = -\frac{V_F(s)}{R_3} - sC V_F(s)$$

$$V_{out}(s) = \left[ \frac{R_2 R_3}{R_3 + R_1 + sC R_1 R_3} \right] \cdot \frac{-V_F(s) - sC V_F(s)}{R_3}$$

$$V_{out}(s) = \left[ \frac{(R_2 R_3) / (R_1 + R_3)}{\frac{R_3 + R_1}{R_1 + R_3} + \frac{sC R_1 R_3}{R_1 + R_3}} \right] \cdot \frac{-V_F(s) - sC V_F(s)}{R_3}$$

$$V_{out}(s) = \left[ \frac{R_2 R_3 / (R_1 + R_3)}{1 + s C R_1 R_3} \right] \cdot \left[ \frac{-V_e(s) - s C V_e(s)}{R_3} \right]$$

recall  $R = \text{effective resistance} = \frac{R_1 R_3}{R_1 + R_3}$

$$V_{out}(s) = \left[ \frac{R_2 R_3 / (R_1 + R_3)}{1 + s C R} \right] \cdot \left[ \frac{-V_e(s) - s C V_e(s)}{R_3} \right]$$

if  $s C R \ll 1$   $1 + s C R \approx 1$

$$V_{out}(s) \approx \frac{R_2 R_3}{R_1 + R_3} \cdot \left[ \frac{-V_e(s) - s C V_e(s)}{R_3} \right]$$

$$V_{out}(s) = -V_e(s) \cdot \left[ \frac{R_2}{R_1 + R_3} \right] - s C V_e(s) \cdot \left[ \frac{R_2 R_3}{R_1 + R_3} \right]$$

inverse Laplace  $L^{-1}$

$$V_{out}(t) = -V_e \left[ \frac{R_2}{R_1 + R_3} \right] - C \frac{dV_e}{dt} \cdot \left[ \frac{R_2 R_3}{R_1 + R_3} \right]$$

from the inverter circuit

$$V_{out} = -(V_{out} - V_0) = V_0 - V_{out}$$

$$V_0 - V_{out} = -V_e \left[ \frac{R_2}{R_1 + R_3} \right] - C \frac{dV_e}{dt} \left[ \frac{R_2 R_3}{R_1 + R_3} \right]$$

$$-V_{out} = \left[ \frac{R_2}{R_1 + R_3} \right] \cdot V_e - \left[ \frac{R_2 R_3}{R_1 + R_3} \right] \cdot C \frac{dV_e}{dt} - V_0$$

$$V_{out} = V_e \left[ \frac{R_2}{R_1 + R_3} \right] + R_3 C \frac{dV_e}{dt} \left[ \frac{R_2}{R_1 + R_3} \right] + V_0$$

Proportional gain  $G_p = \frac{R_2}{R_1 + R_3}$

Integrative gain  $G_D = R_3 C$

$$V_{out} = G_p \cdot V_e + G_D G_p \cdot \frac{dV_e}{dt} + V_0$$