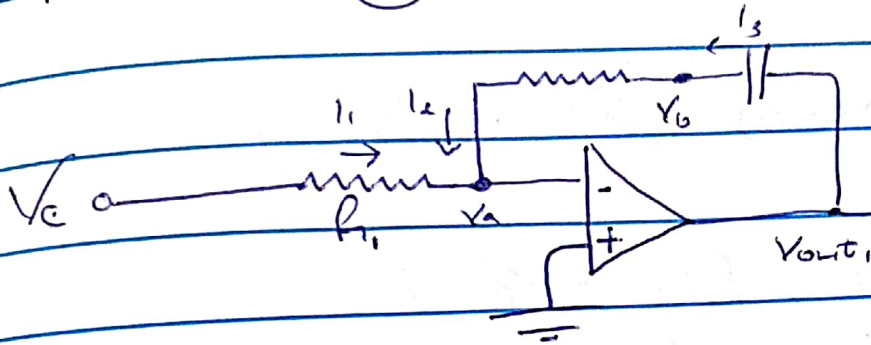


Victor Adeboyo - Ktünpe R

17 / Aug 04 / 079

Electrical and Electronics Engineering  
Process control and Automation

1) Proportional - Integral controller



Taking KCL equations

$$I_1 + I_2 = 0 \quad \dots (a)$$

$$I_2 - I_3 = 0 \quad \dots (b)$$

$$I_1 = \frac{V_c - V_a}{R_1} \Rightarrow \frac{V_c}{R_1}$$

$$I_2 \Rightarrow \frac{V_b - V_a}{R_2} \Rightarrow \frac{V_b}{R_2}$$

$$I_3 = C \frac{d(V_{out} - V_b)}{dt}$$

Subbing into equation (a) and (b)

$$\frac{V_c}{R_1} + \frac{V_b}{R_2} = 0 \quad \Rightarrow V_b = -\frac{R_2}{R_1} V_c$$

$$\frac{V_b}{R_2} - C \frac{d(V_{out} - V_b)}{dt} = 0 \quad \dots (c)$$

Taking Laplace transform of equ (c)

$$V_b(s)/R_2 - sC(V_{out}(s) - V_b(s)) = 0$$

$$V_b(s)/R_2 + sCV_b(s) = sC(V_{out}(s))$$

$$V_b(s) \left( sC + \frac{1}{R_2} \right) = sC V_{out}(s)$$

$$V_b(s) = -\frac{R_2}{R_1} V_e(s)$$

$$sC V_{out}(s) = -\frac{R_2}{R_1} V_e(s) \left( sC + \frac{1}{R_2} \right)$$

$$V_{out}(s) = \frac{-R_2}{sCR_1} V_e(s) \left( sC + \frac{1}{R_2} \right)$$

$$V_{out}(s) = -\frac{R_2}{R_1} V_e(s) + \frac{R_2}{R_1} \cdot \frac{1}{sCR_2} V_e(s)$$

$V_{out} = -V_{out}$  is Inverting amplifier

$$V_{out}(s) = \frac{R_2}{R_1} V_e(s) + \frac{R_2}{R_1} \cdot \frac{1}{sCR_2} V_e(s)$$

Taking inverse Laplace

$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1} \cdot \frac{1}{R_2} \int_0^t V_e(\tau) d\tau + V_0$$


Expressed alternatively

$$V_{out} = G_P V_e + G_P G_I \int_0^t V_e d\tau + V_0$$

where  $G_P = R_2/R_1$

$$G_I = \frac{1}{R_2 C}$$

2) Proportional Derivative controller.

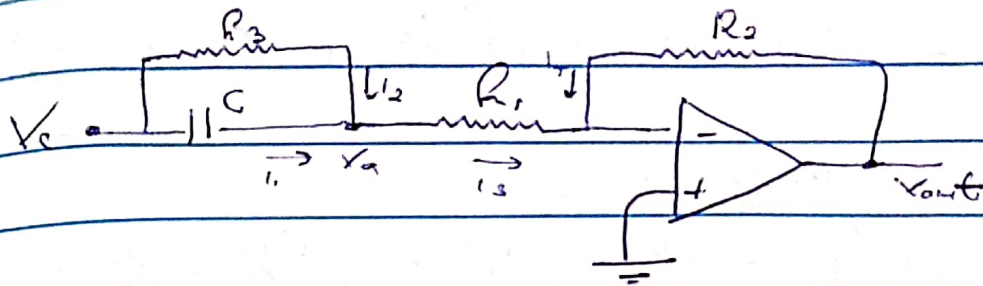

$$I_1 + I_2 = I_3 \quad \dots (a)$$

$$I_2 + I_4 = 0 \quad \dots (b)$$

$$I_1 = \frac{V_c - V_a}{R_3}$$

$$I_2 = C \frac{d}{dt} (V_c - V_a)$$

$$I_3 = \frac{V_a - V_b}{R_1} \quad (1.c) \Rightarrow I_3 = \frac{V_a}{R_1}$$

$$I_4 = \frac{V_{out} - V_b}{R_2} \Rightarrow I_4 = \frac{V_{out}}{R_2}$$

Sub into eqn (a) and (b)

$$\frac{V_c - V_a}{R_3} + C \frac{d(V_c - V_a)}{dt} = \frac{V_a}{R_1} \quad \dots (c)$$

$$\frac{V_a}{R_1} + \frac{V_{out}}{R_2} = 0 \quad \dots (d)$$

$$\therefore \frac{V_a}{R_1} = -\frac{V_{out}}{R_2}$$

$$= V_a = -\frac{R_1}{R_2} V_{out}$$

From equation (c)

$$\frac{V_c - V_a}{R_3} + C \frac{d(V_c - V_a)}{dt} - \frac{V_a}{R_1} = 0$$

Taking Laplace transform

$$\frac{V_c(s) - V_a(s)}{R_3} + sC(V_c(s) - V_a(s)) - \frac{V_a(s)}{R_1} = 0$$

$$\frac{V_e(s)}{R_3} + S(V_e(s)) = \frac{V_a(s)}{R_1} + \frac{V_a(s)}{R_3} + S C(V_a(s))$$

$$V_e(s) \left( \frac{1}{R_3} + S C \right) = V_a(s) \left\{ \frac{1}{R_1} + \frac{1}{R_3} + S C \right\}$$

But  $V_a = -\frac{R_1}{R_2} V_{out}$

$$V_e(s) \left\{ \frac{1}{R_3} + S C \right\} = -\frac{R_1}{R_2} V_{out}(s) \left\{ \frac{1}{R_1} + \frac{1}{R_3} + S C \right\}$$

$$V_e(s) \left\{ 1 + \frac{R_3 S C}{R_3} \right\} = -\frac{R_1}{R_2} V_{out}(s) \left\{ \frac{R_3 + R_1 + S C R_1 R_3}{R_1 R_3} \right\}$$

$$\Rightarrow V_e(s) \{ 1 + S C R_3 \} = -\frac{V_{out}}{R_2} \{ R_3 + R_1 + S C R_1 R_3 \}$$

$$-V_{out}(s) = \frac{V_e(s) (1 + S C R_3) R_2}{R_1 + R_3 + S C R_1 R_3}$$

Dividing through by  $R_1 + R_3$  and also since  $\frac{R_1 R_3}{R_1 + R_3} = R$  [equivalent resistance]

$$-V_{out}(s) = V_e(s) \frac{R_2 + S C R_3 R_2}{R_1 + R_3 + \frac{S C R_1 R_3}{R_1 + R_3}}$$

$$-V_{out}(s) = V_e(s) \cdot \frac{R_2 + S C R_3 R_2}{1 + S C R}$$

If  $S C R \ll 1$

$$-V_{out}(s) = V_e(s) \frac{R_2 + S C R_3 R_2}{R_1 + R_3}$$

$$V_{out} = -V_{out} + V_0$$

$$V_{out}(s) + V_0 = \frac{V_e (R_2 + sC R_2 R_3)}{R_1 + R_3}$$

$$V_{out}(s) - V_0 = \frac{V_e(s) R_2}{R_1 + R_3} + \frac{s C R_2 R_3 V_e(s)}{R_1 + R_3}$$

Taking inverse laplace

$$V_{out} = \frac{R_2}{R_1 + R_3} V_e + \frac{R_2}{R_1 + R_3} R_3 C \frac{dV_e}{dt} + V_0$$

$$V_{out} = G_p V_e + G_p G_D \frac{dV_e}{dt} + V_0$$

where,  $G_p = \frac{R_2}{R_1 + R_3}$

$$G_D = R_3 C$$