

EEE 561 ASSIGNMENT (PROCESS CONTROL & AUTOMATION)

(1) PI controller

$$V_A = 0, I_1 + I_2 = 0, I_3 - I_2 = 0$$

Current through the capacitor

$$I_c = C \frac{dV_c}{dt}$$

$$I_1 = \frac{V_e - V_A}{R_1} \quad (V_A = 0)$$

$$= V_e / R_1$$

$$I_2 = \frac{V_b - V_A}{R_2} \quad (V_A = 0)$$

$$= V_b / R_2$$

$$I_3 = C \frac{d(V_{out1} - V_b)}{dt}$$

Sub into eqn (1) and (2)

$$V_e / R_1 + V_b / R_2 = 0 \quad \dots (3)$$

$$C \frac{d(V_{out1} - V_b)}{dt} - V_b / R_2 = 0 \quad \dots (4)$$

from (3)

$$V_b / R_2 = -V_e / R_1$$

$$V_b = -R_2 / R_1 V_e$$

taking Laplace transform of (4)

$$sC(V_{out1}(s) - V_b(s)) - (V_b(s) / R_2) = 0$$

$$sC V_{out1}(s) = sC V_b(s) + V_b(s) / R_2$$

$$sC V_{out1}(s) = V_b(s) (sC + 1/R_2)$$

$$\text{recall, } V_b = -R_2 / R_1 V_e$$

$$sC V_{out1}(s) = -R_2 / R_1 V_e(s) (sC + 1/R_2)$$

$$V_{out1}(s) = -R_2 / s R_1 V_e(s) (sC + 1/R_2)$$

$$V_{out1}(s) = -R_2 / R_1 V_e(s) - (R_2 / R_1) (1 / s C R_2) V_e(s)$$

from the inverting circuit

$$V_{out1} = -V_{out}$$

$$\therefore V_{out}(s) = - \left(-R_2 / R_1 V_e(s) - \frac{R_2}{R_1} \frac{1}{s C R_2} V_e(s) \right)$$

$$V_{out}(s) = \frac{R_2}{R_1} V_e(s) + \frac{R_2}{R_1} \frac{1}{s C R_2} V_e(s)$$

taking the inverse laplace

$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1 R_2 C} \int_0^t V_e(t) dt + V_0$$
$$\left(\frac{1}{s} = \int_0^t dt + K \right)$$

$$V_{out} = G_p V_e + G_p G_I \int_0^t V_e dt + V_0$$

$$\text{where } G_p = R_2/R_1$$

$$G_I = 1/R_2 C$$

2) PD controller

$$I_1 + I_2 = I_3 \quad \dots (1)$$

$$I_3 + I_4 = 0 \quad \dots (2)$$

$$I_1 = \frac{V_e - V_a}{R_3}$$

$$I_2 = C \frac{d(V_e - V_a)}{dt}$$

$$I_3 = \frac{V_a - V_b}{R_1} \quad (V_b = 0)$$

$$= \frac{V_a}{R_1}$$

$$I_4 = \frac{V_{out2} - V_b}{R_2} \quad (V_b = 0)$$

$$= \frac{V_{out2}}{R_2}$$

$$\# R = \frac{R_1 R_3}{R_1 + R_3} \quad \text{--- effective resistance}$$

Sub into eq(1) and eq(2)

$$\frac{V_e - V_a}{R_3} + C \frac{d(V_e - V_a)}{dt} = \frac{V_a}{R_1} \quad \dots (3)$$

$$\frac{V_a}{R_1} + \frac{V_{out2}}{R_2} = 0 \quad \dots (4)$$

from (4)

$$\frac{V_a}{R_1} = -\frac{V_{out2}}{R_2}$$

$$V_a = -R_1/R_2 V_{out1}$$

rearranging (3)

$$\frac{V_e - V_a}{R_3} + C \frac{d(V_e - V_a)}{dt} - \frac{V_a}{R_1} = 0$$

taking laplace transform

$$\frac{V_{e(s)} - V_{a(s)}}{R_3} + sC(V_{e(s)} - V_{a(s)}) - \frac{V_{a(s)}}{R_1} = 0$$

(initial conditions go to zero)

$$\frac{V_{e(s)}}{R_3} + sC V_{e(s)} = \frac{V_{a(s)}}{R_1} + \frac{V_{a(s)}}{R_3} + sC V_{a(s)}$$

$$V_{e(s)} \left(\frac{1}{R_3} + sC \right) = V_{a(s)} \left(\frac{1}{R_1} + \frac{1}{R_3} + sC \right)$$

recall $V_a = -R_1/R_2 V_{out1}$

$$V_{e(s)} \left(\frac{1}{R_3} + sC \right) = -R_1/R_2 V_{out1(s)} \left(\frac{1}{R_1} + \frac{1}{R_3} + sC \right)$$

~~XXXXXXXXXX~~ taking the LCM

$$V_{e(s)} \left(\frac{1 + R_3 s C}{R_3} \right) = -\frac{R_1}{R_2} V_{out1(s)} \left(\frac{R_3 + R_1 + s C R_1 R_3}{R_1 R_3} \right)$$

$$V_{e(s)} (1 + s C R_3) = -\frac{V_{out1(s)}}{R_2} (R_3 + R_1 + s C R_1 R_3)$$

making $-V_{out1(s)}$ subject of formula

$$-V_{out1(s)} = \frac{V_{e(s)} (R_2 + s C R_2 R_3)}{(R_1 + R_3 + s C R_1 R_3)}$$

dividing the numerator and denominator by $(R_1 + R_3)$

$$-V_{out1(s)} = \frac{V_{e(s)} (R_2 + s C R_2 R_3) / (R_1 + R_3)}{\frac{R_1 + R_3}{R_1 + R_3} + \frac{s C R_1 R_3}{R_1 + R_3}}$$

recall, $R = \frac{R_1 R_3}{R_1 + R_3}$

$$-V_{out1(s)} = \frac{V_{e(s)} (R_2 + s C R_2 R_3) / (R_1 + R_3)}{1 + s C R}$$

if $s C R \ll 1$

$$-V_{out1(s)} = \frac{V_{e(s)} (R_2 + s C R_2 R_3)}{R_1 + R_3}$$

from the inverting circuit, $V_{out1} = -V_{out} + V_0$

$$\therefore -(-V_{out(s)} + V_0) = \frac{V_{e(s)} (R_2 + s C R_2 R_3)}{R_1 + R_3}$$

$$V_{out}(s) - V_0 = \frac{V_{in}(s) R_2}{R_1 + R_3} + \frac{s C R_2 R_3}{R_1 + R_3} V_{in}(s)$$

$$V_{out}(s) = \frac{V_{in}(s) R_2}{R_1 + R_3} + \frac{V_{in}(s) s C R_2 R_3}{R_1 + R_3} + V_0$$

taking inverse laplace

$$V_{out} = \frac{R_2}{R_1 + R_3} V_{in} + \frac{R_2 R_3 C}{R_1 + R_3} \frac{dV_{in}}{dt} + V_0$$

comparing with

$$V_{out} = G_p V_{in} + G_p G_D \frac{dV_{in}}{dt} + V_0$$

$$\text{where } G_p = \frac{R_2}{R_1 + R_3}$$

$$G_D = R_3 C$$