

NAME: Tomilayo Aduco


MATRIC NO: 17/ENG05/042

COURSE CODE: MCI 511

DATE: 30/12/2020

Assignment

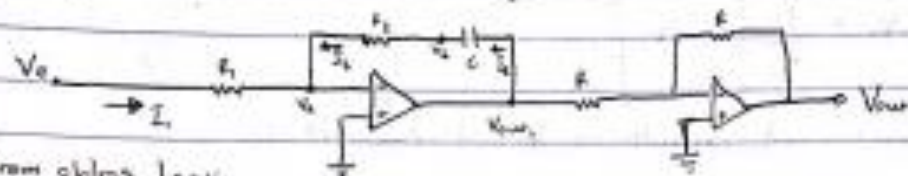Proving for Proportional-Integral mode [PI]



From Ohm's Law;

$$V_a = 0 \quad \text{Current through the capacitor}$$

$$I_1 + I_2 = 0 \quad \text{--- (1)} \quad I_c = C \frac{dV_b}{dt}$$

$$I_3 - I_2 = 0 \quad \text{--- (2)}$$

* Combining this with Ohm's law

$$I_1 = \frac{V_a}{R_1} \quad I_2 = \frac{V_b}{R_2}$$

$$I_3 = C \frac{d}{dt} [V_{out} - V_b]$$

* Plugging back into eqn 1

$$\frac{V_a}{R_1} + \frac{V_b}{R_2} = 0$$

$$V_b = -\frac{R_2}{R_1} V_a$$

* Plugging back into eqn 2

$$C \frac{d}{dt} [V_{out} - V_b] - \frac{V_b}{R_2} = 0$$

* We then add eqn (1) & (2)

which will give $I_1 + I_2 = 0$

$$\therefore \frac{V_a}{R_1} + C \frac{d}{dt} [V_{out} - V_b] = 0$$

$$C \frac{d}{dt} [V_{out} - V_b] = -\frac{V_a}{R_1}$$

$$d[V_{out} - V_b] = -\frac{1}{CR_1} V_a dt$$

$$V_{out} - V_b = -\frac{1}{CR_1} \int V_a dt$$

$$V_{out,1} - V_0 = -\frac{1}{CR_1} \int V_e dt$$

$$V_{out,1} = V_0 - \frac{1}{CR_1} \int V_e dt$$

$$V_{out,1} = -\frac{R_2}{R_1} V_e - \frac{1}{CR_1} \int V_e dt$$

$$V_{out,1} = -\left[\frac{R_2}{R_1} V_e + \frac{1}{CR_1} \int V_e dt \right]$$

* After Inverting circuit and considering initial conditions

$$V_{out} = -V_{out,1}$$

$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1} \cdot \frac{1}{R_2 C} \int V_e dt$$


$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1} \frac{1}{R_2 C} \int_0^t V_e dt + V(0)$$

$$\text{Proportional Gain } (G_P) = \frac{R_2}{R_1}$$

$$\text{Integral Gain } (G_I) = \frac{1}{R_2 C}$$

$$V_{out} = G_P V_e + G_P G_I \int_0^t V_e dt + V(0)$$

Proving for Proportional Derivative mode

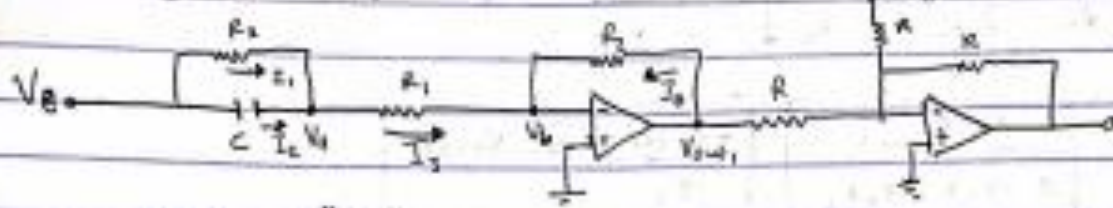

where:

$$R = \frac{R_1 R_2}{R_1 + R_2} \quad R = \text{Effective Resistance}$$

The condition becomes as used $\rightarrow 2\pi f_m R C = 0.1$

by Kirchhoff's Current Law

$$I_1 + I_2 = I_3$$

$$I_1 + I_2 - I_3 = 0 \quad \text{--- (1)}$$

$$I_4 + I_3 = 0 \quad \text{--- (2)}$$

$$I_1 = \frac{V_e - V_o}{R_2} \quad I_2 = C \frac{d}{dt} [V_e - V_o] \quad I_3 = \frac{V_o}{R_1} \quad I_4 = \frac{V_{out1}}{R_2}$$

Eqn 1 * Putting back into eqn 1

$$\frac{V_e - V_o}{R_2} + C \frac{d}{dt} [V_e - V_o] - \frac{V_o}{R_1} = 0$$

* Putting back into eqn 2

$$\frac{V_{out1}}{R_2} + \frac{V_o}{R_1} = 0$$

$$V_o = -\frac{R_1}{R_2} V_{out1}$$

adding eqn (1) * (2)

$$I_1 + I_2 + I_4 = 0$$

hence;

$$\frac{V_e - V_o}{R_2} + C \frac{d}{dt} [V_e - V_o] + \frac{V_{out1}}{R_2} = 0$$

* taking Laplace transform

$$\frac{V_e(s) - V_o(s)}{R_2} + sC [V_e(s) - V_o(s)] + \frac{V_{out1}(s)}{R_2} = 0$$

$$\frac{V_{out1}(s)}{R_2} = \frac{1}{R_2} \left(-\frac{R_1}{R_1} V_{out1}(s) \right) = sC \left(\frac{-R_1}{R_2} V_{out1}(s) \right) = \frac{V_e(s)}{R_2} - sC V_e(s)$$

$$V_{out}(s) \left[\frac{1}{R_2} + \frac{R_1}{R_2 R_3} + \frac{SC R_1}{R_2} \right] = \frac{-V_0(s) - SC V_0(s)}{R_3}$$

$$V_{out}(s) = \left[\frac{R_2 R_3}{R_1 + R_2 + SC R_1 R_3} \right] \left[\frac{-V_0(s) - SC V_0(s)}{R_2} \right]$$

$$V_{out}(s) = \left[\frac{\frac{R_2 R_3}{R_1 + R_2}}{1 + SC R} \right] \left[\frac{-V_0(s) - SC V_0(s)}{R_2} \right]$$

* assume $SC R \ll 1$

$$V_{out}(s) = \left[\frac{R_2 R_3}{R_1 + R_2} \right] \left[\frac{-V_0(s) - SC V_0(s)}{R_2} \right]$$

$$V_{out}(s) = - \left[\frac{R_2}{R_1 + R_2} \right] V_0(s) - \left[\frac{R_2 R_3}{R_1 + R_2} \right] SC V_0(s)$$

* Inverse Laplace will give

$$V_{out} = - \left[\frac{R_2}{R_1 + R_2} \right] V_0 - \left[\frac{R_2 R_3}{R_1 + R_2} \right] C \frac{dV_0}{dt}$$

* From inverter circuit we have

$$V_{out} = -V_{in} + V_0$$

$$V_{out} = - \left[\frac{R_2}{R_1 + R_2} \right] V_0 - \left[\frac{R_2 R_3}{R_1 + R_2} \right] C \frac{dV_0}{dt}$$

$$G_F = \frac{R_2}{R_1 R_2}$$

Hence

$$V_{out} = \left[\frac{R_2}{R_1 + R_2} \right] V_0 + \left[\frac{R_2}{R_1 + R_2} \right] R_3 C \left(\frac{dV_0}{dt} + V_0 \right) \quad G_D = R_3 C$$

then,

$$V_{out} = G_F V_0 + G_D G_D \frac{dV_0}{dt} + V_0$$