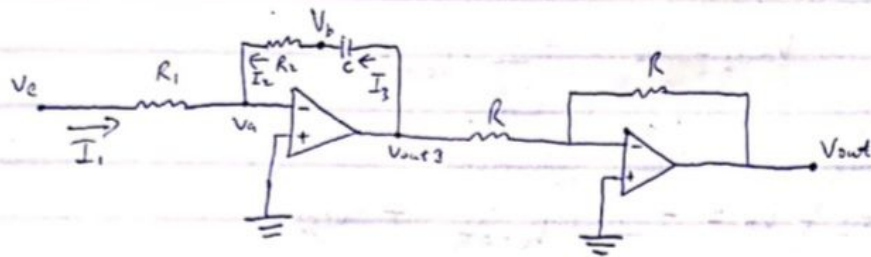


Assignment Solution

Proportional-Integral mode Controller (PI Controller)



$$V_a = 0$$

using Ohm's law

$$I_1 + I_2 = 0 \quad \text{--- (1)}$$

$$I_3 - I_2 = 0 \quad \text{--- (2)}$$

$$I_1 = \frac{V_e}{R_1}$$

$$I_2 = \frac{V_b}{R_2}$$

$$I_3 = C \frac{d[V_{out1} - V_b]}{dt}$$

from eqn (1)

$$\frac{V_e}{R_1} + \frac{V_b}{R_2} = 0$$

$$V_b = -\frac{R_2}{R_1} V_e$$

\therefore adding eqn (1) & (2) we have

$$I_1 + I_3 = 0$$

$$\therefore \frac{V_e}{R_1} + C \frac{d[V_{out1} - V_b]}{dt} = 0$$

$$\therefore C \frac{d[V_{out1} - V_b]}{dt} = -\frac{V_e}{R_1}$$

$$d[V_{out1} - V_b] = -\frac{1}{CR_1} \cdot V_e dt$$

~~taking the~~ Integrating Both sides

$$\int d[V_{out1} - V_b] = \int -\frac{1}{CR_1} \cdot V_e dt$$

$$\therefore V_{out1} - V_b = -\frac{1}{CR_1} \int V_e dt$$

Considering initial conditions

~~$$V_{out1} - V_b = -\frac{1}{CR_1} \left(\int_0^t V_e \cdot dt + V_{cos} \right)$$~~

~~$$\therefore V_{out1} = V_b - \frac{1}{CR_1} \left(\int_0^t V_e \cdot dt + V_{cos} \right)$$~~

~~$$V_{out1} = -\frac{R_2 \cdot V_e}{R_1} - \frac{1}{CR_1} \int_0^t V_e dt + V_{cos}$$~~

~~$$\therefore V_{out1} = -\left[\frac{R_2}{R_1} V_e + \frac{1}{R_1 CR_1} \int_0^t V_e dt + V_{cos} \right]$$~~

$$\therefore V_{out1} - V_b = -\frac{1}{CR_1} \int V_e dt$$

$$V_{out1} = V_b - \frac{1}{CR_1} \int V_e dt$$

$$V_{out1} = -\frac{R_2}{R_1} V_e - \frac{1}{CR_1} \int V_e dt$$

$$V_{out1} = -\left[\frac{R_2}{R_1} V_e + \frac{1}{CR_1} \int V_e dt \right]$$

After inverting

$$V_{out} = -V_{out1}$$

$$\therefore V_{out} = \left[\frac{R_2}{R_1} V_e + \frac{1}{R_1 CR_1} \int V_e dt \right]$$

\therefore take initial conditions into consideration


$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1} \cdot \frac{1}{R_1 C} \int_0^t V_e dt + V_{os}$$

$$G_P = \frac{R_2}{R_1} \quad \text{--- --- --- Proportional Gain}$$

$$G_I = \frac{1}{R_1 C} \quad \text{--- --- --- Integral Gain}$$

$$\therefore V_{out} = G_P V_e + G_P G_I \int_0^t V_e dt + V_{os}$$

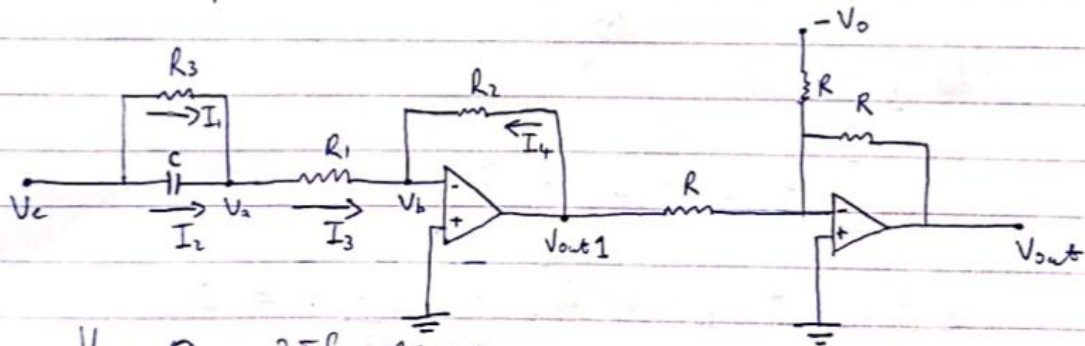Proportional - Derivative mode Controller (PD Controller)



$$V_b = 0 \quad 2\pi f_{max} RC = 0.1$$

Using KCL (Kirchhoff's Current Law)

$$I_1 + I_2 = I_3$$

$$I_1 + I_2 - I_3 = 0 \quad \text{--- --- --- (1)}$$

$$I_4 + I_3 = 0 \quad \text{--- --- --- (2)}$$

effective Resistance, $R = \frac{R_1 R_3}{R_1 + R_3}$

$$I_1 = \frac{V_e - V_a}{R_3}$$

$$I_2 = C \frac{d}{dt} [V_c - V_a]$$

$$I_3 = \frac{V_a}{R_1}$$

$$I_4 = \frac{V_{out1}}{R_2}$$

from equation (1)

$$\therefore \frac{V_c - V_a}{R_3} + C \frac{d}{dt} [V_c - V_a] - \frac{V_a}{R_1} = 0$$

from equation (2)

$$\frac{V_{out1}}{R_2} + \frac{V_a}{R_1} = 0$$

$$V_a = - \frac{R_1}{R_2} V_{out1}$$

adding eqn (1) & (2)

$$I_1 + I_2 + I_4 = 0$$

$$\therefore \frac{V_c - V_a}{R_3} + C \frac{d}{dt} [V_c - V_a] + \frac{V_{out1}}{R_2} = 0$$

taking the Laplace transform

$$\frac{V_c(s) - V_a(s)}{R_3} + sC [V_c(s) - V_a(s)] + \frac{V_{out1}(s)}{R_2} = 0$$

$$\therefore \frac{V_{out1}(s)}{R_2} - \frac{V_a(s)}{R_3} - sC V_a(s) = - \frac{V_c(s)}{R_3} + sC V_c(s)$$

$$\frac{V_{out1}(s)}{R_2} - \frac{1}{R_3} \left(- \frac{R_1}{R_2} V_{out1}(s) \right) - sC \left(- \frac{R_1}{R_2} V_{out1}(s) \right) = - \frac{V_c(s)}{R_3} + sC V_c(s)$$

$$\frac{V_{out1}(s)}{R_2} + \frac{R_1}{R_3 R_2} V_{out1}(s) + \frac{SC R_1}{R_2} V_{out1}(s) = -\frac{V_e(s)}{R_3} - SC V_e(s)$$

$$V_{out1}(s) \left[\frac{1}{R_2} + \frac{R_1}{R_3 R_2} + \frac{SC R_1}{R_2} \right] = -\frac{V_e(s)}{R_3} - SC V_e(s)$$

$$V_{out1}(s) \left[\frac{R_3 + R_1 + SC R_1 R_3}{R_2 R_3} \right] = -\frac{V_e(s)}{R_3} - SC V_e(s)$$

$$V_{out1}(s) = \left[\frac{R_2 R_3}{R_1 + R_3 + SC R_1 R_3} \right] \left[-\frac{V_e(s)}{R_3} - SC V_e(s) \right]$$

$$\therefore V_{out1}(s) = \left[\frac{\frac{R_2 R_3}{R_1 + R_3}}{\frac{R_1 + R_3}{R_1 + R_3} + \frac{SC R_1 R_2}{R_1 + R_3}} \right] \left[-\frac{V_e(s)}{R_3} - SC V_e(s) \right]$$

$$V_{out1}(s) = \left[\frac{\frac{R_2 R_3}{R_1 + R_3}}{1 + SC R} \right] \left[-\frac{V_e(s)}{R_3} - SC V_e(s) \right]$$

$$\cancel{V_{out1}(s)} = \text{if } SC R \ll 1$$

$$V_{out1}(s) = \left[\frac{R_2 R_3}{R_1 + R_3} \right] \left[-\frac{V_e(s)}{R_3} - SC V_e(s) \right]$$

$$V_{out1}(s) = -\left[\frac{R_2}{R_1 + R_3} \right] V_e(s) - \left[\frac{R_2 R_3}{R_1 + R_3} \right] SC V_e(s)$$

taking the inverse Laplace Transform

$$V_{out1} = -\left[\frac{R_2}{R_1 + R_3} \right] V_e - \left[\frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dV_e}{dt}$$

from the inverter circuit

$$V_{out1} = -(V_{out} + (-V_o))$$

$$\therefore \cancel{V_{out1}} = -V_{out} + V_0$$

$$V_{out1} = - \left[\frac{R_2}{R_1 + R_3} \right] V_e - \left[\frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dV_e}{dt}$$

$$\therefore -V_{out} + V_0 = - \left[\frac{R_2}{R_1 + R_3} \right] V_e - \left[\frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dV_e}{dt}$$

$$-V_{out} = - \left[\frac{R_2}{R_1 + R_3} \right] V_e - \left[\frac{R_2 R_3}{R_1 + R_3} \right] C \frac{dV_e}{dt} - V_0$$

$$\therefore V_{out} = \left[\frac{R_2}{R_1 + R_3} \right] V_e + \left[\frac{R_2}{R_1 + R_3} \right] R_3 C \frac{dV_e}{dt} + V_0$$

where

$$G_P = \frac{R_2}{R_1 + R_3} \quad \text{--- --- --- Proportional Gain}$$

$$G_D = R_3 C \quad \text{--- --- --- Derivative Gain}$$

$$\therefore V_{out} = G_P V_e + G_P G_D \frac{dV_e}{dt} + V_0$$