


Mordi Mark Chigozie

16/ENG05/023

Mechatronic Engineering

MCT 511

Assignment

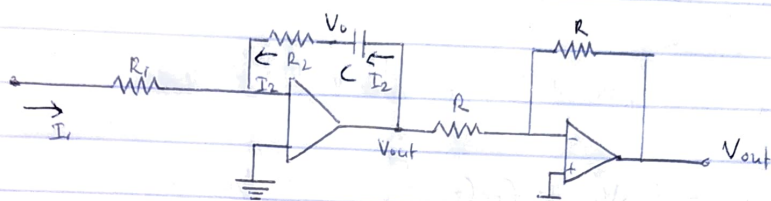

$$I_1 + I_2 = 0$$

$$I_3 - I_2 = 0$$

$$I_c = C \frac{dV_c}{dt}$$

Combine these with ohm's law

$$\frac{V_e}{R_1} + \frac{V_b}{R_2} = 0 \quad \text{--- (I)}$$

$$\frac{V_e}{R_1} - \frac{V_c}{R_2} = 0$$

$$C \frac{d}{dt} [V_{out} - V_0] - \frac{V_b}{R_2} = 0 \quad \text{--- (II)}$$

from (I)

$$V_0 = - \frac{R_2}{R_1} V_e \quad \text{--- (III)}$$

substitute (III) in (II)

$$C \frac{dV_{out}}{dt} - C \frac{d}{dt} \left[-\frac{R_2}{R_1} V_e \right] - \frac{1}{R_2} \left[-\frac{R_2}{R_1} V_e \right] = 0$$

$$C \frac{dV_{out}}{dt} + \frac{C R_2}{R_1} \frac{d}{dt} V_e + \frac{R_2}{R_1} \left[\frac{1}{R_2 C} V_e \right] = 0$$

multiply through by $1/C$

$$\frac{dV_{out}}{dt} + \frac{R_2}{R_1} \frac{d}{dt} V_e + \frac{R_2}{R_1} \left[\frac{1}{R_2 C} V_e \right] = 0$$

$$\frac{dV_{out}}{dt} = - \frac{R_2}{R_1} \frac{d}{dt} V_e - \left[\frac{1}{R_2 C} V_e \right] \frac{R_2}{R_1}$$

Integrating both sides

$$V_{out} = -\frac{R_2}{R_1} V_e - \frac{R_2}{R_1} \int_0^t \frac{1}{R_2 C} V_e dt + V_{e0}$$

After Inverting

$$V_{out} = \frac{R_2}{R_1} V_e + \frac{R_2}{R_1 R_2 C} \int_0^t V_e dt + V_{e0}$$

$$V_{out} = G_P V_e + G_P G_I \int_0^t V_e dt + V_{e0}$$


$$V_{out} = G_P V_e + G_P G_I \int_0^t V_e dt + V_{e0}$$

Where

$$G_P = \frac{R_2}{R_1} \quad \text{Proportional Gain}$$

$$G_I = \frac{1}{R_2 C} \quad \text{Integral Gain}$$

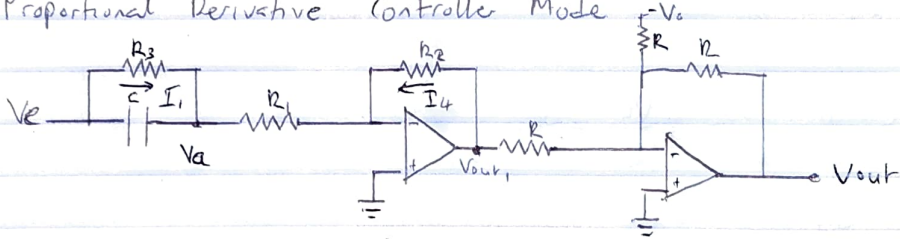2 Proportional Derivative Controller Mode



By KCL

$$I_1 + I_2 - I_3 = 0$$

$$I_4 + I_3 = 0$$

Combine with ohm's Law

$$\frac{V_e - V_0}{R_3} + C \frac{d}{dt} [V_e - V_0] - \frac{V_0}{R_1} = 0 \quad \text{--- (I)}$$

$$\frac{V_{out}}{R_2} + \frac{V_0}{R_1} = 0 \quad \text{--- (II)}$$

from equation (II)

$$V_0 = -\frac{R_1}{R_2} V_{out} \quad \text{--- (III)}$$

Substituting (iii) into (i)

$$\frac{V_e}{R_3} - \frac{1}{R_2} \left[\frac{-R_1 V_{out}}{R_2} \right] + \frac{C dV_e}{dt} - \frac{C d}{dt} \left[\frac{-R_1 V_{out}}{R_2} \right] - \left[\frac{-R_1 V_{out}}{R_2} \right] \frac{1}{R_1} = 0$$

$$\frac{V_e}{R_3} + \frac{R_1}{R_2 R_2} V_{out} + \frac{C dV_e}{dt} + \frac{R_1 C d}{dt} V_{out} + \frac{1}{R_2} V_{out} = 0$$

Multiply through by R_3

$$V_e + \frac{R_1}{R_2} V_{out} + R_3 \frac{C dV_e}{dt} + \frac{R_1 R_3 C dV_{out}}{dt} + \frac{R_3}{R_2} V_{out} = 0$$

$$\frac{R_3}{R_2} V_{out} + \frac{R_1 R_3 C dV_{out}}{dt} + \frac{R_3}{R_2} V_{out} = -V_e - R_3 \frac{C dV_e}{dt}$$

$$\left[\frac{R_1 + R_3}{R_2} \right] V_{out} + \frac{R_1 R_3 C dV_{out}}{dt} = -V_e - R_3 \frac{C dV_e}{dt}$$

Multiply through by $\left[\frac{R_2}{R_1 + R_3} \right]$

$$V_{out} + \left[\frac{R_1}{R_1 + R_3} \right] R_3 C \frac{dV_{out}}{dt} = - \left[\frac{R_2}{R_1 + R_3} \right] V_e - \left[\frac{R_2}{R_1 + R_3} \right] R_3 C \frac{dV_e}{dt}$$

After inverting

$$V_{out} + \left[\frac{R_1}{R_1 + R_3} \right] R_3 C \frac{dV_{out}}{dt} = \left[\frac{R_2}{R_1 + R_3} \right] V_e + \left[\frac{R_2}{R_1 + R_3} \right] R_3 C \frac{dV_e}{dt}$$

$$V_{out} \left[\frac{R_2}{R_1 + R_3} \right] V_e + \left[\frac{R_2}{R_1 + R_3} \right] R_3 C \frac{dV_e}{dt} + V_{out}$$

OR

$$V_{out} = G_p V_e + G_p G_{int} \frac{dV_e}{dt} + V_{out}$$

where

$$G_P = \frac{R_2}{R_1 + R_3} \quad - \quad \text{Proportional Gain}$$

$$G_D = R_3 C \quad - \quad \text{Derivative gain}$$