

NAME: NORNAH - ANOH ANNOJOH - NUTWAH.

COURSE: EEE 561 (Process Control & Automation)

MAT. NO: 16/EN904/035

DEPT: ELECTRICAL & ELECTRONICS

Derive the analysis for the output voltage using Operational Amplifier for:

① Proportional Integral controller mode (PI Mode)

②
From: $I_1 + I_2 = 0$ ——— ①

$$I_3 - I_2 = 0 \text{ ——— ②}$$

$$\text{But, } V_3 = 0$$

$$I_C = C \frac{dV_C}{dt}$$

$$I_1 = \frac{V_e - V_2}{R_1} \quad \{\text{subst. } V_2\}$$

$$= \frac{V_e}{R_1} \text{ ——— ③}$$

$$I_2 = \frac{V_b - V_2}{R_2} \Rightarrow \frac{V_b - 0}{R_2}$$

$$= \frac{V_b}{R_2} \text{ ——— ④}$$

$$I_3 = \frac{C d(V_{out1} - V_b)}{dt} \text{ ——— ⑤}$$

Subst. equ. 2, 4, 5 into equ. 1 & 2;

We have;


$$\frac{V_e}{R_1} + \frac{V_b}{R_2} = 0 \text{ ——— (*)}$$

$$\frac{C d(V_{out1} - V_b)}{dt} - \frac{V_b}{R_2} = 0 \text{ ——— (**)}$$

From equ. *

making V_b subject of formulae;

$$\frac{V_b}{R_2} = -\frac{V_e}{R_1}$$

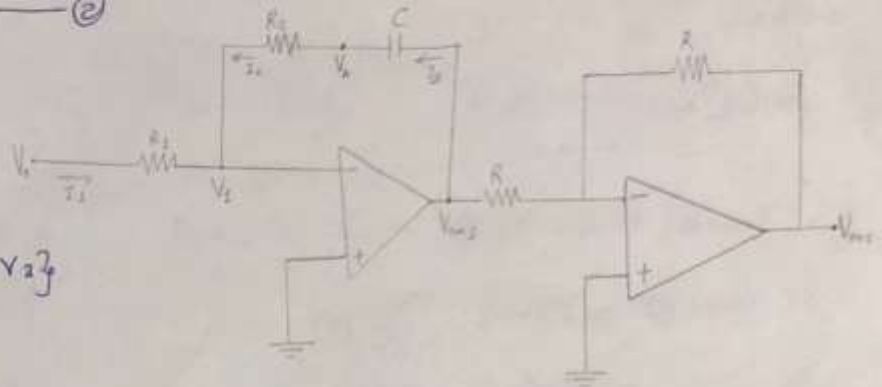

$$V_b = -\frac{V_e}{R_1} \times R_2$$

$$V_b = -\frac{R_2}{R_1} V_e$$

Take the Laplace transform of equ. (*),
We have;

$$sC[V_{out}(s) - V_b(s)] - \frac{V_b(s)}{R_2} = 0$$

$$[sC V_{out}(s) - sC V_b(s)] - \frac{V_b(s)}{R_2} = 0$$

$$sC V_{out}(s) = sC V_b(s) + \frac{V_b(s)}{R_2}$$

$$= V_b(s) \left(sC + \frac{1}{R_2} \right)$$

Subst. V_b ;

$$sC V_{out}(s) = -\frac{R_2}{R_1} V_e(s) \left[sC + \frac{1}{R_2} \right]$$

$$sC V_{out}(s) = -\frac{R_2}{R_1} sC V_e(s) - \frac{R_2}{R_1} \frac{1}{R_2} V_e(s) \quad (\text{Dividing both sides by } sC)$$

$$V_{out}(s) = -\frac{R_2}{R_1} V_e(s) - \frac{R_2}{R_1} \frac{1}{R_2} \frac{1}{sC} V_e(s)$$

But $V_{out}(s) = -V_{out}$ (From Inverting circuit)

$$-V_{out}(s) = -\frac{R_2}{R_1} V_e(s) - \frac{R_2}{R_1} \frac{1}{R_2} \frac{1}{s} V_e(s)$$

$$V_{out}(s) = -\left[-\frac{R_2}{R_1} V_e(s) - \frac{R_2}{R_1} \frac{1}{R_2} \frac{1}{s} V_e(s) \right]$$

$$= \frac{R_2}{R_1} V_e(s) + \frac{R_2}{R_1} \frac{1}{R_2} \frac{1}{s} V_e(s)$$

Taking the Laplace inverse,

We have;

$$V_{out} = \frac{R_2}{R_1} V_e(s) + \frac{R_2}{R_1} \frac{1}{R_2 C} \int_0^t V_e(t) \cdot dt + V(\omega)$$

But, $\frac{1}{s} = \int_0^t dt + K$

$$V_{out} = G_p V_e + G_p G_I \int_0^t V_e dt + V(\omega)$$

where $G_p = \frac{R_2}{R_1}$

$\times G_I = \frac{1}{R_2 C}$

② Proportional Differential controller mode (PD mode).

$I_1 + I_2 = I_3$ ——— ①

$I_3 + I_4 = 0$ ——— ②

$I_3 + I_4 = 0$
 $V_a = 0$

$I_2 = \frac{V_e - V_2}{R_3}$


$I_e = \frac{C d(V_e - V_2)}{dt}$

$I_3 = \frac{V_2 - V_b}{R_1}$

$I_3 = \frac{V_2}{R_1}$

$I_4 = \frac{V_{out1} - V_b}{R_2}$

$I_3 \Rightarrow \frac{V_{out1}}{R_1}$

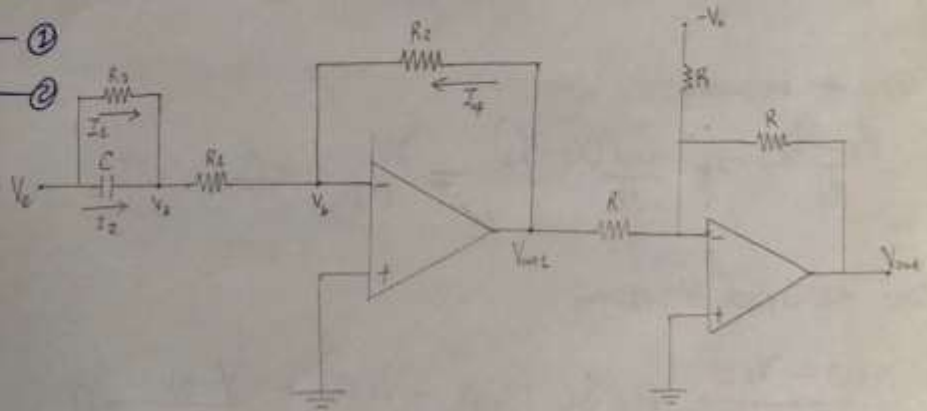

Effective resistance, $R = \frac{R_1 R_3}{R_1 + R_3}$

Subt $I_2, I_3, I_3 \times I_1$ into eqn. ① \times ③

We have;

$$\frac{V_e - V_2}{R_3} + \frac{C d(V_e - V_2)}{dt} = \frac{V_2}{R_1} \quad \text{--- (*)}$$

$$\frac{V_2}{R_1} + \frac{V_{out 1}}{R_2} \rightarrow \underline{\underline{0}} \quad \text{--- (**)}$$

From eqn. 2;

Making V_2 subj. of the formulae.

$$\frac{V_2}{R_1} = -\frac{V_{out 1}}{R_2}$$

$$V_2 = -\frac{R_1}{R_2} V_{out 1}$$

Eqn. * becomes;

$$\frac{V_e - V_2}{R_3} + \frac{C d(V_e - V_2)}{dt} = \frac{V_2}{R_1} = 0$$

Taking the Laplace transform;

$$\frac{V_e(s) - V_2(s)}{R_3} + sC (V_e(s) - V_2(s)) - \frac{V_2(s)}{R_1} = 0$$

Taking initial conditions to be zero we have;

$$\frac{V_e(s)}{R_3} + sC V_e(s) = \frac{V_2(s)}{R_1} + \frac{V_2(s)}{R_3} + sC V_2(s)$$

$$V_e(s) \left(\frac{1}{R_3} + sC \right) = V_2(s) \left(\frac{1}{R_1} + \frac{1}{R_3} + sC \right)$$

Subt. V_2 , we have;

$$V_e(s) \left(\frac{1}{R_3} + sC \right) = \frac{R_2}{R_1} V_{out 1}(s) \left(\frac{1}{R_1} + \frac{1}{R_3} + sC \right)$$

CS

Scanned with CamScanner

$$V_e(s) \left(\frac{1 + R_3 s C}{R_3} \right) = - \frac{R_1}{R_2} \cdot V_{out1}(s) \left(\frac{R_3 + R_1 + R_1 R_3 s C}{R_1 R_3} \right)$$

$$V_e(s) \left(\frac{1 + R_3 s C}{R_3} \right) = - \frac{R_1}{R_2} V_{out1}(s) \frac{R_1}{R_1} \left(\frac{R_3 + R_1 + R_1 R_3 s C}{R_3} \right)$$

$$V_e(s) \left(\frac{1 + R_3 s C}{R_3} \right) = - \frac{V_{out1}(s)}{R_2} \left(\frac{R_3 + R_1 + R_1 R_3 s C}{R_3} \right)$$

$$V_e(s) (1 + R_3 s C) = - \frac{V_{out1}(s)}{R_2} (R_3 + R_1 + R_1 R_3 s C)$$

$$- \frac{V_{out1}(s)}{R_2} = \frac{V_e(s) (1 + R_3 s C)}{(R_3 + R_1 + R_1 R_3 s C)}$$

$$- V_{out1}(s) = R_2 \times \left[\frac{V_e(s) (1 + R_3 s C)}{(R_3 + R_1 + R_1 R_3 s C)} \right] \Rightarrow \frac{V_e(s) (R_2 + R_2 R_3 s C)}{R_3 + R_1 + R_1 R_3 s C}$$

Dividing the numerator & denominator by $R_1 + R_3$;

$$- V_{out1}(s) = \frac{V_e(s) (R_2 + R_2 R_3 s C)}{R_1 + R_3} \cdot \frac{R_1 + R_3}{R_1 + R_3 + \frac{R_2 R_3 s C}{R_1 + R_3}}$$

$$\frac{R_1 + R_3}{R_1 + R_3} = \frac{R_1 + R_3}{R_1 + R_3}$$

$$- V_{out1}(s) = \frac{V_e(s) \cdot (R_2 + R_2 R_3 s C)}{R_1 + R_3} \cdot \frac{1}{1 + \frac{R_2 R_3 s C}{R_1 + R_3}}$$

$$\text{If } \frac{R_2 R_3 s C}{R_1 + R_3} \ll 1$$

$$- V_{out1}(s) = \frac{V_e(s) (R_2 + R_2 R_3 s C)}{R_1 + R_3}$$

From the inverting circuit;

$$V_{out1} = -V_{out} + V_o$$

$$- (-V_{out}(s) + V_o) = \frac{V_e(s) R_2}{R_1 + R_3} + \frac{R_2 R_3 s C}{R_1 + R_3} V_o$$

$$V_{out}(s) - V_0 = \frac{R_2}{R_1 + R_3} V_e(s) + \frac{R_2}{R_1 + R_3} R_3 s C V_e(s)$$

$$V_{out}(s) = \frac{R_2}{R_1 + R_3} V_e(s) + \frac{R_2}{R_1 + R_3} R_3 s C V_e(s) + V_0$$

Taking the Inverse Laplace Transform

$$V_{out}(s) = \frac{R_2}{R_1 + R_3} V_e + \frac{R_2}{R_1 + R_3} R_3 C \frac{dV_e}{dt} + V_0$$

$$V_{out}(s) = G_p V_e + G_p \cdot G_D \frac{dV_e}{dt} + V_0$$

where; $G_p = \frac{R_2}{R_1 + R_3}$

and, $G_D = R_3 C$

