

ETIM PATRICK INI-OBONG

16/ENG041018

Electrical Electronics

EEE 553 Assignment

Solution

[A]

$$\text{Base} = 25 \text{ MVA} \quad x = 10\% = \frac{10}{100} = j0.1 \pi \quad V_{\text{base}} = 11 \text{ kV}$$

$$X_m = 25\% = \frac{25}{100} = j0.25 \pi, \quad X_s = 20\% = \frac{20}{100} = j0.2 \pi$$

$$\text{Transmission line Voltage base} = 11 \times \frac{121}{10.8} = \del{11} 123.2 \text{ kV}$$

$$\text{Motor Voltage base} = \frac{123.2 \times 10^{-3}}{121} = 11 \text{ kV}$$



The transformer line and motor reactances are converted to pu values on appropriate bases as follows

$$\text{Transformer reactance } X_T = 0.1 \times \frac{25}{30} \times \left(\frac{10.8}{11} \right)^2 = 0.0805 \text{ pu}$$

$$\text{Line reactance } X_L = \frac{100 \times 25}{(123.2)^2} = 0.164 \text{ pu}$$

$$\text{Motor reactance } X_{M1} = 0.25 \times \frac{25}{15} \left[\frac{10}{11} \right]^2 = 0.344 \text{ pu}$$
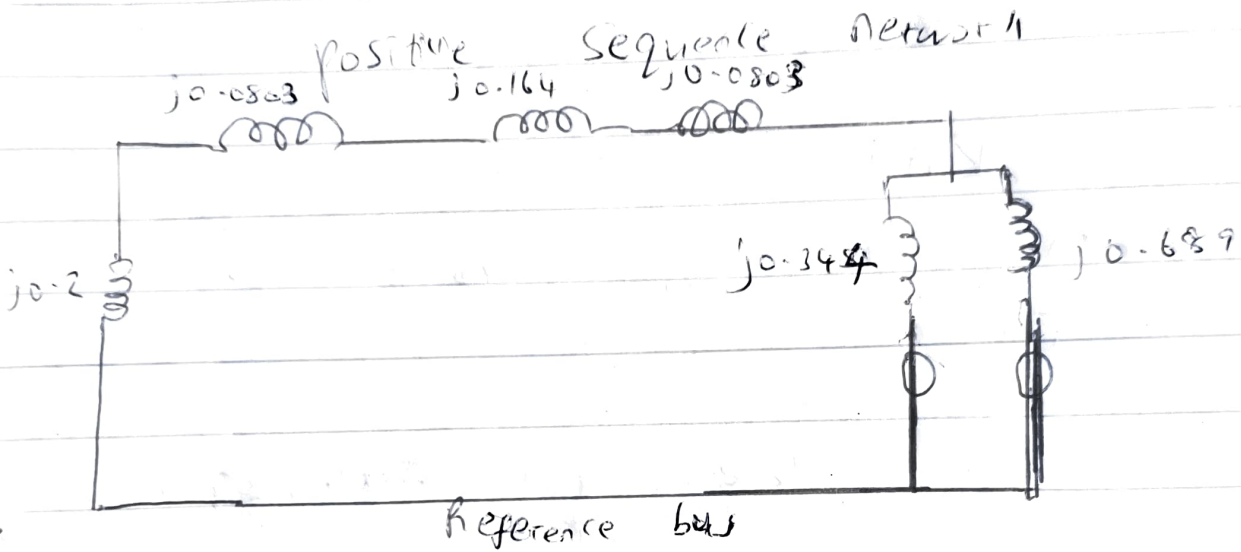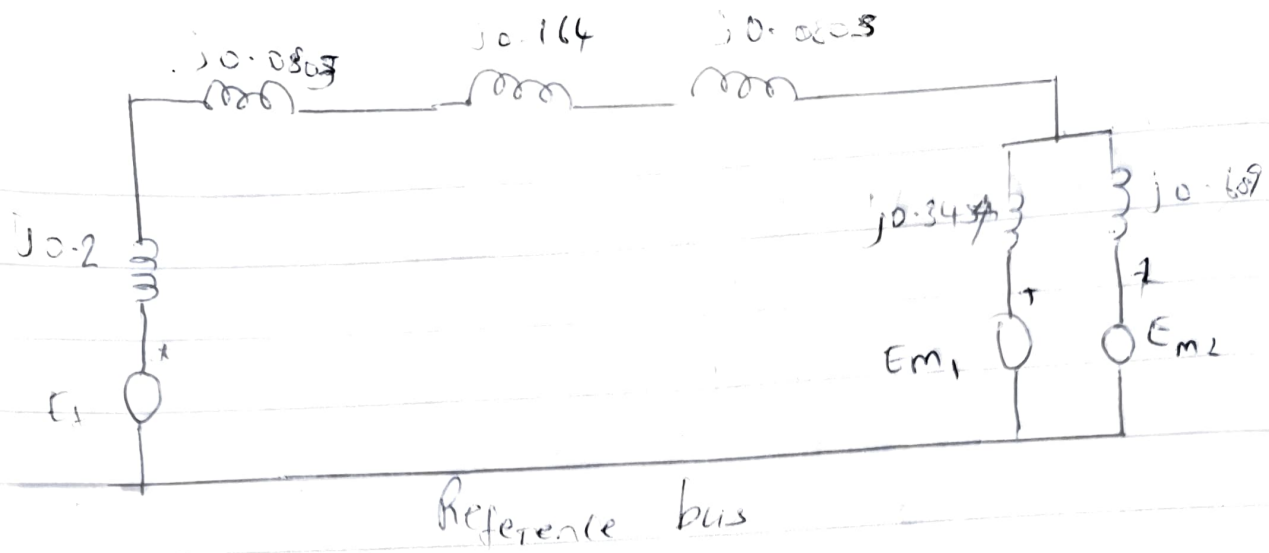
$$X_{M2} = 0.25 \times \frac{25}{7.5} \left[\frac{10}{11} \right]^2 = 0.689 \text{ pu}$$



Negative Sequence network

Zero Sequence

Zero Sequence reactance of the transmission line

$$X_{2STL} = \frac{300 \times 25}{(123.2)^2} = j0.494 \mu$$

Zero Sequence reactance of motor 1

$$X_{2SRM1} = 0.06 \times \left(\frac{25}{15}\right)^2 \times \left(\frac{10}{11}\right)^2$$

$$= 0.0826 \mu$$


Motor 2 " " " motor 2

$$X_{2SRM2} = 0.06 \times \left(\frac{25}{7.5}\right)^2 \times \left(\frac{10}{11}\right)^2 = j0.164 \mu$$

Reactance of Current limiting reactor,

$$\frac{2.5 \times 2.5}{11^2} = j0.516 \mu$$

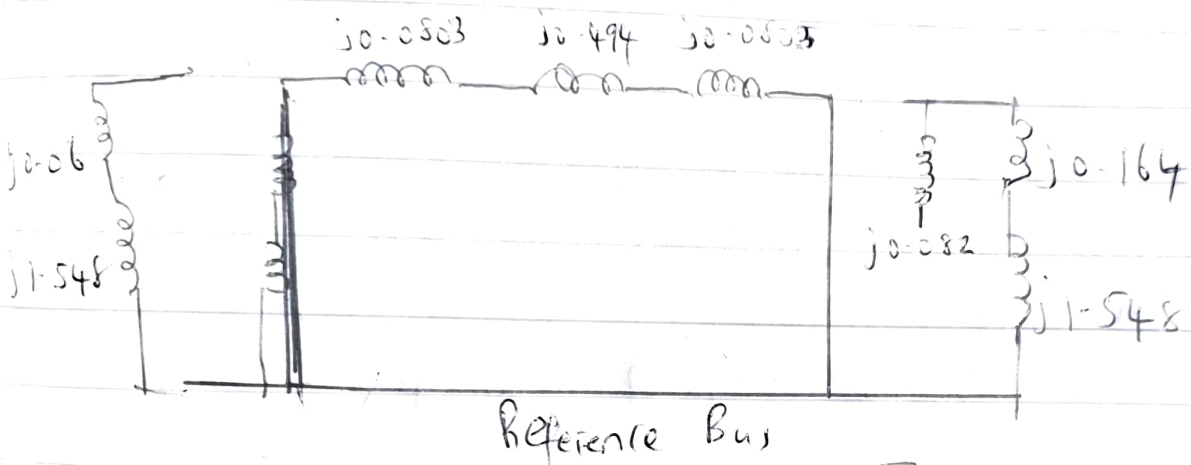Reactance of Current limiting reactor induced in zero negative network = $3 \times 0.516 = j1.548 \mu$




[B] Solution


If pre fault currents are neglected

$$E_g'' = E_{m1}'' = E_{m2}'' = V_f'' \frac{10}{11} = 0.909 \mu$$

Connection of the Sequence Network

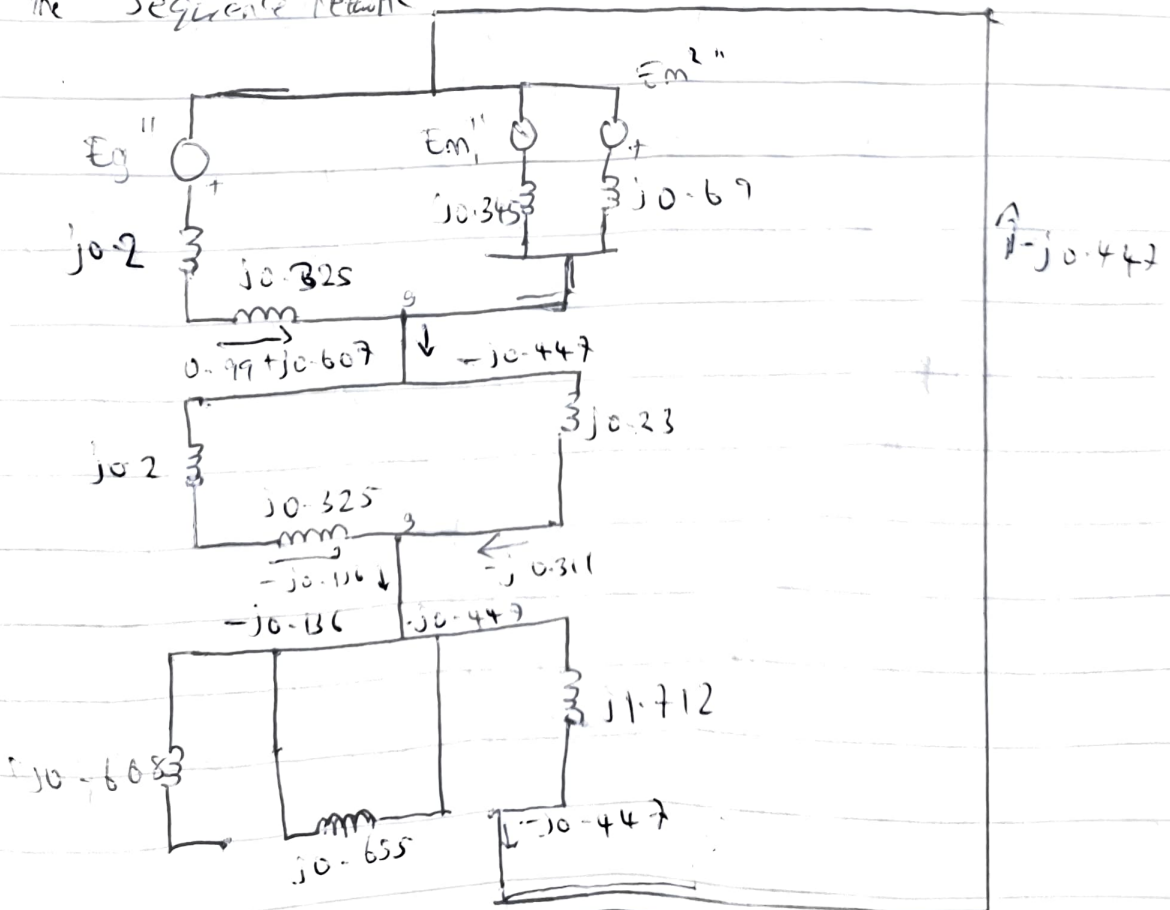

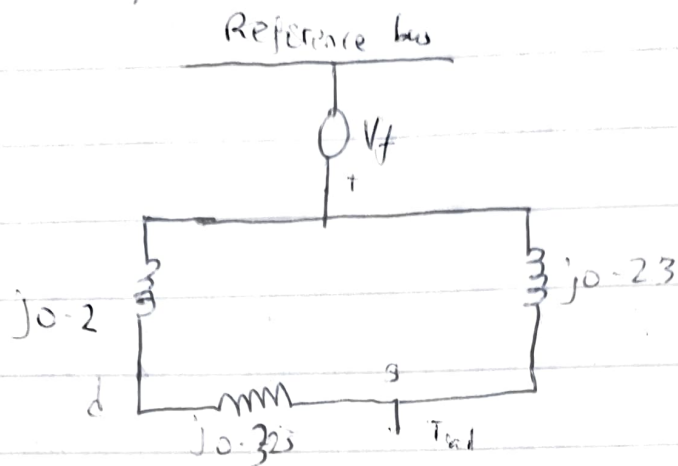The positive sequence network can be easily replaced by its Thevenin equivalent circuit shown below



New Calculations z_1

$$z_1 = \frac{j0.525 \times j0.23}{j0.755} = j0.16 \mu$$

$$z_2 = z_1 = j0.16 \mu$$

From the sequence network connection

$$I_{a1} = \frac{V_f \angle 0^\circ}{z_1 + z_2 + z_0} = \frac{0.909}{j2.032} = -j0.447 \mu$$

$$I_{a2} = I_{a0} = -I_{a1} = j0.447 \mu$$

$$\text{fault current} = 3I_{a0} = 3 \times (-j0.447) = -j1.341 \mu$$

The component of the I_{a1} flowing towards 'g' from the generator side.

$$-j0.447 \times \frac{j0.23}{j0.755} = -j0.136 \mu$$

and its component flowing towards 'g' from the motor side.

$$-j0.447 \times \frac{j0.525}{0.755} = j0.311 \mu$$

Fault Current from the generator towards G.G.M

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ \alpha^2 & \alpha & 1 \\ \alpha & \alpha^2 & 1 \end{bmatrix} \begin{bmatrix} -j0.136 \\ -j0.136 \\ 0 \end{bmatrix} = \begin{bmatrix} -j0.272 \\ -j0.136 \\ -j0.136 \end{bmatrix} \text{ pu}$$

and to G from Motor side:

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ \alpha^2 & \alpha & 1 \\ \alpha & \alpha^2 & 1 \end{bmatrix} \begin{bmatrix} -j0.311 \\ -j0.311 \\ -j0.447 \end{bmatrix} = \begin{bmatrix} -j0.069 \\ -j0.136 \\ j0.136 \end{bmatrix} \text{ pu}$$

Positive Sequence Component of the transmission line current has phase shift -90°

Negative Sequence Component of the transmission line current is shift $+90^\circ$

Positive Sequence Current = $j \times (-j0.136) = -0.136 \text{ pu}$

Negative Sequence Current = $j \times (j0.136) = 0.136 \text{ pu}$

Zero Sequence Current = 0

Line a Current on the transmission line

$$I_a = -0.136 + 0.136 + 0 = 0$$

Calculating the voltages behind the subtransient reactance to be used if the load changes are accumulated for

$$\text{Multi } \left(\frac{j15}{25 \times 0.409 \times 0.8} \right) \times 36.86^\circ = 0.825 \angle 36.86^\circ = 0.66 + j0.475 \text{ pu}$$

Motor 2; 7-5

$$\angle 36.82^\circ$$

$$25 \times 0.909 \times 0.6$$

$$= 0.4 \angle 25 \angle 36.86^\circ = 0.33 + j0.24 \text{ pu}$$

Total Current drawn by both motors = $0.99 + j0.743 \text{ pu}$

Total Voltage behind Substation bus Teacings

$$\text{Motor 1: } E_{m1}'' = 0.107 - j0.245 \times 0.825 \angle 36.86^\circ \\ = 1.08 - j0.228 = 1.104 \angle -11.92^\circ$$

$$\text{Motor 2: } E_{m2}'' = 0.909 - j0.69 \times 0.4125 \angle 36.86^\circ \\ = 1.08 - j0.228 = 1.104 \angle -11.92^\circ$$

$$\text{Generator: } E_g'' = 0.909 + j0.525 \times 1.2375 \angle 36.86^\circ \\ = 0.52 + j0.52 = 0.735 \angle 45^\circ \text{ pu}$$

Therefore the actual value of positive sequence current from the generator towards the fault is

$$0.99 + (-j0.73) - 0.436 = 0.99 - j1.054$$

The actual value of positive sequence current from the motor to the fault is

$$= 0.99 - j0.743 - j0.311 \\ = -0.99 - j1.054$$