

OKOLOCTHA KENALD UGOCHUKWU

17H0904/089

King
14/01

ELECT

POWER SYSTEMS ASSIGNMENT

$$S_{base, new} = 25 \text{ MVA}$$

$$V_{base_1, new} = 11 \text{ KV}$$

$$V_{base_2, new} = 10.8 \text{ KV}$$

$$V_{base_3, new} = 11 \text{ KV}$$

$$G_{em} = 30 \text{ MVA}, 25 \text{ MVA}, 11 \text{ KV}, 20\%$$

$$M_1 = 15 \text{ MVA}, 10 \text{ KV}, 25\%$$

$$M_2 = 7.5 \text{ MVA}, 10 \text{ KV}, 25\%$$

$$T_1 = 30 \text{ MVA}, 10.8 \text{ KV}, 10\%$$

$$T_2 = 30 \text{ MVA}, 10.8 \text{ KV}, 10\%$$

$$X_L = 100 \Omega$$

$$X_{gen, pu} = \frac{20}{100} \times \left(\frac{25}{25}\right) \times \left(\frac{11}{11}\right)^2 = j0.2 \text{ pu}$$

$$X_{m_1} = \frac{25}{100} \times \left(\frac{25}{35}\right) \times \left(\frac{10}{11}\right)^2 = j0.344 \text{ pu}$$

$$X_{m_2} = \frac{25}{100} \times \left(\frac{25}{75}\right) \times \left(\frac{10}{11}\right)^2 = j0.689 \text{ pu}$$

$$X_{T_1} = \frac{10}{100} \times \left(\frac{25}{30}\right) \times \left(\frac{10.8}{10.8}\right)^2 = j0.083 \text{ pu}$$


$$X_{T_2} = \frac{10}{100} \times \left(\frac{25}{30}\right) \times \left(\frac{10.8}{10.8}\right)^2 = j0.083 \text{ pu}$$

Base voltage for transmission line;


$$= 11 \times \frac{10.8}{11} \frac{11}{10.8} = 11.2 \text{ KV}$$

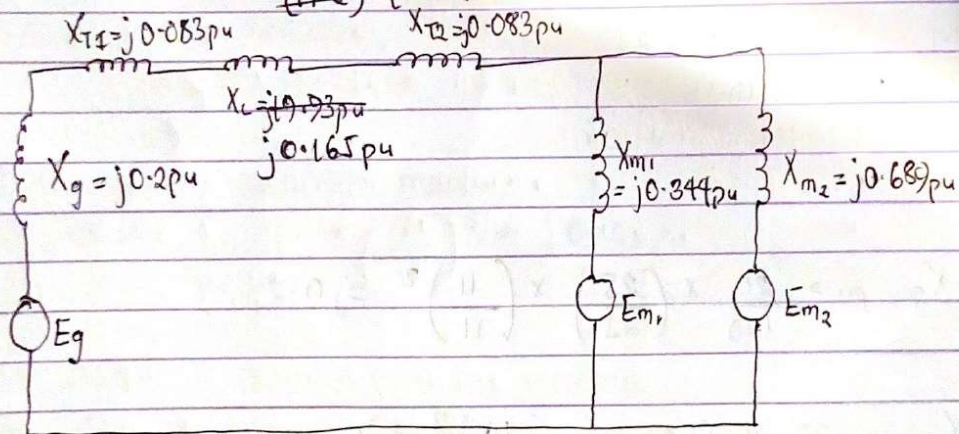123.2 KV


$$X_L \text{ pu} = 100 \times \frac{25}{(11.2)^2} = 19.93 \text{ pu}; 0.165 \text{ pu}$$



Per unit diagram of the system

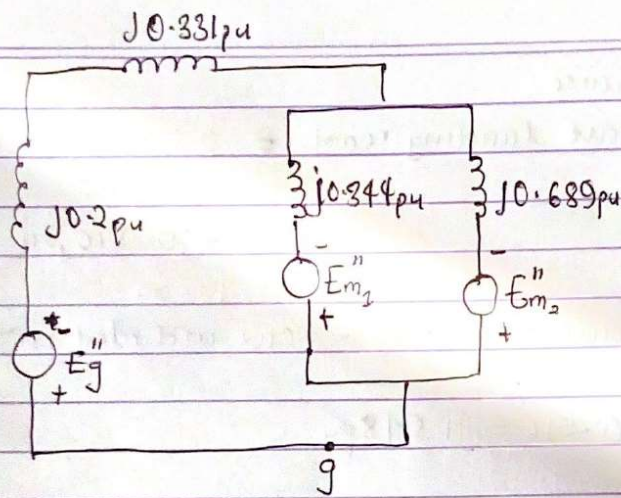

positive sequence network

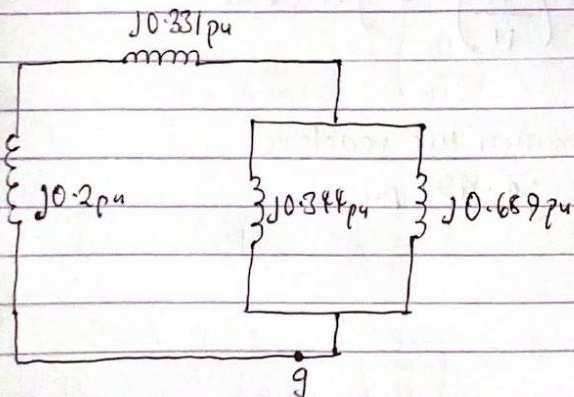

negative sequence network

for the zero sequence

$$\begin{aligned} \text{reactance of current limiting reactor} &= 2.5 \times \frac{25}{11^2} \\ &= j0.516 \text{ pu} \end{aligned}$$

reactance of the current limiting reactor included in the zero sequence network;

$$3 \times 0.516 = j1.548 \text{ pu}$$

zero sequence generator reactance

$$0.06 \times \frac{25}{25} \times \left(\frac{11}{11}\right)^2 = j0.06 \text{ pu}$$

zero sequence transmission line reactance


$$\frac{300 \times 125}{(123.2)^2} = j0.494 \text{ pu}$$

$$X_{T1} = j0.08 \text{ pu}$$

$$X_{T2} = j0.08 \text{ pu}$$


$$X_{m1} = 0.06 \times \frac{25}{15} \times \left(\frac{10}{11}\right)^2 = j0.083 \text{ pu}$$
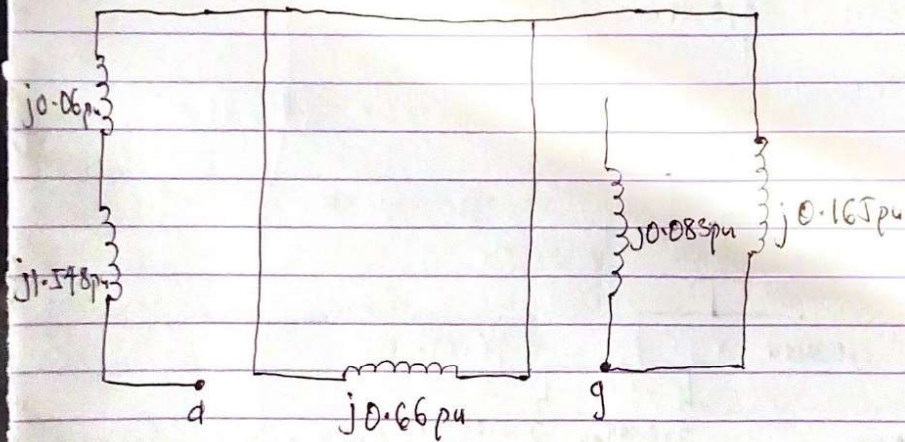
$$X_{m2} = 0.06 \times \frac{25 \times \left(\frac{10}{11}\right)^2}{7.5} = j0.165 \text{ pu}$$




Zero sequence network

CONNECTION OF THE SEQUENCE NETWORKS

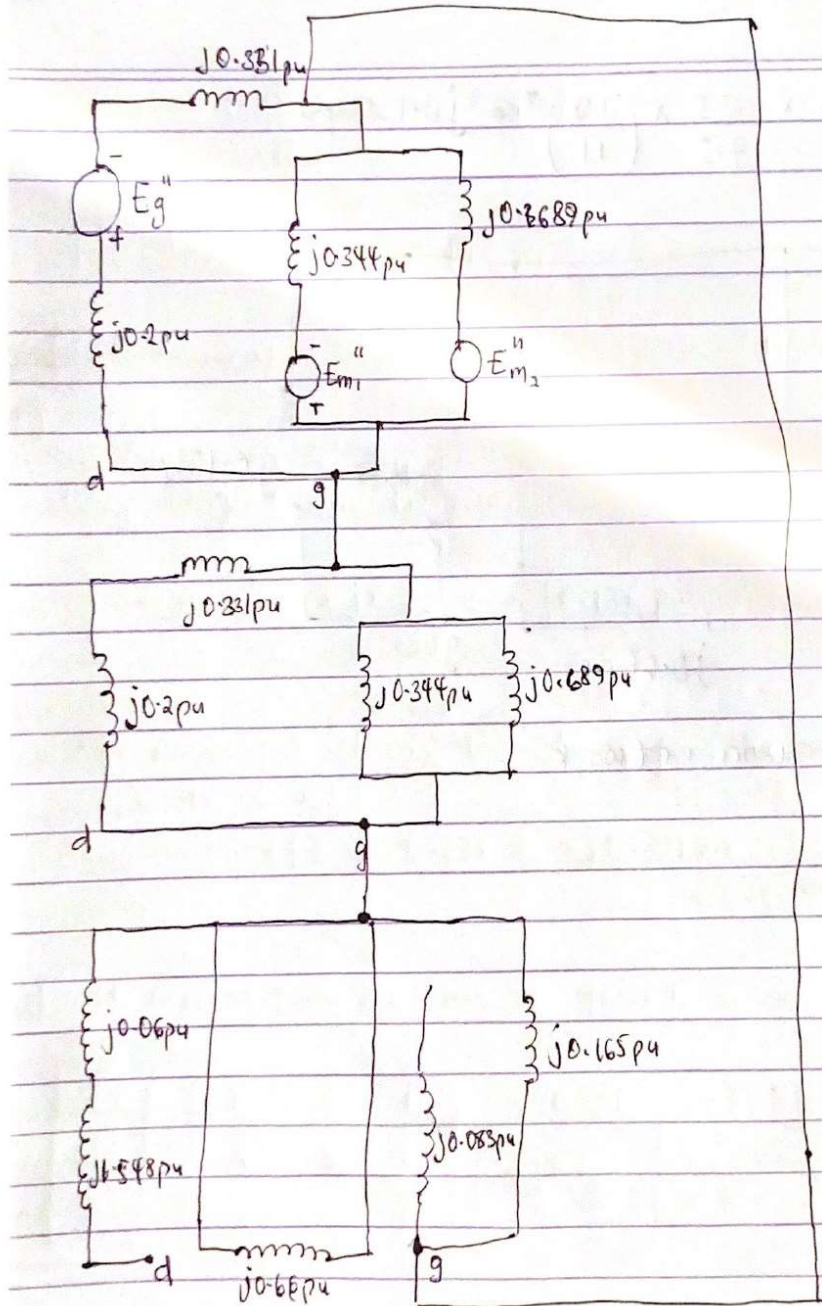

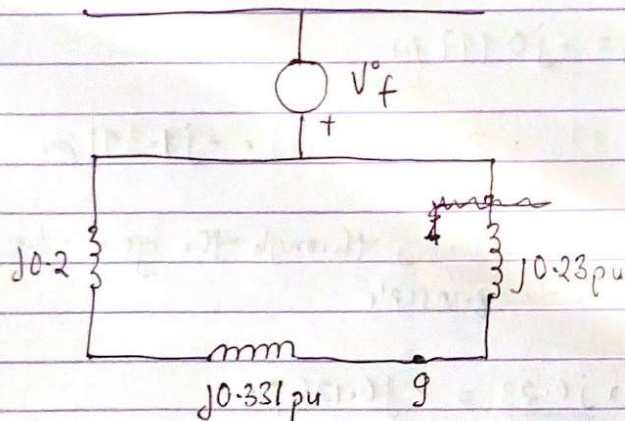b) Taking the Thevenin's equivalent of the positive sequence network



$$Z_1 = \frac{(j0.2 + j0.331) \times j0.23}{(j0.2 + j0.331) + j0.23} = j0.161 \text{ pu}$$

$$Z_1 = Z_2 = j0.161 \text{ pu}$$

from the sequence connection

$$I_{a1} = \frac{V^0_f}{Z_1 + Z_2 + Z_0}$$

$$V^0_f = E_g^0 = E_m^0 = -E_m^0 = \frac{10}{11} = 0.909 \text{ pu}$$

$$\therefore I_{a1} = \frac{0.909}{j2.032} = -j0.447 \text{ pu}$$

$$I_{a2} = I_{a0} = I_{a1} = -j0.447 \text{ pu}$$

$$\text{fault current} = 3I_{a0} = 3 \times (-j0.447) = -j1.341 \text{ pu}$$

a) The component of I_{a1} flowing through the generator.
Using current divider principle

$$-j0.447 \times \frac{j0.23}{j0.755} = -j0.136 \text{ pu}$$

- Its component flowing towards g from the motor side
using KCL

$$-j0.447 + j0.136 = -j0.311 \text{ pu}$$

Fault current from the generator towards g are;

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ \alpha^2 & \alpha & 1 \\ \alpha & \alpha^2 & 1 \end{bmatrix} \begin{bmatrix} -j0.136 \\ -j0.136 \\ 0 \end{bmatrix} = \begin{bmatrix} -j0.272 \\ -j0.136 \\ +j0.136 \end{bmatrix} \text{ pu}$$

Fault current from the motor towards g

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ \alpha^2 & \alpha & 1 \\ \alpha & \alpha^2 & 1 \end{bmatrix} \begin{bmatrix} -j0.311 \\ -j0.311 \\ -j0.477 \end{bmatrix} = \begin{bmatrix} -j1.069 \\ -j0.136 \\ -j0.136 \end{bmatrix} \text{ pu}$$

Positive and negative sequence are shifted $\pm 90^\circ$ & -90° respectively

$$\text{Positive sequence current} = -j \times (-j0.136) = -0.136 \text{ pu}$$

$$\text{negative sequence current} = j \times (-j0.136) = 0.136 \text{ pu}$$

$$\text{zero sequence current} = 0$$

\therefore Line a current on the transmission line

$$= -0.136 + 0.136 + 0 = 0$$