

## MESH, NODAL AND LOOP ANALYSIS


In this section, we will apply our knowledge and understanding of Ohm's and Kirchoff's laws — the fundamental laws of circuit theory — to develop mesh and nodal circuit analysis. The nodal analysis is based on systematic application of Kirchoff's current law (KCL), while mesh analysis is based on systematic application of Kirchoff's voltage law (KVL). Virtually any linear circuit can be analysed using these two techniques.

### NODAL ANALYSIS

This technique involves using node voltages as the circuit variables. Steps here include:

- (i) Selecting a node as the reference node (usually  $V=0$  ground) and assigning  $V_1, V_2, \dots, V_{n-1}$  to the remaining nodes.
- (ii) Applying KCL to each  $n-1$  nonreference nodes; then using Ohm's law to express the branch currents in terms of node voltages.
- (iii) Solve the equations simultaneously to obtain the unknown node voltages.

Illustration

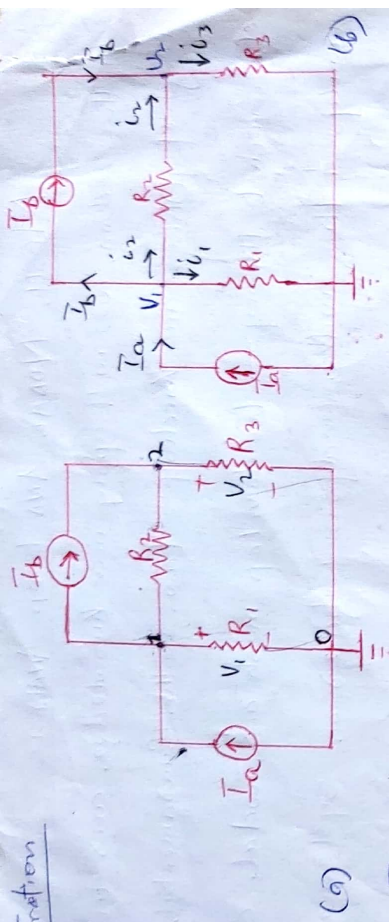

Figs: A Typical nodal circuit analysis

From (a) the ground is the reference node. i.e.  $V = 0$ .

At node 1, applying KCL:

$$I_a = i_1 + i_2$$

where  $i_1 = \frac{V_1 - 0}{R_1}$ , and  $i_2 = \frac{V_1 - V_2}{R_2}$

$$\Rightarrow I_a = I_b + \frac{V_1}{R} + \frac{V_1 - V_2}{R_2} \quad \text{--- (i)}$$

At node 2, applying KCL:

$$i_2 + I_b = i_3$$


where  $i_2 = \frac{V_1 - V_2}{R_2}$ , and  $i_3 = \frac{V_2}{R_3}$

$$\Rightarrow \frac{V_1 - V_2}{R_2} + I_b = \frac{V_2}{R_3} \quad \text{--- (ii)}$$

Equations (i) and (ii) can then be solved simultaneously or using elimination or matrix inversion or Cramer's rule.

Exam

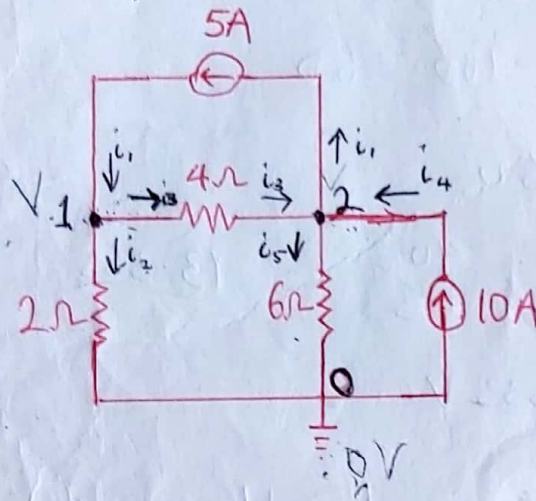Examples: (i) Calculate the node voltages in the circuit shown below. Also, what current flows through the three resistors?



Solution:

Applying KCL at node 1:

$$i_1 = i_2 + i_3 \Rightarrow 5 = \frac{V_1 - V_2}{4} + \frac{V_1 - 0}{2}$$

$$\Rightarrow 20 = V_1 - V_2 + 2V_1$$

$$\Rightarrow 3V_1 - V_2 = 20 \quad \text{--- (i)}$$

Applying KCL at node 2:

$$i_3 + i_4 = i_1 + i_5$$

$$\Rightarrow \frac{V_1 - V_2}{4} + 10 = 5 + \frac{V_2 - 0}{6}$$

$$\Rightarrow 13(V_1 - V_2) + 120 = 60 + 2V_2$$

$$\Rightarrow -3V_1 + 5V_2 = 60 \quad \text{--- (ii)}$$

Using elimination technique:

$$\text{from (i), } V_2 = 3V_1 - 20 \quad \text{--- (iii)}$$

Substituting eq. (iii) into eq. (ii):

$$\Rightarrow -3V_1 + 5(3V_1 - 20) = 60$$

$$-3V_1 + 15V_1 - 100 = 60$$

$$12V_1 = 160$$

$$V_1 = \frac{160}{12} = \frac{40}{3} = 13.333$$

$$V_1 = \underline{\underline{13.333 \text{ V}}}$$

Substituting  $V_1 = 13.333$  for  $V_1$  in eq. (i):

$$\Rightarrow 3(13.333) - V_2 = 20$$

$$40 - V_2 = 20$$

$$V_2 = 40 - 20 = 20$$

$$V_2 = \underline{\underline{20 \text{ V}}}$$

For currents flowing through  $2\Omega$ ,  $4\Omega$ , &  $6\Omega$ -resistors:


$$\underline{2\Omega} : i_2 = \frac{V_1}{2} = \frac{13.333}{2} = \underline{\underline{6.6667 \text{ A}}}$$

$$\underline{4\Omega} : i_3 = \frac{V_1 - V_2}{4} = \frac{13.333 - 20}{4} = \underline{\underline{-1.6668 \text{ A}}}$$

$$\underline{6\Omega} : i_5 = \frac{V_2}{6} = \frac{20}{6} = \underline{\underline{3.333 \text{ A}}}$$

3/ The negative orientation of  $i_3$  implies that  $i_3$  flows in the direction opposite assumed direction.

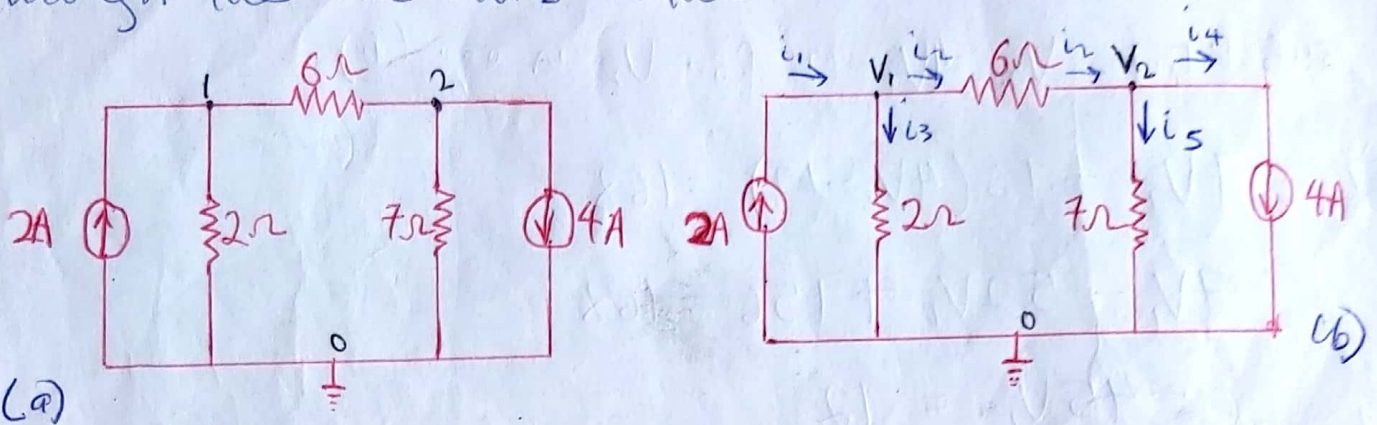(ii) Obtain the node voltages and the currents flowing through the resistors in the circuit below.



Figs (a) & (b) For example above

Solution:

From (b),

Applying KCL to node 1:

$$i_1 = i_2 + i_3 \Rightarrow 2 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$\Rightarrow 12 = V_1 - V_2 + 3V_1$$

$$4V_1 - V_2 = 12 \quad 4V_1 - V_2 = 12 \quad \text{--- (i)}$$

Applying KCL to node 2:

$$i_2 = i_4 + i_5$$

$$\Rightarrow \frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$\Rightarrow 7(V_1 - V_2) = 168 + 6V_2$$

$$7V_1 - 13V_2 = 168 \quad \text{--- (ii)}$$

From eq (i),  $V_2 = 4V_1 - 12$

Substitute  $V_2 = 4V_1 - 12$  for  $V_2$  in eq. (ii)

$$\Rightarrow 7V_1 - 13(4V_1 - 12) = 168$$

$$7V_1 - 52V_1 + 156 = 168$$

$$-45V_1 = 12$$

$$V_1 = \frac{-12}{45} = \underline{\underline{-\frac{4}{15} \text{ V}}} = \underline{\underline{-0.2667 \text{ V}}}$$

Substituting  $-\frac{4}{15}$  for  $V_1$  in eq. (i)

$$4\left(-\frac{4}{15}\right) - V_2 = 12$$

$$\frac{-16}{15} - V_2 = 12$$

$$V_2 = \frac{-16}{15} - \frac{12}{1} = \frac{-16 - 180}{15} = \underline{\underline{-\frac{196}{15}}}$$


$$V_2 = \underline{\underline{-13.0667 \text{ V}}}$$

$$i_3 = \frac{V_1}{2} = \frac{-0.2667}{2} = \underline{\underline{-0.13335 \text{ A}}}$$

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-0.2667 + 13.0667}{6} = \underline{\underline{2.1333 \text{ A}}}$$

$$i_5 = \frac{V_2}{7} = \frac{-13.0667}{7} = \underline{\underline{-1.8667 \text{ A}}}$$


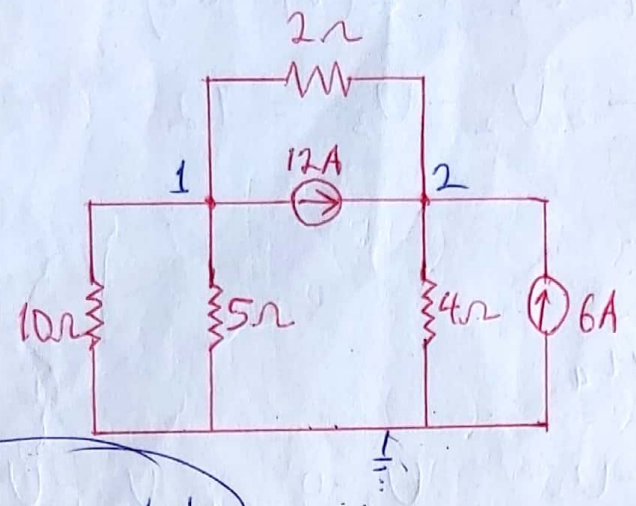
ii) Find the voltages at nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below.



Class example

iii) Obtain  $V_1$  and  $V_2$  and the currents through the resistors for the circuit in example (ii) if the 2A current source was replaced by a 1A current source.

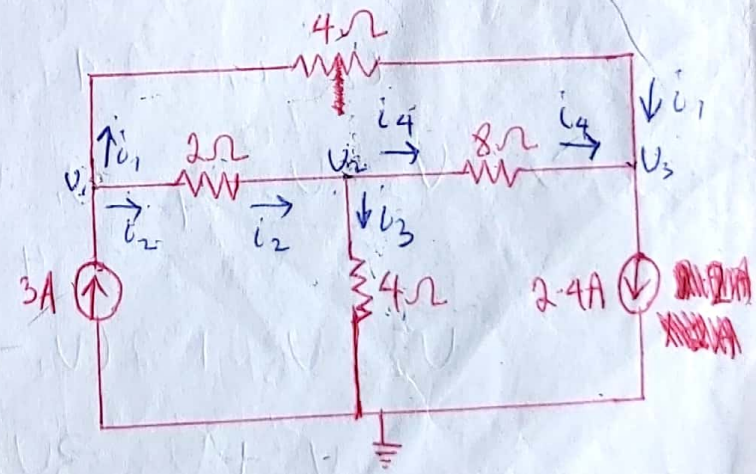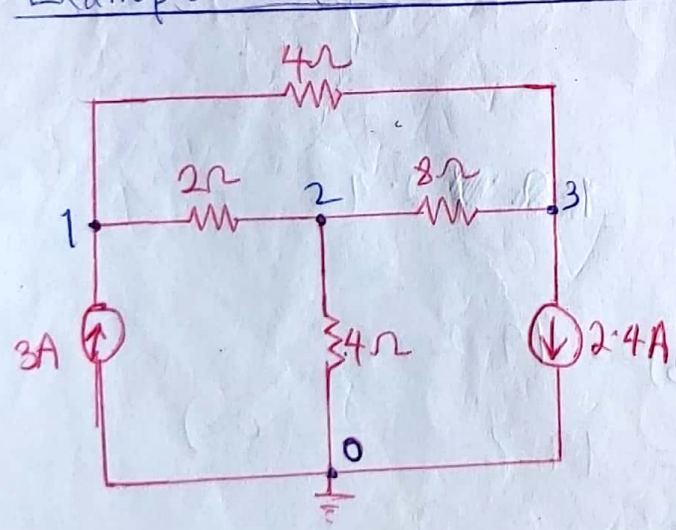Example: Circuit with 3 reference nodes (Test)



Determine the voltages at the nodes 1, 2 and 3.

At node 1,

KCL:

$$3 = i_1 + i_2 \Rightarrow 3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2}$$

$$\Rightarrow 12 = V_1 - V_3 + 2(V_1 - V_2)$$

$$3V_1 - 2V_2 - V_3 = 12 \quad \text{--- (i)}$$

At node 2, KCL:

$$i_2 = i_3 + i_4$$

$$\Rightarrow \frac{V_1 - V_2}{2} = \frac{V_2 - 0}{4} + \frac{V_2 - V_3}{8}$$

$$\Rightarrow 4(V_1 - V_2) = 2V_2 + V_2 - V_3$$

$$4V_1 - 7V_2 + V_3 = 0 \quad \text{--- (ii)}$$

At node 3, KCL:

$$i_4 + i_1 = 2.4$$

$$\Rightarrow \frac{V_2 - V_3}{8} + \frac{V_1 - V_3}{4} = 2.4$$

$$V_2 - V_3 + 2(V_1 - V_3) = 19.2$$

$$2V_1 + V_2 - 3V_3 = 19.2 \quad \text{--- (iii)}$$



5/ Hence, we have three equations with three unknowns.

Using Cramer's rule:

$$3V_1 - 2V_2 - V_3 = 12 \quad \text{--- (i)}$$

$$4V_1 - 7V_2 + V_3 = 0 \quad \text{--- (ii)}$$

$$2V_1 + V_2 - 3V_3 = 19.2 \quad \text{--- (iii)}$$

In matrix representation:

$$\begin{bmatrix} 3 & -2 & -1 \\ 4 & -7 & 1 \\ 2 & 1 & -3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 19.2 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}; \quad V_2 = \frac{\Delta_2}{\Delta}; \quad V_3 = \frac{\Delta_3}{\Delta}$$

where  $\Delta = \begin{vmatrix} 3 & -2 & -1 \\ 4 & -7 & 1 \\ 2 & 1 & -3 \end{vmatrix} = 3 \begin{vmatrix} 21 & -1 \\ 21 & 1 \end{vmatrix} - (-2) \begin{vmatrix} 21 & -2 \\ 2 & -2 \end{vmatrix} + (-1) \begin{vmatrix} 4 & 14 \\ 2 & 1 \end{vmatrix}$

$$= 3(+20) + 2(-14) - 1(18)$$

$$= 60 - 28 - 18 = \underline{\underline{14}}$$

$$\Delta_1 = \begin{vmatrix} 12 & -2 & -1 \\ 0 & -7 & 1 \\ 19.2 & 1 & -3 \end{vmatrix} = 12 \begin{vmatrix} 20 & -1 \\ 21 & 1 \end{vmatrix} - 0 + 19.2 \begin{vmatrix} 2 & -2 \\ 2 & -7 \end{vmatrix}$$

$$= 240 - 172.8 = \underline{\underline{67.2}}$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{67.2}{14} = \underline{\underline{4.8 \text{ V}}}$$

~~$$\text{for } U_2, \Delta_2 = \begin{vmatrix} 3 & 12 & -1 \\ +4 & 0 & 1 \\ 2 & 19.2 & -3 \end{vmatrix} = 12(-12-2) + 0 + 19.2(3+4)$$

$$= -14 + 19.2(3+4)$$

$$= 120 + 117.6$$~~

for  $U_2$ :

from eq. (i),  $3U_1 - 2U_2 - U_3 = 12$  — (iv)

u u (ii),  $4U_1 - 7U_2 + U_3 = 0$  — (v)

where  $U_1 = 4.8$

$$\Rightarrow 3(4.8) - 2U_2 - U_3 = 12 \quad \text{--- (iv)}$$

$$4(4.8) - 7U_2 + U_3 = 0 \quad \text{--- (v)}$$

$$14.4 - 2U_2 - U_3 = 12$$

$$U_3 = 2.4 - 2U_2$$

substitute  $2.4 - 2U_2$  for  $U_3$  in eq. (v)

$$\Rightarrow 19.2 - 7U_2 + 2.4 - 2U_2 = 0$$

$$\Rightarrow 21.6 - 9U_2 = 0$$

$$U_2 = \frac{21.6}{9} = \underline{\underline{2.4V}}$$

for  $U_3$ :

from eq. (i),

$$4U_1 - 7U_2 + U_3 = 0$$


$$\Rightarrow 19.2 - 16.8 = -U_3$$

$$U_3 = \underline{\underline{-2.4V}}$$

6/ Hence  $U_1 = 4.8V$ ;  $U_2 = 2.4V$ ,  $U_3 = -2.4V$

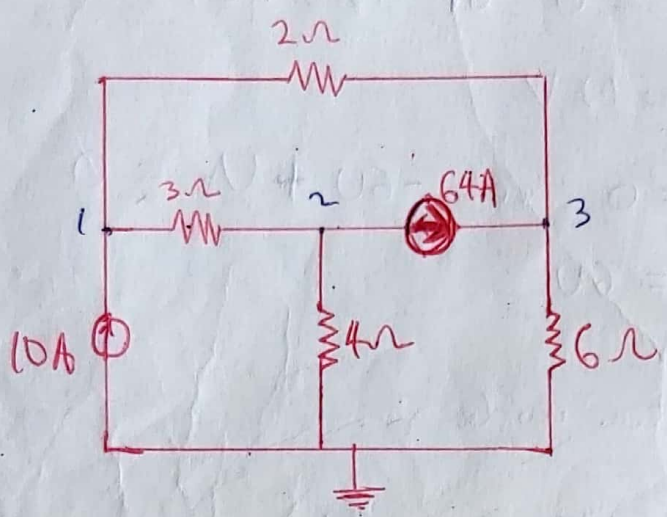Exercise: ~~Find~~ Classwork ✓

Find the voltages at nodes 1, 2 and 3 in the circuit below.




Ans:  $U_1 = 80V$   
 $U_2 = 64V$   
 $U_3 = 156V$

### Circuits with Independent Voltage Sources

So far, we have considered circuits with independent current sources; we now consider some examples of circuits with independent voltage sources.

#### Examples:

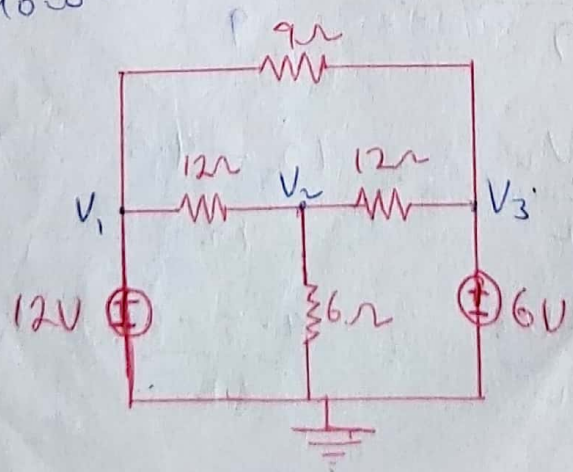(i) Determine the node voltages and the branch currents in the circuit below.



## Solution

First, the 12V and 6V independent voltage sources connected between  $V_1$  and ground and  $V_3$  and ground respectively simply means:

$$V_1 - 12V = 0 \quad \text{or} \quad -12V + V_1 = 0$$

$$\Rightarrow V_1 = 12V$$

and

$$V_3 - 6V = 0 \quad \text{or} \quad -6V + V_3 = 0$$

$$\Rightarrow V_3 = 6V$$

Applying KCL to the node 2:

$$\frac{V_1 - V_2}{12} = \frac{V_2 - V_3}{12} + \frac{V_2}{6}$$

$$\Rightarrow V_1 - V_2 = V_2 - V_3 + 2V_2 \equiv 12 - V_2 = V_2 - 6 + 2V_2$$

$$\Rightarrow 18 = V_2 + 2V_2 + V_2 \equiv 18 = 4V_2$$

$$V_2 = 18/4 = \underline{\underline{4.5V}}$$

Currents:


$$I_{9\Omega} = \frac{V_1 - V_3}{9} = \frac{12 - 6}{9} = \underline{\underline{0.667A}}$$

$$I_{12\Omega} = \frac{V_1 - V_2}{12} = \frac{12 - 4.5}{12} = \frac{7.5}{12} = \underline{\underline{0.625A}}$$

$$I_{12\Omega} = \frac{V_2 - V_3}{12} = \frac{4.5 - 6}{12} = \frac{-1.5}{12} = \underline{\underline{-0.125A}}$$

$$I_6 = \frac{V_2}{6} = \frac{4.5}{6} = 0.75 \text{ A}$$

Exercise

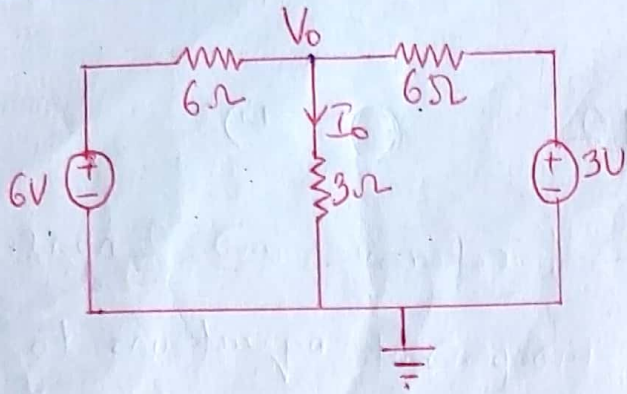


Find the current  $I_0$  in the network using nodal analysis.

Solution

At node  $V_0$ ,
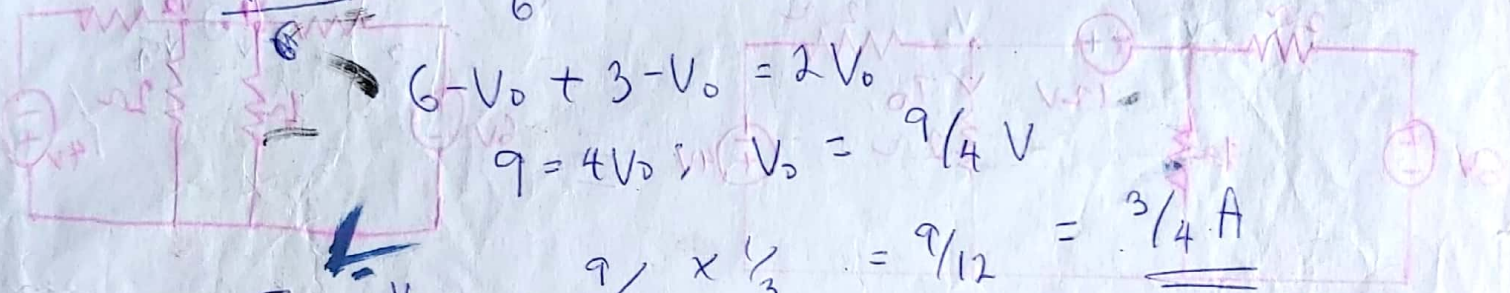
$$\frac{6 - V_0}{6} + \frac{3 - V_0}{6} = \frac{V_0}{3}$$




$$6 - V_0 + 3 - V_0 = 2V_0$$

$$9 = 4V_0 \Rightarrow V_0 = 9/4 \text{ V}$$

$$I_0 = \frac{V_0}{3} = \frac{9/4}{3} = 9/12 = 3/4 \text{ A}$$

A voltage source between two nodes (supernode)

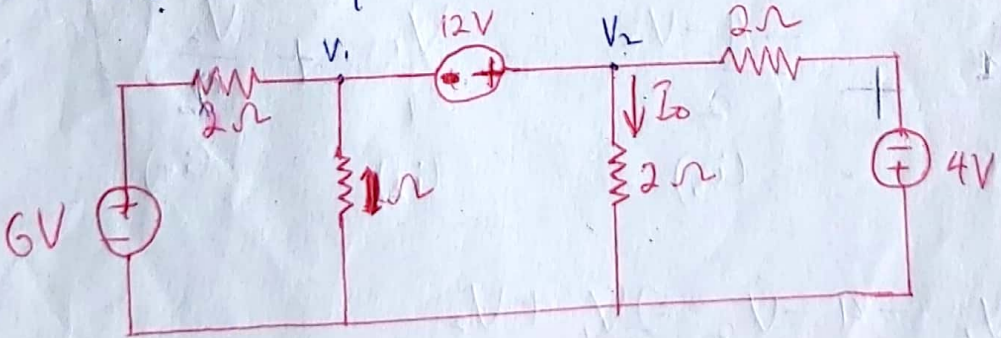Use nodal analysis to find  $I_0$  in the network below.




~~At node V1~~  
~~At node V2~~

In this example, we have an independent voltage source (12V) connected between two non-reference nodes. The difference in potential between the two nodes is constrained by the voltage source, and hence,

$$V_2 - V_1 = 12 \quad \text{--- (i)}$$

Since we have 3 nodes - 1 reference and 2 non-reference, we thus require two linearly independent equations to solve the problem. The above equation is one of these.

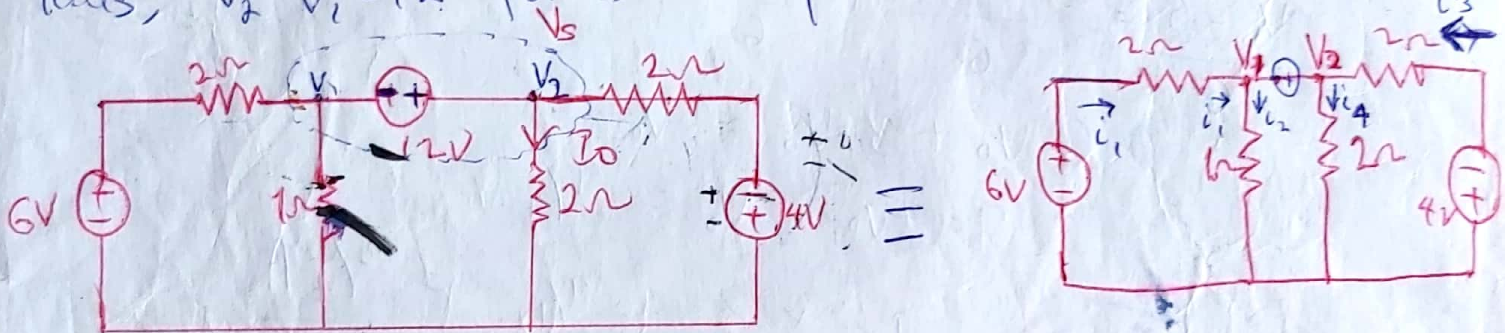Thus,  $V_2 - V_1 = 12$  forms a supernode:



Applying KCL at the supernode:

$$i_3 + i_1 = i_2 + i_4$$

$$\Rightarrow \frac{6 - V_1}{2} + \frac{-4 - V_2}{2} = \frac{V_1}{1} + \frac{V_2}{2}$$

$$\Rightarrow 6 - V_1 - 4 - V_2 = 2V_1 + V_2$$

$$2 = 3V_1 + 2V_2 \quad \text{--- (ii)}$$

from (i),  $V_2 = 12 + V_1$

substituting  $12 + V_1$  for  $V_2$  in eq. (ii)

$$\Rightarrow 2 = 3V_1 + 2(12 + V_1)$$

$$2 = 3V_1 + 24 + 2V_1 ; 5V_1 = -22$$

$$V_1 = -22/5 \text{ V}$$


hence,  $V_2 - (-22/5) = 12$

$$V_2 = \frac{12 + 22}{5} = \frac{60 + 22}{5} = \frac{38}{5} \text{ V}$$

and  $I_0 = V_2 / 2 = \frac{38}{5} \div 2 = \frac{38}{5} \times \frac{1}{2}$


$$I_0 = \frac{38}{10} = \underline{\underline{3.8 \text{ A}}}$$

Class work

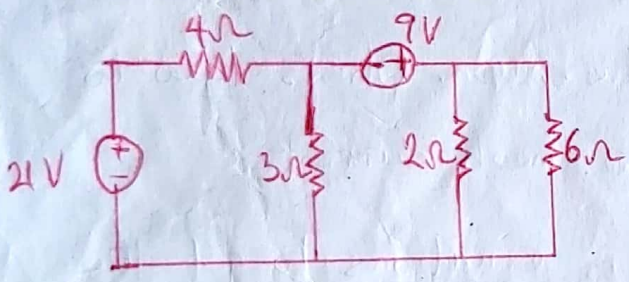

Find the current through the 3Ω and 2Ω resistors -

Ans: -0.2A, 4.2A

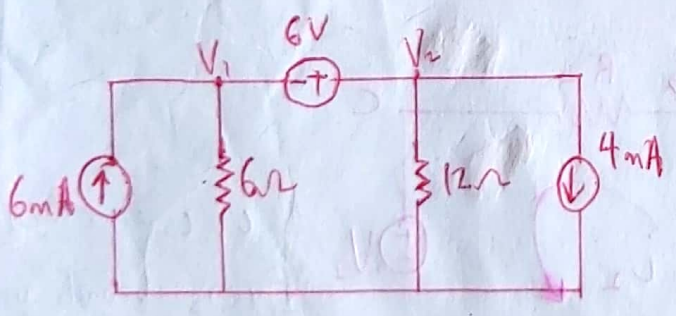

find the node voltages and the currents through the 6Ω and 12Ω resistors -