

# MESH ANALYSIS


This procedure involves analysing circuits using mesh currents as the circuit variables. This reduces the number of simultaneous equations that need to be solved.

A mesh is a loop that contains no other loop within it; a loop is a closed path with no node passed more than once.

Mesh analysis applies KVL to find unknown currents; it is applicable only to planar circuits - circuits that can be drawn with no branches crossing one another.

To determine mesh currents in mesh analysis:

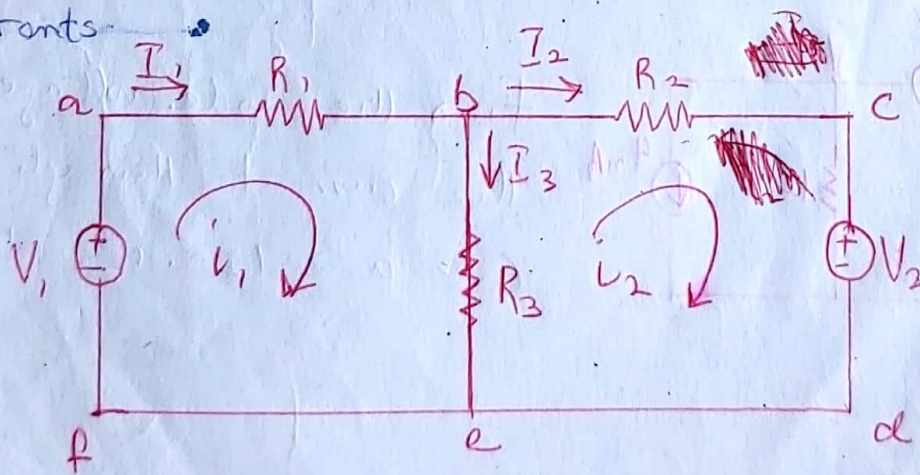- Assign mesh currents  $i_1, i_2, i_3, \dots, i_n$  to the  $n$  meshes.
- Apply KVL to each of the  $n$  meshes; use Ohm's law to express the voltages in terms of the mesh currents.
- Solve the resulting  $n$  simultaneous equations to get the mesh currents.



$i_1, i_2 =$  mesh currents

$I_1, I_2, I_3 =$  branch currents

$$I_1 = i_1$$

$$I_2 = i_2$$

$$I_3 = i_1 - i_2$$

abefa and bcdeb = meshes

abcdefa  $\neq$  mesh



Apply KVL to both meshes:

$$V_1 = i_1 R_1 + (i_1 - i_2) R_3 \quad (1)$$

$$V_2 = i_1 (R_1 + R_3) - i_2 R_3$$

and

$$V_2 + i_2 R_2 + (i_2 - i_1) R_3 = 0 \quad \text{--- (2)}$$

$$V_2 = i_1 R_3 - i_2 (R_2 + R_3)$$

This can then be solved simultaneously or elimination or cramer's rule -

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_1 + R_3 & -R_3 \\ R_3 & -(R_2 + R_3) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

### Illustration

Find the branch currents  $I_1$ ,  $I_2$  and  $I_3$  using mesh analysis in the circuit below.

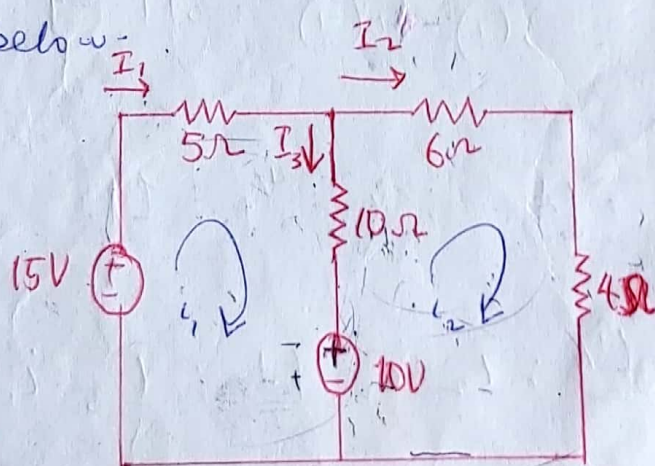


Fig. for illustration above

### Solution

Mesh 1:

$$15 = i_1 \cdot 5 + (i_1 - i_2) 10 \quad \text{--- (1)}$$

$$\Rightarrow 5 = 3i_1 - 10i_2$$

$$1 = 3i_1 - 2i_2 \quad \text{--- (2)}$$

15 - 10 =

Mesh 2:

$$10 = (i_2 - i_1)10 + 6i_2 + 4i_2$$

$$\Rightarrow 10 = 20i_2 - 10i_1$$

$$1 = 2i_2 - i_1 \quad \text{--- (ii)}$$

Using Cramer's rule:

$$\begin{bmatrix} 3 & -2 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$i_1 = \frac{\Delta_1}{\Delta} \quad ; \quad i_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta = 3(2) - (-2)(-1) = 6 - 2 = 4$$

$$\Delta_1 = \begin{vmatrix} 1 & -2 \\ 1 & 2 \end{vmatrix} = 1(2) - 1(-2) = 2 + 2 = 4$$

$$\Delta_2 = \begin{vmatrix} 3 & 1 \\ -1 & 1 \end{vmatrix} = 3(1) - (-1)(-1) = 3 - 1 = 2$$

hence  $i_1 = \frac{4}{4} = 1A$  ;  $i_2 = \frac{2}{4} = 0.5A$

and  $I_1 = i_1 = 1A$  ;  $I_2 = i_2 = 0.5A$  ;  $I_3 = i_1 - i_2 = 0.5A$

or elimination:

$$1 = 3i_1 - 2i_2 - 10i_1$$

$$1 = 2i_2 - 10i_1 - 10$$

from (ii)  $i_1 = 2i_2 - 1$

put this into (i)

$$\Rightarrow 1 = 3(2i_2 - 1) - 2i_2 - 10$$

$$1 = 6i_2 - 3 - 2i_2 - 10$$

$$\Rightarrow 4 = 4i_2$$

$$i_2 = \frac{4}{4} = 1A$$

and from  $i_1 = 2i_2 - 1$

$$\Rightarrow i_1 = 2(1) - 1 = 1$$

$$i_2 = 1$$

$$i_2 = \frac{4}{4} = 1A$$

$$I_1 = i_1 = 1A$$


$$I_2 = i_2 = 1A$$

$$I_3 = 1 - 1 = 0$$




Classwork Practice Questions

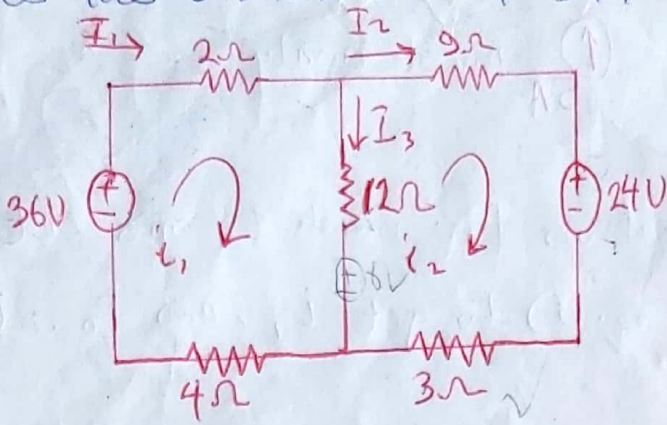(i) Calculate the branch currents  $I_1$ ,  $I_2$  and  $I_3$  in the circuit below.




(ii)

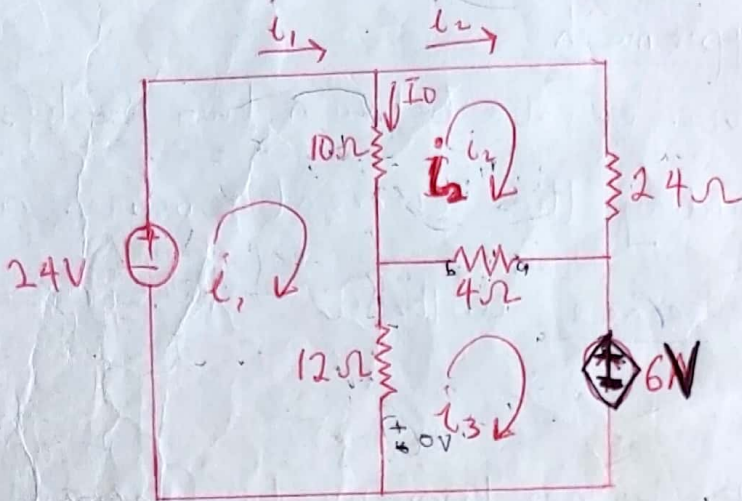

Ans:  
 $i_1 = 2.25A$   
 $i_2 = 0.75A$   
 $i_3 = 1.5A$   
 $I_0 = 1.5A$


Use mesh analysis to obtain the current  $I_0$  in the circuit above.

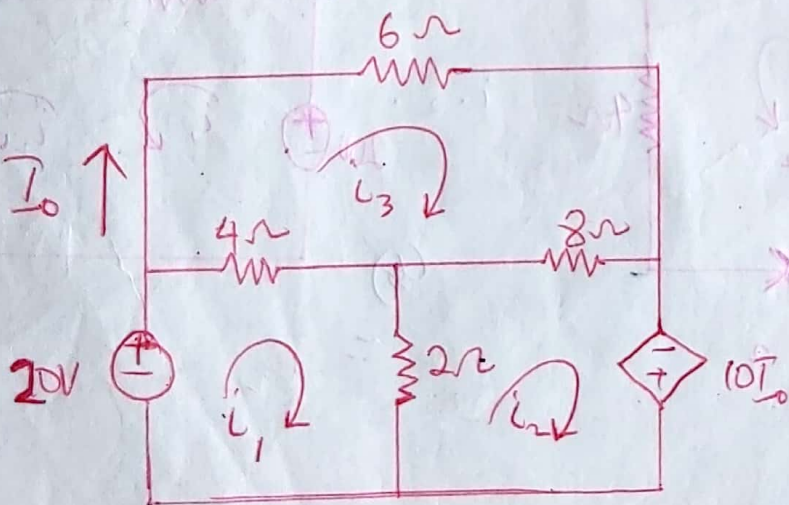(iii) Use mesh analysis to obtain  $I_0$  in the circuit below.



Ans:  $-5A$



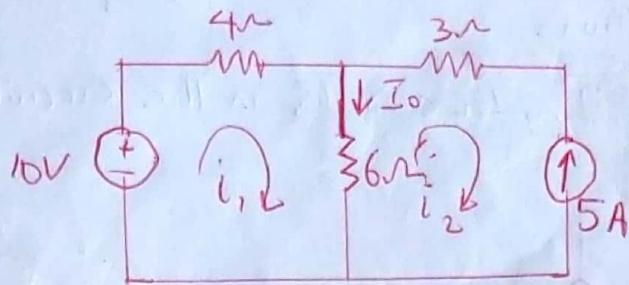

Find  $I_0$  in this circuit, using mesh analysis.



Hint: Write a mesh equation for mesh 1, and set  $i_2 = -5A$ .

Substitute this into eq. (1) to get  $i_1$ , and  $I_0 = i_1 - i_2$
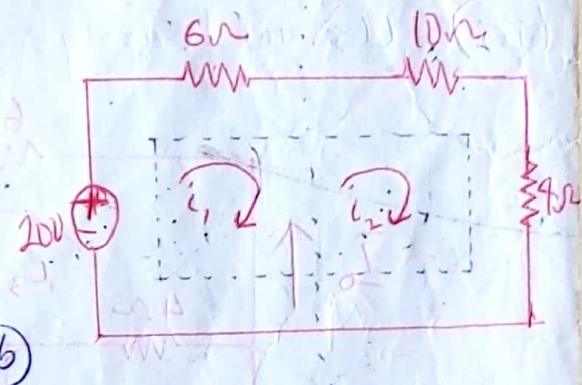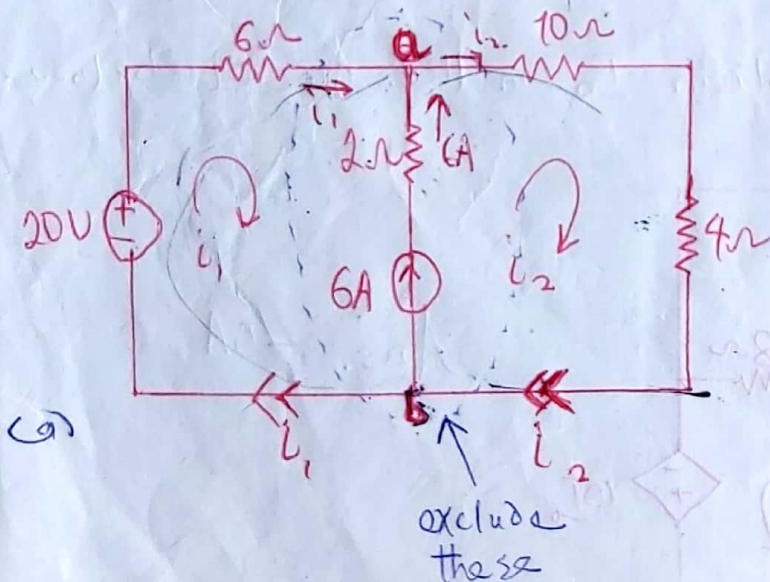
### Special Case: Supermesh

When a current source exists between two meshes, this is approached by excluding the current source and any element(s) connected in series with it — this results in a supermesh.

A supermesh exists when two meshes share a current source — dependent or independent — in common.



Figs (a); (b): Two meshes with a common current source; Supermesh created by excluding (6A & 2Ω) element

$$i_1 + i_2 = i_0$$



11) The supermesh in (b) <sup>forms</sup> the periphery of the two meshes, and is treated separately. A circuit consisting of two (or more) intersecting supermeshes should be resolved by combining these supermeshes to form a larger supermesh.

Supermeshes are treated differently because KVL used in mesh analysis requires a knowledge of the voltage across each branch, ~~but~~ ~~but~~ the voltage across a current source is not known in advance. They must however, satisfy KVL like any other mesh.

Applying KVL to the supermesh in (b):

$$20 = 6i_1 + 10i_2 + 4i_2$$

$$20 = 6i_1 + 14i_2 \quad \text{--- (i)}$$

Applying KCL to any node (a or b) where the two meshes intersect:

$i_1$  and 6A flows into node a and out of node b

$i_2$  flows out of node a and enters node b

hence,

$$i_1 + 6 = i_2 \quad \text{--- (ii)}$$

Substituting (ii) into (i)

$$\Rightarrow 20 = 6i_1 + 14(i_1 + 6)$$



$$20 = 6i_1 + 14i_1 + 84$$

$$-64 = 20i_1$$

$$i_1 = \frac{-64}{20} = \underline{\underline{-3.2 \text{ A}}}$$

$$\text{and } i_2 = i_1 + 6 = -3.2 + 6 = 2.8$$

$$i_2 = \underline{\underline{2.8 \text{ A}}}$$

Conclusively, in solving circuits with supermesh(es), the following need to be known:

- (i) The current source in the supermesh provides the constraint equation necessary to solve for the mesh currents.
- (ii) A supermesh has no currents of its own.
- (iii) A supermesh requires the application of both KVL & KCL.

Example:

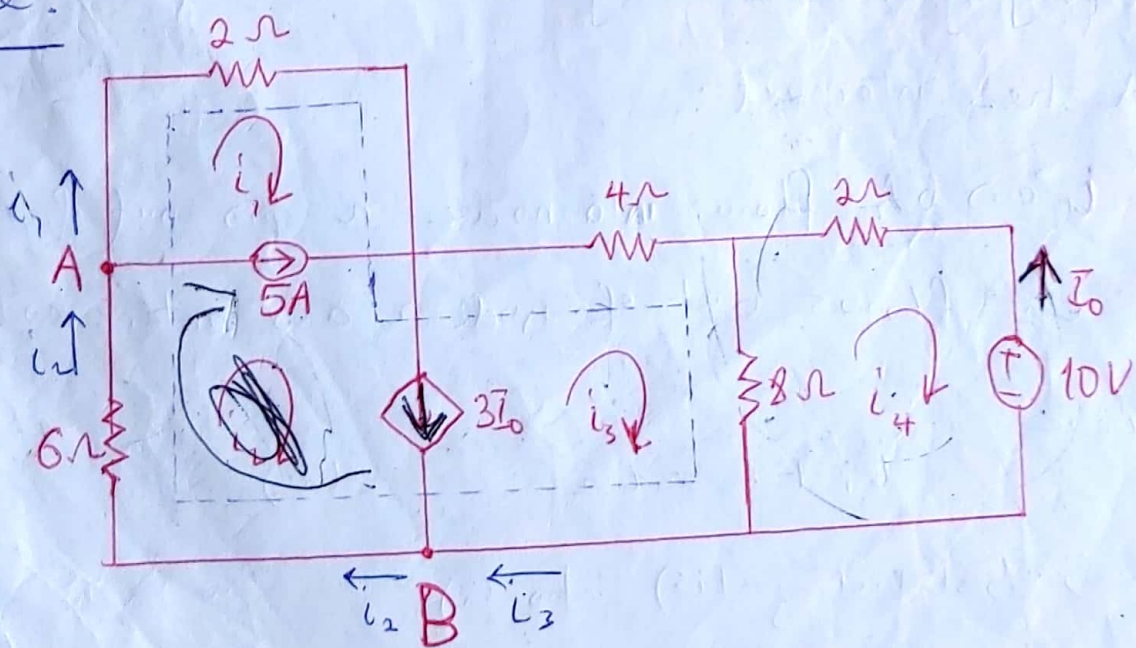


Fig: for mesh analysis example.



12 Find  $i_1, i_2, i_3$  and  $i_4$  using mesh analysis for the circuit shown.

### Analysis:

- Meshes 1 and 2 form a supermesh since they have an independent current source  $(5A)$  in common.
- Meshes 2 and 3 also form another supermesh because they have a dependent current source  $3I_o$  in common.
- These two supermeshes intersect to form a larger supermesh.

Applying KVL to the larger supermesh:

$$\cancel{2i_1} + \cancel{4i_3}$$

$$2i_1 + 4i_3 + 8(i_3 - i_4) + 6i_2 = 0$$

$$2i_1 + 12i_3 + 6i_2 - 8i_4 = 0$$

$$i_1 + 6i_3 + 3i_2 - 4i_4 = 0 \quad \text{--- (i)}$$

For the  $5A$  independent current source, KCL is applied at node A:

$$i_2 = i_1 + 5 \quad \text{--- (ii)}$$

For the dependent current source  $3I_o$ , KCL is applied at node B:

$$i_2 = i_3 + 3I_o$$



$$\text{but } I_0 = -i_4$$

$$\Rightarrow i_2 = i_3 - 3i_4 \quad \text{--- (iii)}$$

Applying KVL to mesh 4!

$$10 + 2i_4 + 8i_4 - 8i_3 = 0$$

$$10 = -10i_4 + 8i_3$$

$$5 = -5i_4 + 4i_3 \quad \text{--- (iv)}$$

Substitution in (iv) into (iii) i.e.

$$10i_4 = 4i_3 - 5$$

$$i_4 = \frac{4i_3 - 5}{10}$$

$$\Rightarrow i_2 = i_3 - 3\left(\frac{4i_3 - 5}{10}\right) = i_1 + 5$$

$$\Rightarrow 10i_3 - 3(4i_3 - 5) = 10i_1 + 50$$

$$10i_1 = 10i_3 - 12i_3 + 15 - 50$$

$$10i_1 = -2i_3 - 35$$

So we have 4 equations - 4 unknowns i.e.

$$i_1 + 3i_2 + 6i_3 - 4i_4 = 0 \quad \text{--- (i)}$$

$$i_1 - i_2 = -5 \quad \text{--- (ii)}$$

$$i_2 - i_3 + 3i_4 = 0 \quad \text{--- (iii)}$$

$$4i_3 - 5i_4 = 5 \quad \text{--- (iv)}$$

From (ii)  $i_1 = i_2 - 5$

put this into (i):



13  
 $i_2 - 5 + 3i_2 + 6i_3 - 4i_4 = 0$

$$4i_2 + 6i_3 - 4i_4 = 5 \quad \text{--- (v)}$$

From (iii),  $i_2 = i_3 - 3i_4$

Put this into (v):

$$4(i_3 - 3i_4) + 6i_3 - 4i_4 = 5$$

$$4i_3 - 12i_4 + 6i_3 - 4i_4 = 5$$

$$10i_3 - 16i_4 = 5 \quad \text{--- (vi)}$$

From (iv),  ~~$i_3$~~   $i_3 = \frac{5 + 5i_4}{4}$

Put this into (vi):

$$10 \left( \frac{5 + 5i_4}{4} \right) - 16i_4 = 5$$

$$12.5 + 12.5i_4 - 16i_4 = 5$$

$$12.5i_4 - 16i_4 = -7.5$$

$$-3.5i_4 = -7.5$$

$$i_4 = \frac{-7.5}{-3.5} = 2.142865$$

$$i_4 = \underline{\underline{2.143 \text{ A}}}$$

Substituting this into eq. (iv):

$$4i_3 - 5(2.142865) = 5$$

$$4i_3 = 5 + 10.714325 = 15.714325$$



$$i_3 = \frac{15.714325}{4} = 3.92858$$

$$i_3 \approx \underline{\underline{3.930A}}$$

from (ii),  $i_2 = i_3 - 3i_4 = 3.93 - 3(2.143)$

$$i_2 = 3.93 - 6.429 = -2.499$$

$$\therefore i_2 \approx \underline{\underline{-2.50A}}$$

from (ii),  $i_1 = i_2 - 5$

$$\Rightarrow i_1 = -2.50 - 5 = -7.50$$

$$\therefore i_1 = \underline{\underline{-7.50A}}$$

### Exercise

Use mesh analysis to determine  $i_1$ ,  $i_2$  and  $i_3$  in the circuit below.

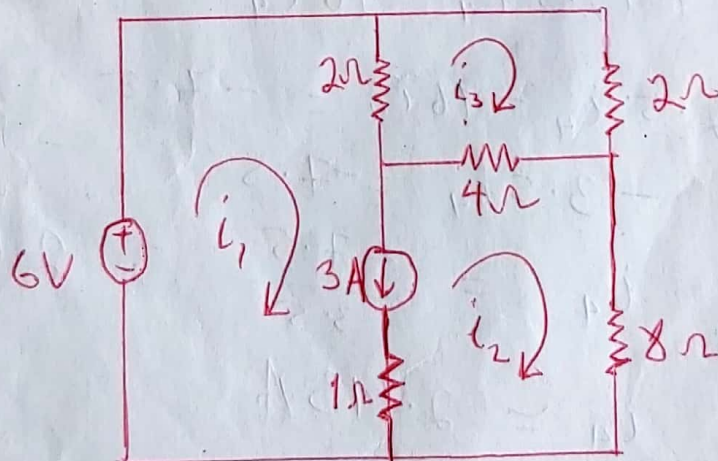


Fig: for exercise above

$$\text{Ans: } i_1 = 3.474A; i_2 = 0.4737A$$

$$i_3 = 1.1052A$$